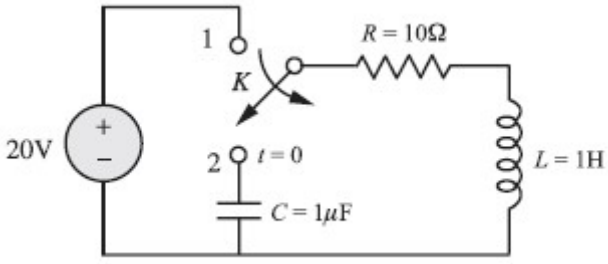
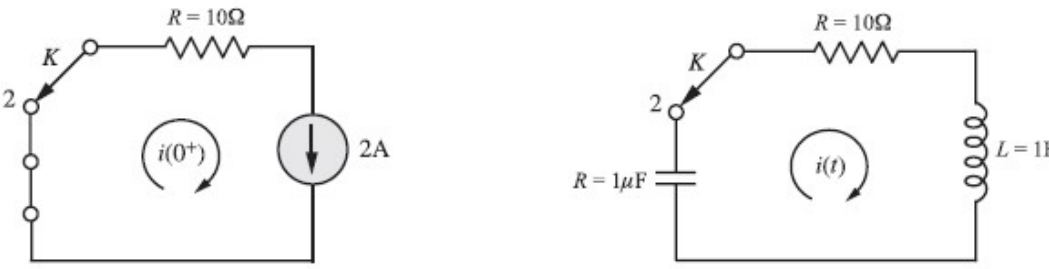


Internal Test 2–December 2024

Scheme and solution

Sub: Network Analysis Code: BEC304

Note: Answer any FIVE full questions with neat diagram wherever necessary.

	Marks	OBE	
		CO	RB T
<p>1.</p>  <p>Refer to the circuit shown. The switch K is changed from position 1 to position 2 at <math>t=0</math>. The steady-state condition has been reached at position 1, find the values of <math>i</math>, <math>\frac{di}{dt}</math>, <math>\frac{d^2i}{dt^2}</math> at <math>t=0^+</math></p> $i(0^-) = \frac{20}{10} = 2A$ <p>.....2M</p>  <p>.....2M</p>	[10]	CO3	L3

$$Ri(t) + L \frac{di(t)}{dt} + \frac{1}{C} \int_{0^+} i(\tau) d\tau = 0$$

$$\Rightarrow Ri(t) + L \frac{di(t)}{dt} + v_C(t) = 0$$

At  $t = 0^+$  equation (4.3a) becomes

$$Ri(0^+) + L \frac{di(0^+)}{dt} + v_C(0^+) = 0$$

$$\Rightarrow R \times 2 + L \frac{di(0^+)}{dt} + 0 = 0$$

$$\Rightarrow 20 + \frac{di(0^+)}{dt} = 0$$

$$\Rightarrow \frac{di(0^+)}{dt} = -20 \text{ A/sec}$$

Differentiating equation (4.3) with respect to  $t$ , we get

$$R \frac{di}{dt} + L \frac{d^2i}{dt^2} + \frac{i}{C} = 0$$

At  $t = 0^+$ , we get

$$R \frac{di(0^+)}{dt} + L \frac{d^2i(0^+)}{dt^2} + \frac{i(0^+)}{C} = 0$$

$$\Rightarrow R \times (-20) + L \frac{d^2i(0^+)}{dt^2} + \frac{2}{C} = 0$$



Hence,  $\frac{d^2i(0^+)}{dt^2} \approx -2 \times 10^6 \text{ A/sec}^2$  .....6M

2. In the network shown, the input voltage  $V_1(t) = e^{-t}$  for  $t \geq 0$  and is zero for all  $t < 0$ . If the capacitor in the network is initially uncharged, determine  $\frac{dv}{dt}$ ,  $\frac{d^2v}{dt^2}$  and  $\frac{d^3v}{dt^3}$  at  $t=0^+$  at  $t=0^+$ .

[10]

CO3

L3

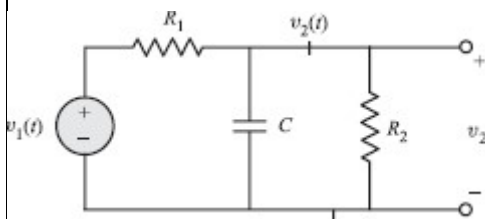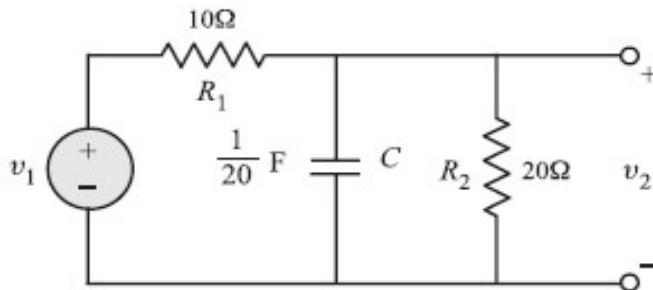

.....2M

$$\frac{v_2(t) - v_1(t)}{R_1} + C \frac{dv_2(t)}{dt} + \frac{v_2(t)}{R_2} = 0$$

$$\Rightarrow \left( \frac{1}{R_1} + \frac{1}{R_2} \right) v_2(t) + C \frac{dv_2(t)}{dt} = \frac{v_1(t)}{R_1}$$

.....2M

Putting  $t = 0^+$ , we get

$$0.15v_2(0^+) + 0.05 \frac{dv_2(0^+)}{dt} = 0.1$$

$$\Rightarrow 0.15 \times 0 + 0.05 \frac{dv_2(0^+)}{dt} = 0.1$$

$$\Rightarrow \frac{dv_2(0^+)}{dt} = \frac{0.1}{0.05} = 2 \text{ Volts/sec}$$

.....3M

Differentiating equation (4.5) with respect to  $t$ , we get

$$0.15 \frac{dv_2}{dt} + 0.05 \frac{d^2v_2}{dt^2} = -0.1e^{-t}$$

Putting  $t = 0^+$  in equation (4.6), we find that

$$\frac{d^2v_2(0^+)}{dt^2} = \frac{-0.1 - 0.3}{0.05} = -8 \text{ Volts/sec}^2$$

Again differentiating equation (4.6) with respect to  $t$ , we get


$$0.15 \frac{d^2v_2}{dt^2} + 0.05 \frac{d^3v_2}{dt^3} = 0.1e^{-t}$$

Putting  $t = 0^+$  in equation (4.7) and solving for  $\frac{d^3v_2}{dt^3}(0^+)$ , we find that

$$\frac{d^3v_2(0^+)}{dt^3} = \frac{0.1 + 1.2}{0.05} = 26 \text{ Volts/sec}^3$$

.....3M

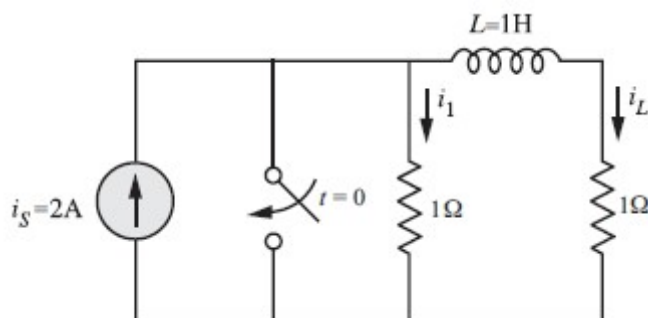
3. Refer the circuit shown . Find  $i_1(0^+)$  and  $i_L(0^+)$ . The circuit is in steady state for  $t < 0$ . (Use any method)



[10]

CO3

L3

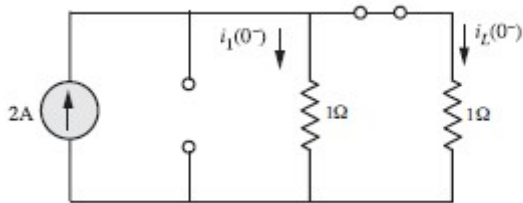

.....3M

$$i_L(0^-) = \frac{2 \times 1}{1 + 1} = 1A$$

.....2M

Since the current in an inductor cannot change instantaneously, we have

$$i_L(0^+) = i_L(0^-) = 1A$$

At  $t = 0^-$ ,  $i_1(0^-) = 2 - 1 = 1A$ . Please note that the current in a resistor can change instantaneously. Since at  $t = 0^+$ , the switch is just closed, the voltage across  $R_1$  will be equal to zero because of the switch being short circuited and hence,

$$i_1(0^+) = 0A$$

Thus, the current in the resistor changes abruptly from 1A to 0A.

.....5M

4. State and prove initial and final value theorems.

[10]

CO4

L3

The initial-value theorem allows us to find the initial value  $x(0)$  directly from its Laplace transform  $X(s)$ .

If  $x(t)$  is a causal signal,

then, 
$$x(0) = \lim_{s \rightarrow \infty} sX(s)$$

**Proof:**

To prove this theorem, we use the time differentiation property.

$$\mathcal{L} \left\{ \frac{dx(t)}{dt} \right\} = sX(s) - x(0) = \int_0^{\infty} \frac{dx}{dt} e^{-st} dt$$

If we let  $s \rightarrow \infty$ , then the integral on the right side of equation (5.10) vanishes due to damping factor,  $e^{-st}$ .

Thus, 
$$\lim_{s \rightarrow \infty} [sX(s) - x(0)] = 0$$
  

$$\Rightarrow x(0) = \lim_{s \rightarrow \infty} sX(s)$$

Statement: 2M

Proof: 3M

The final-value theorem allows us to find the final value  $x(\infty)$  directly from its Laplace transform  $X(s)$ .

If  $x(t)$  is a causal signal,

then 
$$\lim_{t \rightarrow \infty} x(t) = \lim_{s \rightarrow 0} sX(s)$$

**Proof:**

The Laplace transform of  $\frac{dx(t)}{dt}$  is given by

$$sX(s) - x(0) = \int_0^{\infty} \frac{dx(t)}{dt} e^{-st} dt$$

Taking the limit  $s \rightarrow 0$  on both the sides, we get

$$\begin{aligned} \lim_{s \rightarrow 0} [sX(s) - x(0)] &= \lim_{s \rightarrow 0} \int_0^{\infty} \frac{dx(t)}{dt} e^{-st} dt \\ &= \int_0^{\infty} \frac{dx(t)}{dt} \left[ \lim_{s \rightarrow 0} e^{-st} \right] dt \\ &= \int_0^{\infty} \frac{dx(t)}{dt} dt \\ &= x(t) \Big|_0^{\infty} \\ &= x(\infty) - x(0) \end{aligned}$$

Since,

$$\lim_{s \rightarrow 0} [sX(s) - x(0)] = \lim_{s \rightarrow 0} [sX(s)] - x(0)$$

we get,

$$x(\infty) - x(0) = \lim_{s \rightarrow 0} [sX(s) - x(0)]$$

Hence,

$$x(\infty) = \lim_{s \rightarrow 0} [sX(s)]$$

This proves the final value theorem.

Statement: 2M

Proof: 3M

5. Obtain the Laplace transform of  
i) Step function  
ii) Ramp function  
iii) Impulse function

[10]

CO4

L3

**Unit step function**

$$\begin{aligned} f(t) &= u(t) \\ \mathcal{L}\{u(t)\} = F(s) &= \int_0^{\infty} e^{-st} dt = \frac{1}{s} \end{aligned}$$

.....3M

**Impulse function**

$$\begin{aligned} f(t) &= \delta(t) \\ \mathcal{L}\{\delta(t)\} = F(s) &= \int_0^{\infty} \delta(t) e^{-st} dt = e^{-st} \Big|_{t=0} = 1 \end{aligned}$$

.....3M

**Ramp function**



$F(t)=t u(t)$

$$\mathcal{L}\{u(t)\} = F(s) = \int_0^{\infty} t e^{-st} dt :$$

$F(s)=1/s^2$

.....4M

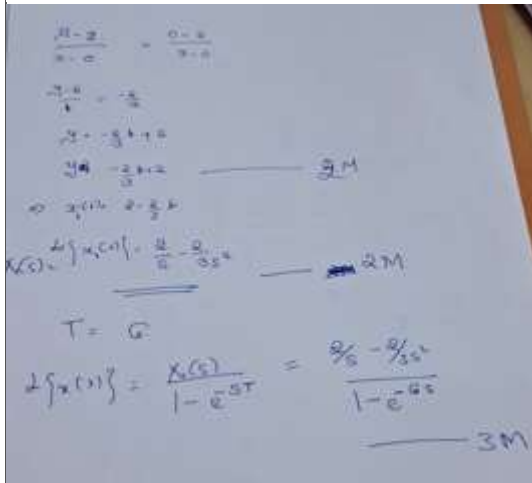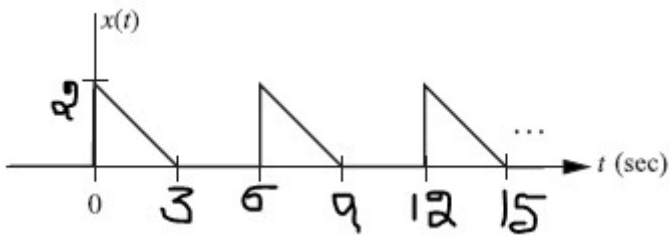6. a. Find the Laplace transform of the periodic signal  $x(t)$ .



b. List any three properties of Laplace transform and write the relevant equations.

$\mathcal{L}\{f_1(t) + f_2(t)\} = F_1(s) + F_2(s)$   
 $\mathcal{L}\{x(t - t_0) u(t - t_0)\} = e^{-t_0 s} X(s)$   
 $\mathcal{L}\{e^{at} u(t)\} = \frac{1}{s - a}$


3\*1=3M

7. a. Develop the time domain equation  $v(t)$  of the staircase waveform shown. (in terms of unit step functions).

[7] CO4 L3

[3] CO4 L2


[2] CO4 L3

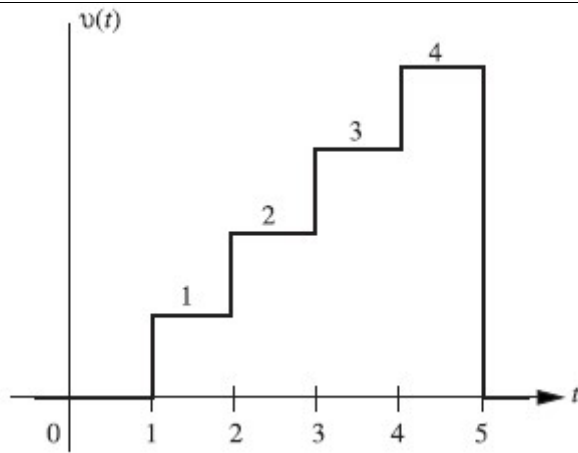

$$\begin{aligned}
 v(t) &= [u(t-1) - u(t-2)] + 2[u(t-2) - u(t-3)] \\
 &\quad + 3[u(t-3) - u(t-4)] + 4[u(t-4) - u(t-5)] \\
 &= u(t-1) + u(t-2) + u(t-3) + u(t-4) - 4u(t-5)
 \end{aligned}$$

.....2M

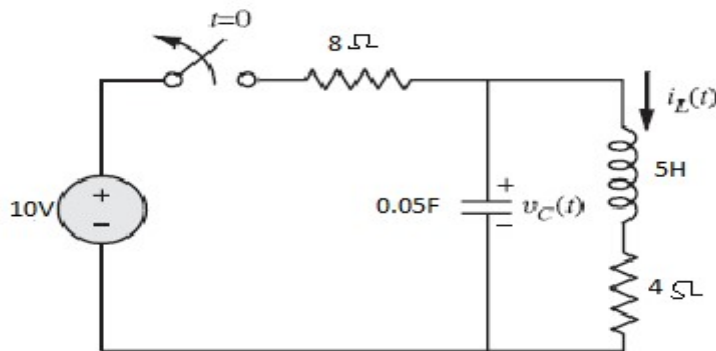b. Determine the current  $i_L(t)$  for  $t > 0$  for the circuit shown using Laplace transform. Write the equivalent circuit in complex frequency domain for  $t > 0$ .



[8]



CO4

L3

$$\begin{aligned}
 & \frac{+10}{3s} - \frac{20}{s} = 5s i_L + \frac{5s}{s} i_L - 0 \\
 & \frac{10}{3s} + \frac{0}{s} = \left[ \frac{20}{s} + 5s + 5 \right] i_L(s) \\
 & i_L(s) = \frac{10}{3} \frac{s}{s^2 + 5s + 4} \\
 & = \frac{10}{3} \frac{s}{(s+1)(s+4)} \\
 & = \frac{10}{3} \left[ \frac{A}{s+1} + \frac{B}{s+4} \right] \\
 & = \frac{10}{3} \left[ \frac{1}{s+1} - \frac{1}{s+4} \right] \\
 & = \frac{10}{3} \left[ 1 - e^{-4t} - (1 - e^{-t}) \right] \\
 & = \frac{10}{3} \left[ e^{-t} - e^{-4t} \right]
 \end{aligned}$$

$$i_L(t) = (1 - e^{-2t}) \text{ A}$$

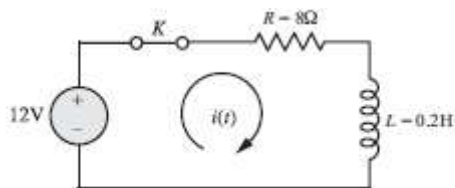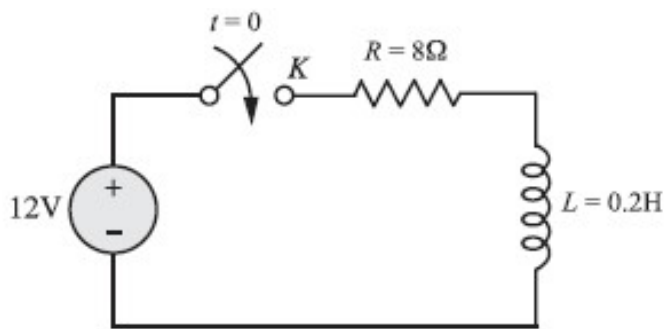8. a. In the given network, K is closed at  $t=0$  with zero current in the inductor. Find the values of  $i$ ,  $\frac{di}{dt}$ ,  $\frac{d^2i}{dt^2}$  at  $t=0^+$



.....2M

[8] CO3 L3

[2] CO3 L2



Applying KVL clockwise to the circuit shown in Fig. 4.12(b), we get

$$ti + L \frac{di}{dt} = 12$$

$$\Rightarrow 8i + 0.2 \frac{di}{dt} = 12$$

At  $t = 0^+$ , the equation (4.1) becomes

$$8i(0^+) + 0.2 \frac{di(0^+)}{dt} = 12$$

$$\Rightarrow 8 \times 0 + 0.2 \frac{di(0^+)}{dt} = 12$$

$$\Rightarrow \frac{di(0^+)}{dt} = \frac{12}{0.2} = 60 \text{ A/sec} \quad \dots\dots\dots 3M$$

Differentiating equation (4.1) with respect to  $t$ , we get

$$8 \frac{di}{dt} + 0.2 \frac{d^2i}{dt^2} = 0$$

At  $t = 0^+$ , the above equation becomes


$$8 \frac{di(0^+)}{dt} + 0.2 \frac{d^2i(0^+)}{dt^2} = 0$$

$$\Rightarrow 8 \times 60 + 0.2 \frac{d^2i(0^+)}{dt^2} = 0$$

Hence  $\frac{d^2i(0^+)}{dt^2} = -2400 \text{ A/sec}^2$

.....3M

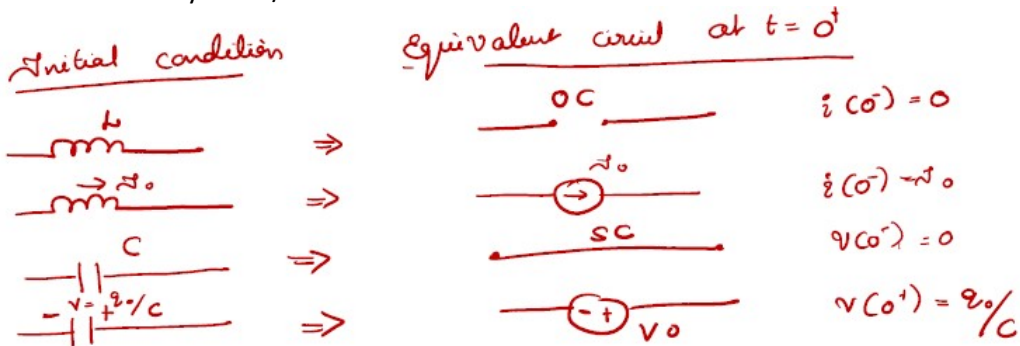b. List the initial conditions of inductor and capacitor with relevant equivalent circuit elements at steady state /  $t=0^-$  and  $t=0^+$



.....2M