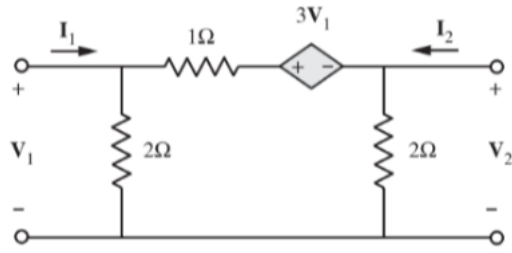
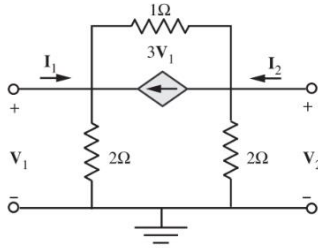
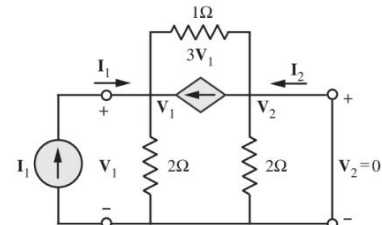


FOR 3A AND 3C ONLY
Internal Test 2 –December 2024

Sub:	Network Analysis							Code:	BEC304
Date:	17/12/2024	Duration:	90 mins	Max Marks:	50	Sem:	3 A&C	Branch:	ECE
Note: Answer any FIVE full questions with neat diagram wherever necessary.									

1	Find Y parameters of the network shown in Figure Q1.	Marks	OBE	
			CO	RBT
		[5+5]	CO5	L3
				
<p>Figure Q 1</p> <p>figure 7.13</p>				
<p>SOLUTION</p> <p>Converting the voltage source into an equivalent current source, we get the circuit diagram shown in Fig. 7.14(a).</p> <p>To find y_{11} and y_{21}, the output terminals of Fig. 7.14(a) are shorted and connect a current source I_1 to the input terminals. This results in a circuit diagram as shown in Fig. 7.14(b).</p>				
 				
<p style="text-align: center;">Figure 7.14(a) Figure 7.14(b)</p>				
<p><i>KCL at node V₁:</i></p> $\frac{V_1}{2} + \frac{V_1 - V_2}{1} = I_1 + 3V_1$				

Since $V_2 = 0$, we get

$$\frac{V_1}{2} + V_1 = I_1 + 3V_1$$

$$\Rightarrow I_1 = \frac{-3}{2}V_1$$

Hence,
$$y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0} = \frac{-3}{2}S$$

KCL at node V_2 :

$$\frac{V_2}{2} + 3V_1 + \frac{V_2 - V_1}{1} = I_2$$



Since $V_2 = 0$, we get

$$0 + 3V_1 - V_1 = I_2$$

$$\Rightarrow I_2 = 2V_1$$

Hence
$$y_{21} = \frac{I_2}{V_1} = 2S$$

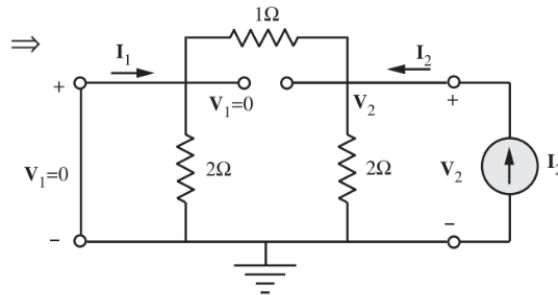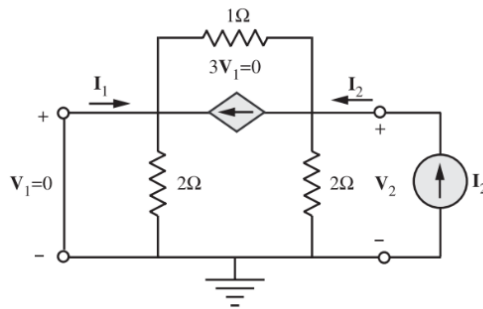To find y_{21} and y_{22} , the input terminals of Fig. 7.14(a) are shorted and connect a current source I_2 to the output terminals. This results in a circuit diagram as shown in Fig. 7.14(c).



KCL at node V_2 :

$$\frac{V_2}{2} + \frac{V_2 - 0}{1} = I_2$$

$$\Rightarrow \frac{3}{2}V_2 = I_2$$

Hence,
$$y_{22} = \frac{I_2}{V_2} = \frac{3}{2}S$$

KCL at node V_1 :

$$I_1 = \frac{V_1}{2} + \frac{V_1 - V_2}{1} = 0$$

Since $V_1 = 0$, we get

$$I_1 = -V_2$$

Hence,
$$y_{12} = \frac{I_1}{V_2} = -1S$$

Transmission Parameters!

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

In matrix form:


$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0}$$

⇒ open circuit voltage ratio

$$B = \left. \frac{V_1}{-I_2} \right|_{V_2=0}$$

⇒ negative short circuit transfer imp.

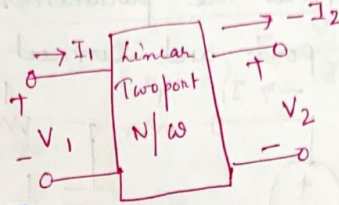

$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0}$$

⇒ open circuit transfer admittance

$$D = \left. \frac{I_1}{-I_2} \right|_{V_2=0}$$

⇒ negative short circuit current ratio

2b) Z parameters of a network are obtained from an experiment. Explain how h parameters can be obtained from the data.

[6] CO5 L1

b) Relation between Z parameters and h parameters (45)

The Z parameter equations are $V_1 = Z_{11}I_1 + Z_{12}I_2$ — (1)

$V_2 = Z_{21}I_1 + Z_{22}I_2$ — (2)

h-parameter equations are

$$V_1 = h_{11}I_1 + h_{12}V_2$$
 — (3)

$$I_2 = h_{21}I_1 + h_{22}V_2$$
 — (4)

from eqn (4) $h_{22}V_2 = I_2 - h_{21}I_1$.

$$V_2 = \frac{1}{h_{22}}I_2 - \frac{h_{21}}{h_{22}}I_1$$
 — (5)

Substituting (5) in eqn (3).

$$V_1 = h_{11}I_1 + h_{12} \left[\frac{1}{h_{22}}I_2 - \frac{h_{21}}{h_{22}}I_1 \right]$$

$$\Rightarrow V_1 = I_1 \left[\frac{h_{11}h_{22} - h_{12}h_{21}}{h_{22}} \right] + \frac{h_{12}}{h_{22}}I_2$$

$$\Rightarrow \boxed{V_1 = I_1 \left[\frac{\Delta h}{h_{22}} \right] + \frac{h_{12}}{h_{22}}I_2} \rightarrow (6)$$

from eqn (5) $V_2 = \frac{1}{h_{22}} I_2 - \frac{h_{21}}{h_{22}} I_1$

$$0_2 V_2 = -\frac{h_{21}}{h_{22}} I_1 + \frac{1}{h_{22}} I_2 \quad (7)$$

Comparing (1) with (6) and (2) with (7)

$$Z = \begin{bmatrix} \frac{\Delta h}{h_{22}} & \frac{h_{12}}{h_{22}} \\ -\frac{h_{21}}{h_{22}} & \frac{1}{h_{22}} \end{bmatrix}$$

3a Prove Initial and Final value Theorem with respect to Laplace Transform.

[5] CO4 L1

Initial Value Theorem:

Initial value theorem allows us to find the initial value $x(0)$ directly from its L.T $X(s)$

$$x(0) = \lim_{s \rightarrow \infty} sX(s).$$

Proof:

We know that,

$$L\left\{\frac{dx(t)}{dt}\right\} = sX(s) - x(0) = \int_0^{\infty} \frac{dx}{dt} e^{-st} dt = 0$$

$\therefore e^{-\infty} = 0.$

If $s \rightarrow \infty$, then

$$\lim_{s \rightarrow \infty} [sX(s) - x(0)] = 0; \quad \lim_{s \rightarrow \infty} [sX(s)] - x(0) = 0.$$

$$x(0) = \lim_{s \rightarrow \infty} [sX(s)].$$

FINAL VALUE THEOREM:

The final value theorem allow us to find the final value $x(\infty)$ directly from its L.T $X(s)$.

If $x(t)$ casual signal.

$$\lim_{t \rightarrow \infty} x(t) = \lim_{s \rightarrow 0} sX(s)$$

Proof: $L\left\{\frac{dx(t)}{dt}\right\} = sX(s) - x(0) = \int_0^{\infty} \frac{dx}{dt} e^{-st} dt$

$$\begin{aligned} \text{if } s \rightarrow 0 \\ \lim_{s \rightarrow 0} [sX(s) - x(0)] &= \lim_{s \rightarrow 0} \int_0^{\infty} \frac{dx}{dt} e^{-st} dt \\ &= \int_0^{\infty} \frac{dx(t)}{dt} \left[\lim_{s \rightarrow 0} e^{-st} \right] dt \\ &= \int_0^{\infty} \frac{dx(t)}{dt} dt = x(t) \Big|_0^{\infty} \\ &= x(\infty) - x(0). \end{aligned}$$

$$\lim_{s \rightarrow 0} [sX(s) - x(0)] = \lim_{s \rightarrow 0} sX(s) - x(0).$$

$$x(\infty) - x(0) = \lim_{s \rightarrow 0} sX(s) - x(0).$$

$$x(\infty) = \lim_{s \rightarrow 0} sX(s).$$

3b Determine Laplace Transform of a) Unit Step Function, b) Ramp Function.

[5]

CO4

L1

Laplace Transform of unit step function:

$$u(t) = \begin{cases} 1 & t \geq 0 \\ 0 & t < 0 \end{cases}$$

$$\begin{aligned} \mathcal{L}\{u(t)\} = F(s) &= \int_0^{\infty} 1 \cdot e^{-st} dt = \left[-\frac{1}{s} e^{-st} \right]_0^{\infty} \\ &= \frac{1}{s} \end{aligned}$$

Laplace transform of ramp function.

Ramp function is defined as $x(t) = tu(t)$

$$\begin{aligned} \mathcal{L}\{x(t)\} &= \mathcal{L}\{tu(t)\} = \int_0^{\infty} tu(t)e^{-st} dt \\ &= \int_0^{\infty} te^{-st} dt \\ &= \left[\frac{te^{-st}}{s} \right]_0^{\infty} - \int_0^{\infty} (1) \frac{e^{-st}}{-s} dt \\ &= 0 - \left[\frac{e^{-st}}{s^2} \right]_0^{\infty} = \left(0 - \frac{1}{s^2} \right) = \frac{1}{s^2} \end{aligned}$$

4. The switch in the network shown in Figure Q4 is closed at $t=0$. Find the voltage across Capacitor using Laplace transform.

[10] CO4 L3


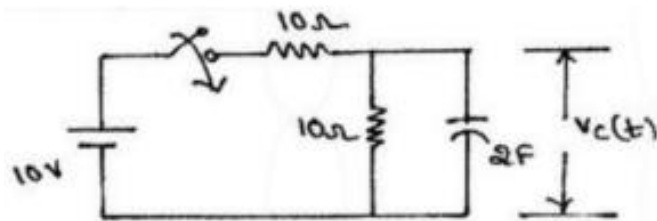



Figure Q 4

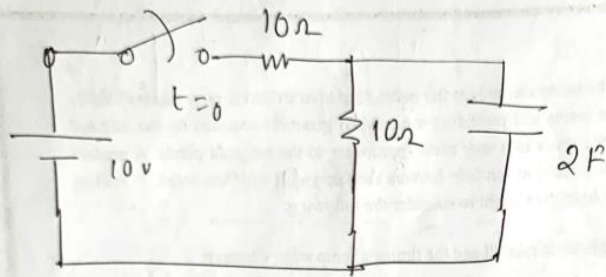

as circuit not activated at $t=0^-$,
 so $V_C(0^-) = 0$

Hence $V_C(0^+) = 0$

Circuit in frequency domain

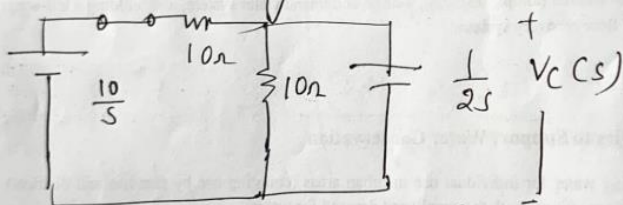

Applying KCL at node $V_C(s)$

$$V_C(s) \left[\frac{1}{10} + \frac{1}{10} + 2s \right] = \frac{10}{s \times 10}$$

$$\text{or } V_C(s) \frac{2+20s}{10} = \frac{1}{s}$$

$$\text{or } V_C(s) = \frac{5}{s(10s+1)}$$

$$= \frac{A}{s} + \frac{B}{10s+1}$$

$$= \frac{10As + Bs + A}{s(10s+1)}$$

Comparing $10A + B = 0$

$$A = 5$$

$$\therefore B = -50$$

$$\therefore V_c(s) = \frac{5}{s} - \frac{50}{s+0.1}$$

$$V_c(t) = 5u(t) - 5e^{-0.1t}u(t)$$

$$V_c(t) = 5u(t) [1 - e^{-0.1t}] \quad \underline{\underline{\text{Ans}}}$$

5. Given the signal

$$x(t) = \begin{cases} 3, & t < 0 \\ -2, & 0 < t < 1 \\ 2t - 4, & t > 1 \end{cases}$$

Find Laplace Transform in terms of singularity function.

Given the signal

$$x(t) = \begin{cases} 3, & t < 0 \\ -2, & 0 < t < 1 \\ 2t - 4, & t > 1 \end{cases}$$

Express $x(t)$ in terms of singularity functions. Also find $\mathcal{L}\{x(t)\}$.

SOLUTION

The signal $x(t)$ may be viewed as follows:

- (i) in the interval, $t < 0$, $x(t)$ may be regarded as $3u(-t)$
- (ii) in the interval, $0 < t < 1$, $x(t)$ may be viewed as $-2[u(t) - u(t-1)]$ and
- (iii) for $t > 1$, $x(t)$ may be viewed as $(2t-4)u(t-1)$

Thus,

$$\begin{aligned} x(t) &= 3u(-t) - 2[u(t) - u(t-1)] + (2t-4)u(t-1) \\ \Rightarrow x(t) &= 3[1 - u(t)] - 2u(t) + 2u(t-1) + 2tu(t-1) - 4u(t-1) \\ &= 3 - 5u(t) - 2u(t-1) + 2(t-1+1)u(t-1) \\ &= 3 - 5u(t) - 2u(t-1) + 2(t-1)u(t-1) + 2u(t-1) \\ &= 3 - 5u(t) + 2r(t-1) \end{aligned}$$

$\mathcal{L}\{x(t)\}$ cannot be found because $x(t)$ contains a constant 3 for $-\infty < t < 0$ (a noncausal signal).

6. Determine the Laplace transform of the following stair case wave form using gate function.

[10] CO4 L3

[10] CO4 L4

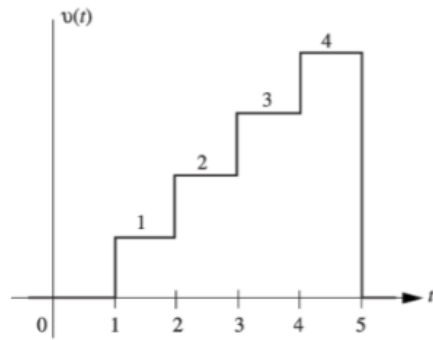


Figure Q6

Solution!

$$v(t) = \begin{cases} 1 & 1 < t < 2 \\ 2 & 2 < t < 3 \\ 3 & 3 < t < 4 \\ 4 & 4 < t < 5 \\ 0 & \text{elsewhere} \end{cases}$$

$$\therefore v(t) = [u(t-1) - u(t-2)] + 2[u(t-2) - u(t-3)] + 3[u(t-3) - u(t-4)] + 4[u(t-4) - u(t-5)]$$

$$= u(t-1) + u(t-2) + u(t-3) + u(t-4) - 4u(t-5)$$

$$\therefore V(s) = \frac{1}{s}e^{-s} + \frac{e^{-2s}}{s} + \frac{e^{-3s}}{s} + \frac{e^{-4s}}{s} - \frac{4e^{-5s}}{s}$$

7 A series RLC circuit has a resistance of 10Ω , an inductance of 0.3H and a capacitance of $100\mu\text{F}$. The applied voltage is 220V . Find i) Resonant Frequency, ii) Quality Factor, iii) Lower and upper cut off frequencies, iv) Band width, v) current at resonance, and vi) voltage across inductance at resonance.

[10]

CO6

L1

$$f_0 = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{0.3 \times 100 \times 10^{-6}}} = 29.05 \text{ Hz}$$

$$B.W = \frac{R}{2\pi L} = \frac{10}{2\pi \times 0.3} = 5.30 \text{ Hz}$$

$$Q_1 = \frac{1}{R} \sqrt{\frac{L}{C}} = 5.47$$

$$B.W = f_2 - f_1 = 5.30$$

$$f_0 = \sqrt{f_1 f_2}$$

$$f_0^2 = f_1 f_2 = 843.90$$

$$f_1 (5.30 + f_1) = 843.90$$

$$f_1^2 + 5.30 f_1 - 843.9 = 0$$

$$f_1 = 1.58 \text{ Hz}$$

$$f_2 = 1.58 + 5.30 = 6.88 \text{ Hz}$$

$$\text{Current at resonance} = \frac{V}{R} = \frac{220}{10} = 22 \text{ A}$$

$$\text{Voltage across inductance} = jX_L V = 90 \text{ V}$$

$$= j 5.47 \times 220 = j 1203 \text{ V}$$

8 Derive the expressions of half power frequencies in terms of resonant frequency, also derive the expression for bandwidth in terms circuit parameters for a series R, L, C circuit.

[10] CO6 L2

Current in the series RLC circuit is given by,

$$I = \frac{V}{\sqrt{R^2 + (X_L - X_C)^2}} \quad \text{--- (1)}$$

Also at resonance cut off frequency,

$$I = \frac{I_0}{\sqrt{2}}, \text{ where } I_0 \text{ is maximum current}$$

$$I = \frac{V}{R\sqrt{2}} \quad \text{--- (2)}$$

Equating (1) and (2)

$$\frac{V}{\sqrt{R^2 + (X_L - X_C)^2}} = \frac{V}{R\sqrt{2}}$$

$$\Rightarrow 2R^2 = R^2 + (X_L - X_C)^2$$

$$\Rightarrow R^2 = \left(\omega L - \frac{1}{\omega C}\right)^2$$

$$\text{or } \omega L - \frac{1}{\omega C} = \pm R. \quad \text{--- (3)}$$

At upper cut off frequency, f_2

$$R = \omega_2 L - \frac{1}{\omega_2 C} \quad \text{--- (4)}$$

At lower cut off frequency

$$-R = \omega_1 L - \frac{1}{\omega_1 C} \quad \text{--- (5)}$$

Adding (4) and (5)

$$\omega_2 L - \frac{1}{\omega_2 C} + \omega_1 L - \frac{1}{\omega_1 C} = R - R$$

$$\Rightarrow L(\omega_2 + \omega_1) - \frac{1}{C} \left(\frac{1}{\omega_2} + \frac{1}{\omega_1}\right) = 0$$

$$\Rightarrow L(\omega_2 + \omega_1) = \frac{1}{C} \left(\frac{\omega_1 + \omega_2}{\omega_1 \omega_2}\right)$$

$$L = \frac{1}{C} \times \frac{1}{\omega_1 \omega_2}$$

$$\Rightarrow \omega_1 \omega_2 = \frac{1}{LC}$$

$$\Rightarrow \omega_1 \omega_2 = \omega_0^2 \quad \left[\text{as } \omega_0^2 = \frac{1}{LC} \right]$$

$$\Rightarrow \boxed{f_1 f_2 = f_0^2}$$

\Rightarrow In series resonance circuit resonant frequency f_0 is geometrical mean of f_1 & f_2 .

Subtracting eqn (4) and (5)

$$\omega_2 L - \frac{1}{\omega_2 C} - \omega_1 L + \frac{1}{\omega_1 C} = R - (-R)$$

$$\Rightarrow L(\omega_2 - \omega_1) - \frac{1}{C} \left(\frac{\omega_1 - \omega_2}{\omega_1 \omega_2} \right) = 2R$$

$$\Rightarrow L(\omega_2 - \omega_1) + \frac{1}{C} \left(\frac{\omega_2 - \omega_1}{\omega_1 \omega_2} \right) = 2R$$

$$\Rightarrow (\omega_2 - \omega_1) \left[L + \frac{1}{C \omega_0^2} \right] = 2R$$

$$\Rightarrow (\omega_2 - \omega_1) \left[\frac{LC\omega_0^2 + 1}{C\omega_0^2} \right] = 2R$$

$$\Rightarrow (\omega_2 - \omega_1) \left[\frac{L \times \frac{1}{L} + 1}{C\omega_0^2} \right] = 2R$$

$$\Rightarrow \frac{(\omega_2 - \omega_1)}{C\omega_0^2} = R$$

$$\text{or } R = \frac{\omega_2 - \omega_1}{\cancel{L} \times \frac{1}{L\cancel{C}}}$$

$$\Rightarrow \boxed{\omega_2 - \omega_1 = \frac{R}{L}}$$

$$\text{or } \boxed{f_2 - f_1 = \frac{R}{2\pi L}}$$