 


USN

18CS33



Third Semester B.E. Degree Examination, Dec.2024/Jan.2025
Analog and Digital Electronics

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Explain the construction, working and V-I characteristics of photo diode. (06 Marks)
- b. List the different types of BJT biasing. Derive the expression for fixed bias circuit. (06 Marks)
- c. With the help of neat circuit diagram and waveform explain the working principle of relaxation oscillator. (08 Marks)

OR

- 2 a. With a neat waveform and circuit diagram, explain the working of monostable multivibrator. (06 Marks)
- b. Explain the working of R-2R ladder D to A converter. (06 Marks)
- c. Explain performance parameters of a power supply. (08 Marks)

Module-2

- 3 a. A logic circuit realizing the function f has four inputs A, B, C and D. The three inputs A, B and C are the binary representation of the digits 0 through 7 with A being the most significant bit. The input D is an odd parity bit, i.e., the value of D is such that A, B, C and D always contain an odd number of 1's. (For example, the digit 1 is represented by ABCD = 001 and D = 0, and the digit 3 is represented by ABCD = 0111). The function f has value 1 if the input digit is an odd number and value 0 if the input digit is an even number.
 - i) List the minterms and don't-care minterms of f in algebraic form.
 - ii) List the maxterms and don't-care maxterms of f in algebraic form. (10 Marks)
- b. Solve for the Boolean expression using K-map to get minimum SOP and minimum POS expression:
 - i) $f(A, B, C, D) = \sum m(0, 1, 4, 8, 9, 10) + d(2, 11)$
 - ii) $f(A, B, C, D) = \pi M(0, 1, 3, 4, 7)$ (10 Marks)

OR

- 4 a. Determine the essential prime implicants using Q method for the function $f(A, B, C, D) = \sum m(0, 1, 2, 3, 10, 12, 11, 13, 14, 15)$. (10 Marks)
- b. Explain with explain Petrik's method. (06 Marks)
- c. Find the minimum SOP for the function $f(A, B, C) = \sum m(2, 6, 7)$ using Quine McCluskey method. (04 Marks)

Module-3

- 5 a. How do you detect static hazards in combinational logic circuits? Explain with examples. (06 Marks)
- b. With a neat diagram, explain 3 to 8 line decoder. (06 Marks)
- c. Design 7 segment decoder and realize using PLA. (08 Marks)

OR

- 6 a. Implement $Y(A, B, C, D) = \sum m(0, 2, 3, 4, 5, 8, 9, 10, 11, 12, 13, 15)$ using 16 – to -1 multiplexer (IC 74150) and 8 – to -1 multiplexer. (08 Marks)
- b. Implement full adder using PAL. (08 Marks)
- c. Explain simulation and testing of digital circuits. (04 Marks)

Module-4

- 7 a. Explain the structure of VHDL program. Write VHDL code for 4-bit parallel adder using full adder as component. (08 Marks)
- b. Construct SR latch using NAND gates and derive the characteristics equation for the same. (08 Marks)
- c. Differentiate between latch and flip flop. Show how SR flip flop can be converted to D flip flop. (04 Marks)

OR

- 8 a. Derive the characteristics equations for D, T, SR and JK flipflops. (08 Marks)
- b. Explain the working of a JK flip flop. Write its Truth table, state diagram and excitation table. (08 Marks)
- c. Give the implementation of T flip flop from D flip flop. (04 Marks)

Module-5

- 9 a. What is register? Explain how 4 bit register with data, load, clear and clock input is constructed using D flip-flops. (06 Marks)
- b. With a neat diagram, explain 4 bit SISO register. (06 Marks)
- c. Design a random counter using T flip flops whose transition graph is shown in Fig.Q.9(c).

 


Fig.Q.9(c)

(08 Marks)

OR

- 10 a. With the help of state graph, state and transistor tables and timing diagrams explain sequential parity checker. (08 Marks)
- b. Differentiate between Moore and Melay machines. Analyze following Moore sequential circuit for an input sequence of X = 01101 and draw the timing diagram. (08 Marks)
- c. Write a note on Ring counter. (04 Marks)

* * * * *