

USN

BEC304

Third Semester B.E./B.Tech. Degree Examination, Dec.2024/Jan.2025

Network Analysis

Time: 3 hrs.

Max. Marks: 100

Note: 1. Answer any FIVE full questions, choosing ONE full question from each module.
2. M: Marks, L: Bloom's level, C: Course outcomes.

Module - 1			M	L	C
Q.1	a.	Three impedances are connected in Delta. Obtain the star equivalent of the network.	7	L3	CO1
	b.	For the circuit shown in Fig. Q1(b), Find the voltage 'V' at node by using nodal analysis. Fig. Q1(b)	6	L3	CO1
	c.	Determine the current in 12Ω resistor shown in Fig. Q1(c) using source transformation method. Fig. Q1(c)	7	L3	CO1
OR					
Q.2	a.	Find the loop currents I_1 , I_2 , and I_3 in the circuit shown in Fig. Q2(a). Fig. Q2(a)	7	L3	CO1

b. Determine the resistance between the terminals X, Y using star delta transformation in the network shown in Fig. Q2(b).

6 L3 CO1

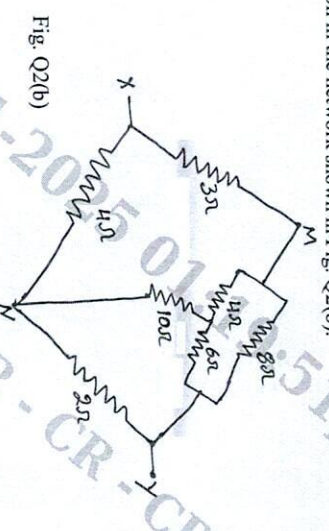


Fig. Q2(b)

c. Use the nodal analysis to find the value of V_x and the circuit shown in Fig. Q2(c). Such that the current through $(2 + j3)\Omega$ impedance is zero.

7 L3 CO1



Fig. Q2(c)

Module - 2

a. State and prove Superposition theorem.

7 L2 CO2

b. For the circuit shown in Fig. Q3(b), obtain the Thevenin's equivalent circuit.

7 L3 CO2

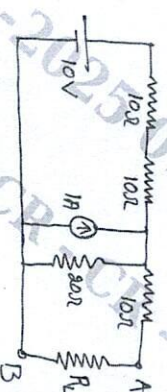


Fig. Q3(b)

c. Using Millman's theorem, find current flowing through $(3 + j4)\Omega$ impedance for the circuit shown in Fig. Q3(c).

6 L3 CO2

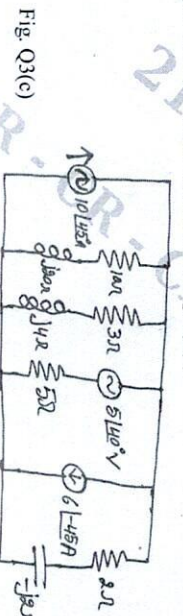
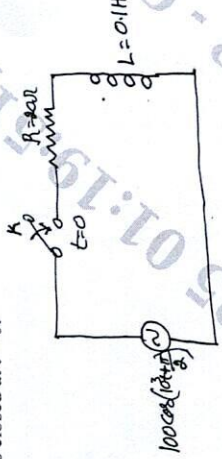
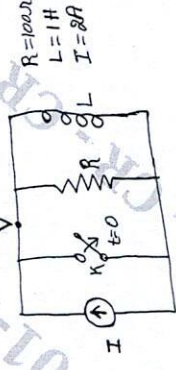
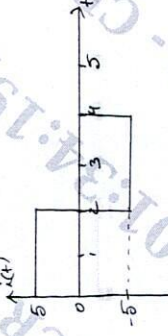
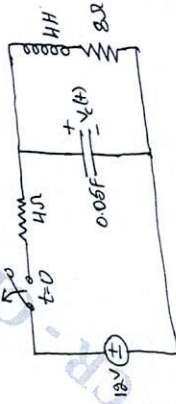


Fig. Q3(c)

OR



Q.6	a.	In the circuit shown in Fig. Q6(a), determine complete solution for current when switch 'K' is closed at $t = 0$.	10	L3	CO3
					
		Fig. Q6(a)			
	b.	Compute v , dv/dt , d^2v/dt^2 at $t = 0^+$ for the circuit shown in below Fig. Q6(b), when the switch K is opened at $t = 0$.	10	L4	CO3
					
		Fig. Q6(b)			

Module - 4



Q.7	a.	Using waveform synthesis method to express the voltage pulse in terms of unit step. Find i) $L\{i(t)\}$ ii) $L\{i(t), dt\}$.	8	L3	CO4
					
		Fig. Q7(a)			
	b.	State and prove initial value and final value theorem for Laplace transform.	6	L2	CO4
	c.	Obtain the Laplace transform of step and ramp function with relevant expressions.	6	L3	CO4
Q.8	a.	Determine $i_L(t)$ for $t \geq 0$ using Laplace transform for circuit shown in Fig. Q8(a).	10	L3	CO4
					
		Fig. Q8(a)			

OR

CMRIT LIBRARY
BANGALORE - 560 037


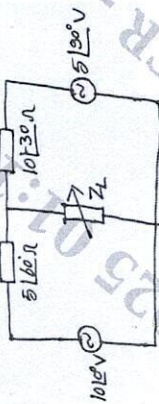
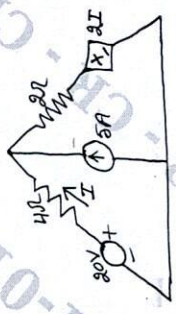
Q.4	a.	State and prove Norton's theorem.	7	L2	CO2
	b.	Find the value of Z_L for Maximum Power transfer and the value of Maximum power for the circuit shown in Fig. Q4(b).	6	L3	CO2
					
		Fig. Q4(b)			
	c.	Find current 'I' using Super position theorem for the circuit shown in Fig. Q4(c).	7	L3	CO2
					
		Fig. Q4(c)			

Module - 3

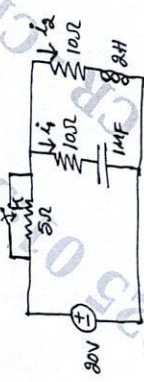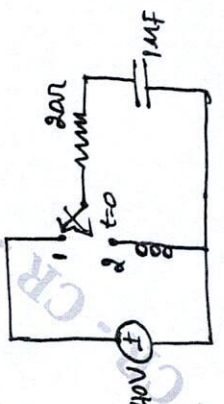Q.5	a.	Use the concepts of initial condition to illustrate the voltage behavior in inductor circuit for DC supply.	6	L3	CO3
	b.	In the circuit steady state is reached with switch 'K' open. The switch is closed at $t = 0$. Compute i , di/dt and d^2i/dt^2 at $t = 0^+$.	7	L3	CO3
					
		Fig. Q5(b)			
	c.	The switch is moved from position (1) to position (2) at $t = 0$. The steady state has been reached before switching. Compute i , di/dt and d^2i/dt^2 at $t = 0^+$ for Fig. Q5(c).	7	L4	CO3
					
		Fig. Q5(c)			

CMRIT LIBRARY
BANGALORE - 560 037

OR

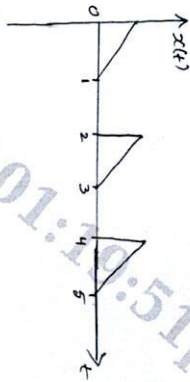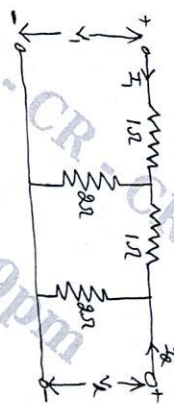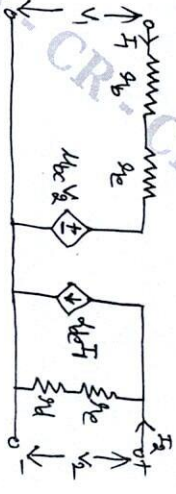b. Find the Laplace transform of the periodic signal $x(t)$ as shown in Fig. Q8(b). Fig. Q8(b) 	10	L3	CO4
Module - 5			
Q.9 a. Define Z – parameters. Determine Y parameters interns if Z – parameters. b. Show that resonant frequency is geometric mean of cut off frequency in series R – L – C circuit. c. Apply the two – port network analysis technique to determine ABCD – parameters of the network shown in Fig. Q9(c). Fig. Q9(c) 	6	L3	CO5
OR			
Q.10 a. Derive the expression for the resonant frequency of the circuit shown in Fig. Q10(a). Also show that the circuit resonate at all frequency if $R_L = R_C = \sqrt{\frac{L}{C}}$. Fig. Q10(a) 	10	L3	CO5
b. The model of a transistor in the CE mode is shown in Fig. Q10(b). Determine the h – parameters. Fig. Q10(b) 	10	L3	CO5



Current Session : 09:30:00

09:30:00 Session is in progress.

09:30:00 Session



Dashboard (dashboard.php)

Download Question Papers (downloadQP.php)

Request Password (requestPass.php)

Request Question Paper (qpRequest.php)

Discrepancy Tab (feedback.php)

CMR INSTITUTE OF TECHNOLOGY KUNDAL HALLI

LOGOUT ! (logout.php)

Feedback/Remarks

Date:21-01-2025 | Session:09:30:00

For Subject Code : BEC304

1. Q. 5) c) the value of the inductor to be taken as 1H (one henry)

CMRIT LIBRARY
BANGALORE - 560 037