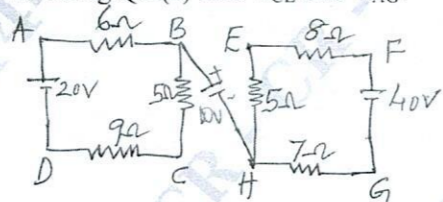
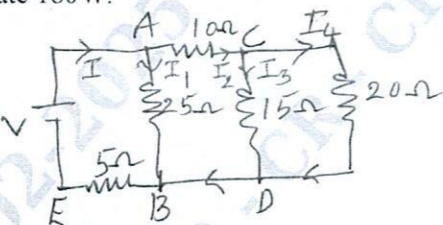


**Second Semester B.E./B.Tech. Degree Examination, Dec.2024/Jan.2025**  
**Introduction to Electrical Engineering**

Time: 3 hrs.

Max. Marks: 100

- Note: 1. Answer any FIVE full questions, choosing ONE full question from each module.  
 2. VTU Formula Hand Book is permitted.  
 3. M : Marks, L: Bloom's level, C: Course outcomes.*

Module – 1				M	L	C
Q.1	a.	Explain a typical electric power system with the help of a labeled single line diagram.		8	L2	CO1
	b.	Draw and explain the working of solar photovoltaic power generation system.		6	L2	CO1
	c.	For the circuit shown in Fig.Q.1(c) find $V_{CE}$ and $V_{AG}$ .		6	L3	CO1
 <p align="center">Fig.Q.1(c)</p>						
OR						
Q.2	a.	List the advantages and disadvantages of conventional and non conventional energy sources.		7	L2	CO1
	b.	State and explain Kirchhoff's laws as applicable to DC circuits.		5	L2	CO1
	c.	In the circuit of Fig.Q.2(c). Find the value of supply voltage V so that $20\Omega$ resistor can dissipate 180W.		8	L3	CO2
 <p align="center">Fig.Q.2(c)</p>						
Module – 2						
Q.3	a.	Define the following terms applied to quantity AC: i) Average value ii) RMS value iii) Form factor iv) Frequency		6	L1	CO2

BESCK204B						
	b.	Establish the relation between voltage and current in ac circuit containing RL in series. Draw the vector diagram.		8	L3	CO2
	c.	List the advantages and limitations of $3\phi$ AC over $1\phi$ AC.		6	L2	CO2
OR						
Q.4	a.	Draw the circuit diagram for three phase star and delta connection. Write the relation between line and phase voltage and currents.		6	L2	CO2
	b.	Define the terms active power, reactive power and apparent power.		6	L1	CO2
	c.	A series circuit with $R = 10\Omega$ , $L = 50\text{ mH}$ and $C = 100\text{ }\mu\text{F}$ is provided with 200 V, 50 Hz supply. Find: i) Impedance ii) Current iii) Power iv) Power factor.		8	L3	CO2
Module – 3						
Q.5	a.	With a neat sketch, explain the principle and operation of a DC generator.		8	L2	CO3
	b.	Derive the EMF equation of DC generator.		6	L3	CO3
	c.	Calculate the emf generated by a 6 pole DC generator having 480 conductors and driven at a speed of 1200 rpm. The flux/pole is 0.012 wb. Assume the generator to be i) Lap wound ii) Wave wound.		6	L3	CO3
OR						
Q.6	a.	Define back emf and explain its significance.		6	L2	CO3
	b.	Derive expression for torque developed in a DC motor.		6	L2	CO3
	c.	Explain speed control of DC motor by i) Armature voltage control method ii) Flux control method.		8	L2	CO3
Module – 4						
Q.7	a.	Derive EMF equation of $1\phi$ transformer.		6	L3	CO4
	b.	List the various losses occurring in a transformer, explain how copper loss varies with load.		8	L2	CO4
	c.	500 KVA, $1\phi$ transformer has $R_1 = 0.4\text{ }\Omega$ , $R_2 = 0.001\text{ }\Omega$ , $V_1 = 6600\text{ V}$ , $V_2 = 400\text{ V}$ , Iron loss = 3 kW, full load copper loss = 3.858 kW. Determine: i) Efficiency at full load, 0.8 pf lagging.		6	L3	CO4
OR						
Q.8	a.	With a neat sketch, explain how rotating magnetic field is produced in a $3\phi$ induction motor.		8	L2	CO4
	b.	With a neat sketch, explain squirrel cage and wound rotor of a $3\phi$ induction motor.		6	L2	CO4

BESCK204B				
	c.	Define slip explain its significance.	6	L2 CO4
Module – 5				
Q.9	a.	With neat circuit and switching table explain the 2 way and 3 way control of lamp.	8	L2 CO5
	b.	With a neat diagram, explain the working of fuse.	6	L2 CO5
	c.	What is earthing? With a neat diagram explain the pipe earthing.	6	L2 CO5
OR				
Q.10	a.	Define tariff, explain 2 part tariff with its advantages and disadvantages.	8	L2 CO5
	b.	What is electric shock? Give the preventive measures against the shock.	6	L2 CO5
	c.	List the power rating of house hold appliances including air conditioners PC's, Laptops, printers, LED bulbs etc. Find the total load installed in a house.	6	L2 CO5

\*\*\*\*\*