

# CBCS SCHEME

BESCK104C



First Semester B.E/B.Tech. Degree Examination, Dec.2024/Jan.2025

**Introduction to Electronics and Communication**

Max. Marks:100

Note: 1. Answer any FIVE full questions, choosing ONE full question from each module.

2. M : Marks , L: Bloom's level , C: Course outcomes.

3.VTU formula Handbook is permitted.

Module – 1				
1	a.	With a neat block diagram, explain the DC power supply.	6	L2 CO1
	b.	With a circuit diagram explain the working of voltage doubler.	6	L2 CO1
	c.	With circuit diagram and waveforms, explain the working of Bi – Phase full wave rectifier.	8	L2 CO1
OR				
2	a.	Draw the circuit of Zener diode voltage regulator and explain the working.	6	L2 CO1
	b.	What is multistage amplifier? Show that the overall gain of multistage amplifier is product of individual stage gains.	6	L3 CO1
	c.	What are the advantages of negative feedback? Derive an expression for overall voltage gain of negative feedback amplifier.	8	L3 CO1
Module – 2				
3	a.	State and explain conditions for oscillations (Barkhausen criterion).	6	L1 CO2
	b.	With circuit diagram, explain the working Wein Bridge Oscillator.	6	L2 CO2
	c.	With circuit diagram and waveforms, explain the working of single stage astable multivibrator circuit using op-amp.	8	L2 CO2
OR				
4	a.	List the ideal characteristics of op-Amp.	6	L1 CO2
	b.	Explain the following parameters of the op-Amp. i) Slew Rate ii) Input offset voltage iii) CMRR.	6	L1 CO2
	c.	How op-Amp can be used as an integrator with necessary output equation and waveforms.	8	L2 CO2
Module – 3				
5	a.	i) Convert $(256.45)_{10} = (?)_2 = (?)_{16}$ ii) Find x if $(211)_x = (152)_8$ iii) Convert $(357.14)_8 = (?)_{16}$ .	8	L3 CO3
	b.	Subtract $(1010.11)_2$ from $(1001.10)_2$ using 1's and 2's complement methods.	6	L3 CO3
	c.	State and prove DeMorgan's theorems for 3 input variables.	6	L2 CO3

1 of 2

BESCK104C				
OR				
6	a.	Simplify the following Boolean expressions : i) $f_1 = \bar{x}\bar{y} + xy + \bar{x}y$ ii) $f_2 = x \oplus y \oplus z$ .	6	L4 CO3
	b.	Obtain canonical forms of the following Boolean expressions [SoP form]. i) $f = a + \bar{b}c$ ii) $f = xy + \bar{x}z$ .	6	L3 CO3
	c.	Design full adder circuit using basic gates.	8	L3 CO3
Module – 4				
7	a.	Define embedded system. Differentiate between embedded systems and general purpose computing system.	6	L1 CO4
	b.	Draw the block diagram of embedded system and explain the different elements.	6	L2 CO4
	c.	Differentiate between : i) Microprocessor Vs Microcontroller ii) RISC Vs CISC.	8	L1 CO4
OR				
8	a.	Draw the block diagram of instrumentation system and explain.	8	L2 CO4
	b.	What is seven segment display? Explain the types of seven segment display.	8	L2 CO4
	c.	What are sensors and Actuators?	4	L2 CO4
Module – 5				
9	a.	With a neat diagram, explain modern communication system.	6	L2 CO5
	b.	Define modulation and explain amplitude modulation with waveforms.	6	L2 CO5
	c.	With waveforms, explain ASK, FSK and SPK modulation techniques.	8	L2 CO5
OR				
10	a.	Explain different modes of radio wave propagation.	8	L1 CO5
	b.	What is multiplexing? Explain different types of multiplexing in communication system.	8	L2 CO5
	c.	Explain the advantages of digital communication over analog communication.	4	L1 CO5

\*\*\*\*\*

2 of 2