

USN										
-----	--	--	--	--	--	--	--	--	--	--

Internal Assessment Test 1 – Nov. 2025



Subject/Code: Digital Design and Computer Organization / BCS302				
Date: 04/11/2025	Duration: 90 mins	Max. Marks: 50	Semester: 03	Branch: AI&DS (CSDS)

Sl.	Answer any FIVE FULL Questions	Marks	CO	RBT
1	Reduce the following Boolean expressions to the minimum number of literals. i) $(x + y)(x + y')$ ii) $xy + x'z + yz$ iii) $(x + y)(x' + z)(y + z)$	5	CO1	L2
	Determine the minimum SOP form using Karnaugh Map $F = A'B'C' + B'CD + A'BCD' + AB'C'$	5	CO1	L2
2	Simplify the Boolean function $F(w, x, y, z) = \Sigma(1, 3, 7, 11, 15)$ which has the don't care conditions $d(w, x, y, z) = \Sigma(0, 2, 5)$	5	CO1	L2
	Simplify and implement the following Boolean function using NAND gates $F(x, y, z) = (1, 2, 3, 4, 5, 7)$	5	CO1	L2

3	Implement the design of combinational circuit BCD and excess-3 code converter .	5	CO2	L3
	Implement full adder circuit using 3:8 decoders .	5	CO2	L3
4	With Truth table and K-map simplification , implement the full adder with basic gates and using two half adders and an OR gate .	5	CO2	L3
	Realize the Boolean function using 8:1 multiplexer $F(A, B, C, D) = \Sigma(1, 3, 4, 11, 12, 13, 14, 15)$	5	CO2	L2
5	Simplify the given Boolean function and find the prime and essential prime implicants. $f(A, B, C, D) = \Sigma m(0, 1, 4, 5, 7, 8, 13, 15) + d(2)$	5	CO1	L2
	Place the following equation into proper canonical form: $P = f(a, b, c) = ab' + bc$ $T = f(a, b, c) = (a + b)(b' + c)$	5	CO1	L2
6	Implement the following functions using 3:8 decoder : $f_1(a, b, c) = \Sigma m(1, 3, 5)$ $f_2(a, b, c) = \Sigma m(0, 1, 6)$	5	CO2	L3
	Differentiate between latches and flipflops. Draw logic diagram and truth table for SR, D, JK and D flipflops .	5	CO2	L2

K. Allytt
CI

CC
CCI

HOD
HOD

1.(a)
(i) $(x+y)(x+y')$

$$= x + y \cdot y'$$

$$= x + 0$$

$$= x$$

(ii) $xy + x'z + yz$ (iii)

yz	00	01	11	10
x		1	1	
		0	1	1

$\Rightarrow x'z + xy$

(iii) $(x+y)(x'z)(y+z)$

yz	00	01	11	10
x	0	0		
	1	0		0

$$= (x+y)(x'z)$$

(b)

$$F = A'B'C' + BCD + A'BC'D' + ABC'$$

CD	00	01	11	10
AB				
00	1	1	1	
01				1
11				
10	1	1	1	

$$f = B'C' + B'D + A'BC'D$$

$$f = \sum (1, 3, 7, 11, 15) + d(0, 2, 5)$$

2
a

yz	00	01	11	10
wx				
00	X	1	1	X
01		X		
11			1	
10			1	


$$f = wx' + wyz$$

② ⑥

$$f(x, y, z) = \sum(1, 2, 3, 4, 5, 7)$$

		00	01	11	10
x	y				
0			1	1	1
1		1	1	1	

$$f = z + xy' + x'y$$

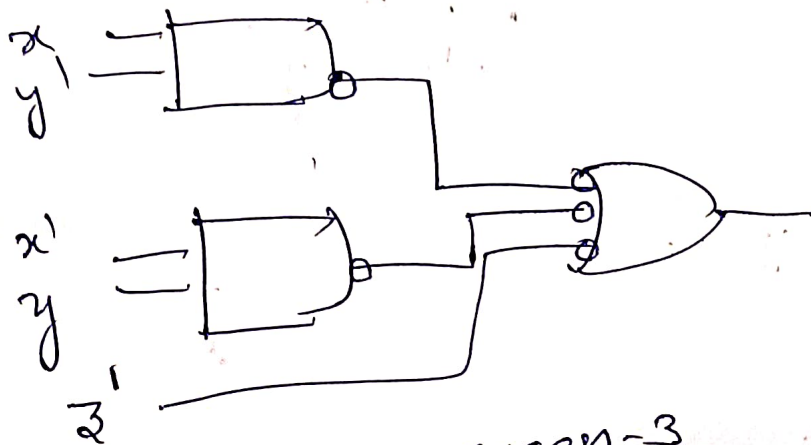

③

BCD to EXCES-3

A	BCD		
	B	C	D
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1

EXCES-3			
w	x	y	z
0	0	0	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1
1	0	1	0
1	0	1	1
1	1	0	0

②

		CD			
		00	01	11	10
W	AB				
	00				
	01			1	
	11	1	1	1	1
	10	1	1	1	1


11y

$$W = A + BC + BD$$

$$x = B'C + B'D + BC'D$$

$$y = CD + C'D$$

$$z = D$$

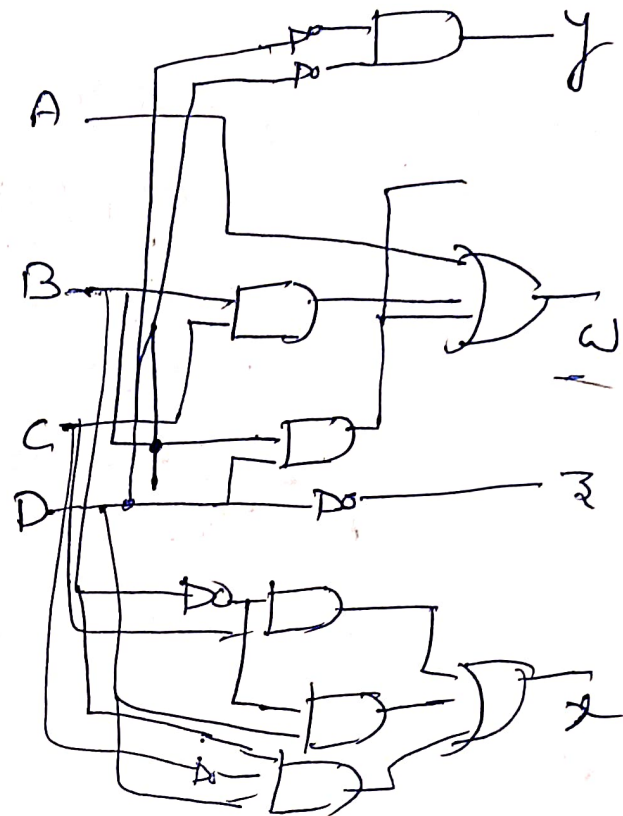


③ ⑥

Full adder

x	y	z	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$S = \Sigma(1, 2, 4, 7)$$

$$C = \Sigma(3, 5, 6, 7)$$

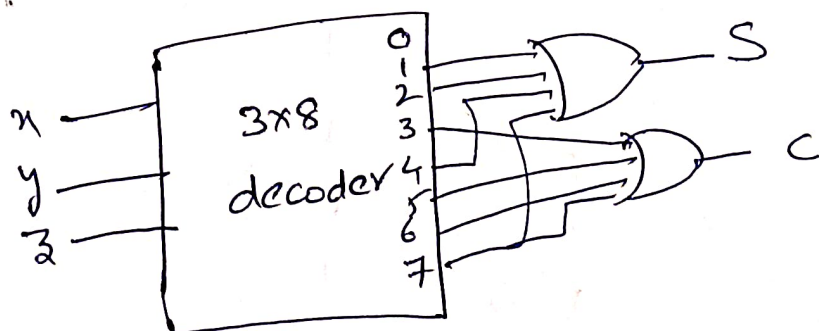

4


Full adder

$$S = x \oplus y \oplus z$$

$$C = xy + yz + xz$$


$$= xy + x'y'z + x'yz'$$

$$= xy + z(xy' + x'y)$$

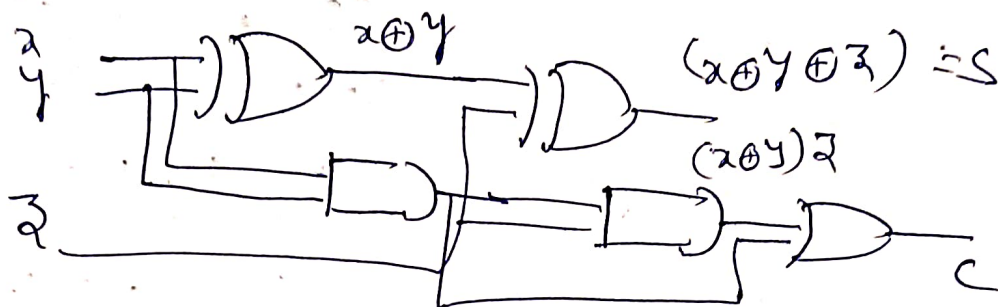

4) 6)

A	B	C	D	F
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

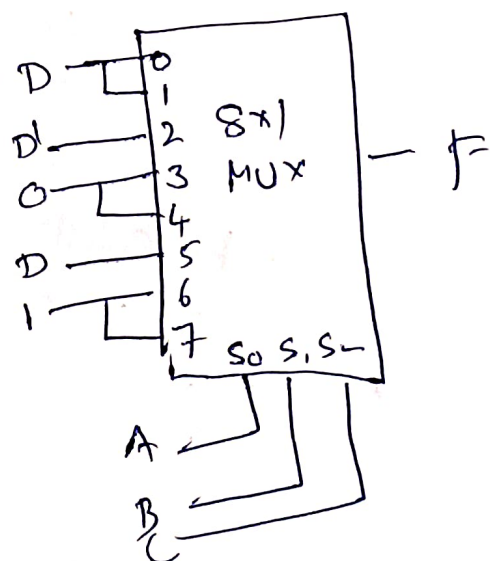

(3)

(5) (a)

	CD	00	01	11	10
AB	00	1	1		*
	01	1	1	1	
	11		1	1	
	10	1			

prime implicant

$$A'c'BD, A'c'D'$$

essential prime implicant


$$A'c', BD, B'c'D'$$

(5) (b)

$$\begin{aligned} \text{(i)} \quad P = f(a, b, c) &= ab' + bc \\ &= ab'(c+c') + (a+a')bc \\ &= ab'c + ab'c' + abc + a'bc \end{aligned}$$


$$\begin{aligned} \text{(ii)} \quad T = f(a, b, c) &= (a+b)(b'+c) \\ &= (a+b+cc')(a'+b'+c) \\ &= (a+b+c)(a+b+c')(a+b'+c) \\ &\quad (a'+b'+c) \end{aligned}$$

(6) (a)

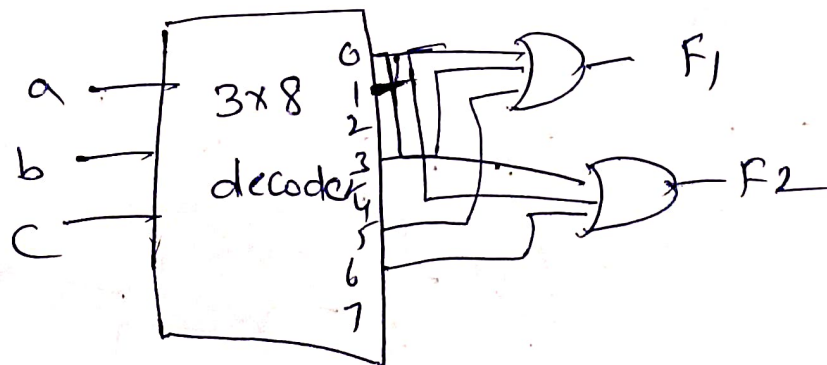


(6) (6)


S	R	$Q(t+1)$
0	0	No change
0	1	0
1	0	1
1	1	Indeterminate

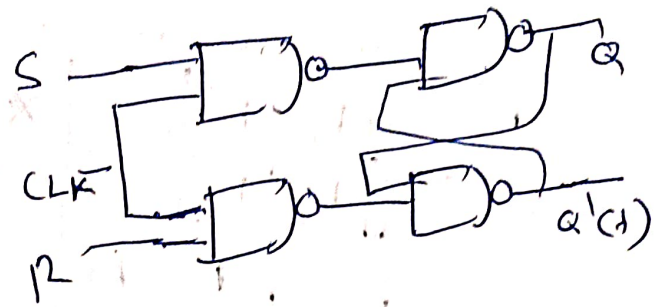

D	$Q(t+1)$
0	0
1	1

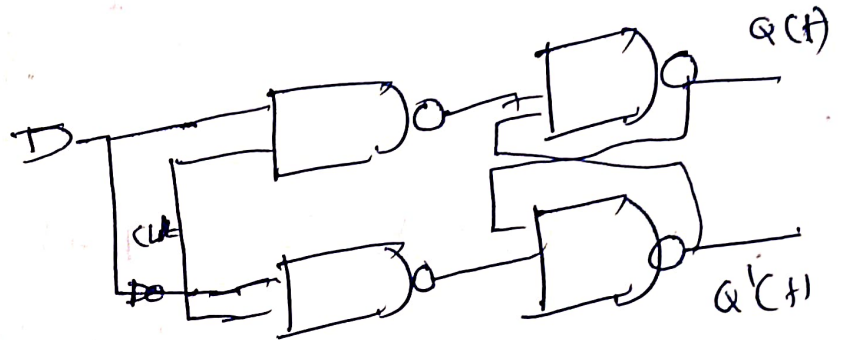

J	K	$Q(t+1)$
0	0	$Q(t)$
0	1	0
1	0	1
1	1	$Q'(t)$

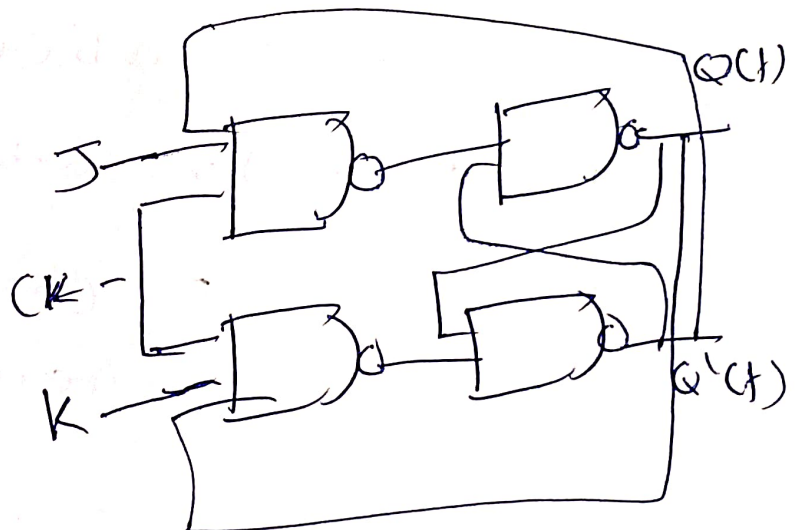

T	$Q(t+1)$
0	$Q(t)$
1	$Q'(t)$

