

USN

--	--	--	--	--	--	--	--	--	--

Internal Assessment Test 1 – NOV 2025

Sub:	Digital Design and Computer Organization					Sub Code:	BCS302	Branch:	CSE	
Date:	6/11/25	Duration:	90 mins	Max Marks:	50	Sem/Sec:	3 rd semesterA,B,C		OBE	
<u>Answer any FIVE FULL Questions</u>								MARKS	CO	RBT
1a.	Express $F(x,y,z)=xy+x'z$ as product of maxterms(pos).							[5+5]	CO1	L2,L3
b.	Express $F(x,y,z)=xy'z+x'y+x'z+yz$ as sum of products(sop).									
2 a.	Obtain the minimum POS of the function $Y = X'Z' + WYZ + W'Y'Z' + X'Y$ using K-MAP.							[7+3]	CO1	L2,L3
b.	Determine the complement of the following function(i) $F = XY' + X'Y$.(ii) $F = X'YZ' + X'YZ$.									
3	Design a BCD to Excess-3 Code converter and obtain the expression for excess -3 code using K-MAP and draw the circuit.							[10]	CO2	L2,L3
4 a.	Explain a 4-bit adder subtractor with the circuit diagram?							[5+5]	CO2	L2,L3
b.	Implement a full adder circuit with truth table, circuit diagram and expression for sum and carry.									
5.a	What is a multiplexer? Design a 4*1 mux write truth table and draw the logic circuit and give the expression for output?							[6+4]	CO2	L1,L2
b	Implement $F(A, B, C,D) = \sum (1,3,4,11,12,13,14,15)$ using a 8:1 MUX?									
6.	Explain the carry look ahead adder with expressions for carry generate and carry propagate and circuit diagram?							[10]	CO2	L2,L3


CI

CCI /Anchor Teacher

HOD



Internal Assessment Test 1 – NOV 2025

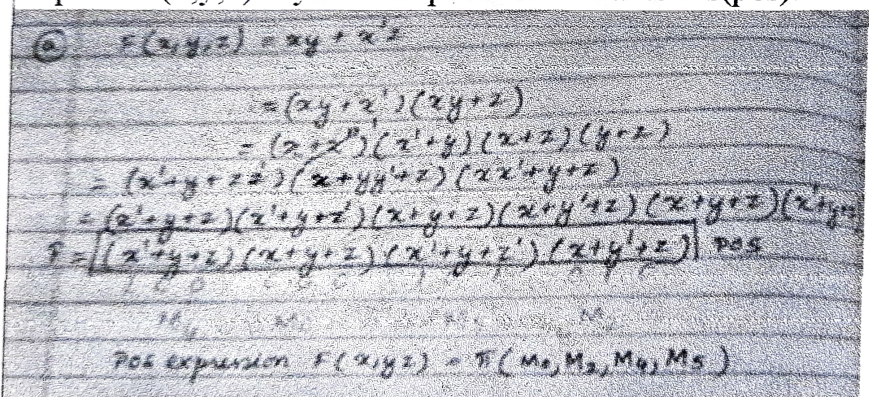Sub: Digital Design and Computer Organization		Sub Code: BCS302		Branch: CSE	
Ms. Smruthi Nair/Ms. Lini					
Date: 6/11/25	Duration: 90 mins	Max Marks: 50	Sem/Sec: 3rd semester A,B,C	OBE	
Answer any FIVE FULL Questions				MARKS	CO
1a.	Express $F(x,y,z)=xy+x'z$ as product of maxterms(pos).			[5+5]	CO1
 <p>Handwritten solution for Question 1a:</p> $F(x,y,z) = xy + x'z$ $= (xy + x'z)(x + x')$ $= (xy + x'z)(x + x')(y + y')$ $= (xy + x'z)(x + x')(y + y')(x + x')$ $= (x + y + z)(x + y + z')(x' + y + z)(x' + y + z')(x + y' + z)$ $F = \Pi(M_0, M_2, M_4, M_5)$ <p>Pos expression $F(x,y,z) = \Pi(M_0, M_2, M_4, M_5)$</p>					L2L3
	Express $F(x,y,z)=xy'z+x'y+x'z+yz$ as sum of products(sop).				

$$F(x,y,z) = xy'z + x'y + x'z + yz$$

$$= xy'z + x'y(z+z') + x'(y+y')z + (x+x')yz$$

$$= xy'z + x'yz + x'y'z + x'yz + x'y'z + x'yz + x'yz + x'yz$$


$$= x'y'z + x'yz + x'y'z + x'yz$$

- 2 a. Obtain the minimum POS of the function $Y = X'Z' + WYZ + W'Y'Z' + X'Y$ using K-MAP.

[7+3]

CO1

L2,L3

 

- b. Determine the complement of the following function (i) $F = XY' + X'Y$. (ii) $F = X'YZ' + X'Y'Z$.
- (I) $F = (X' + Y)(X + Y')$
- (II) $(X + Y' + Z)(X + Y + Z')$

3. Design a BCD to Excess-3 Code converter and obtain the expression for excess -3 code using K-MAP and draw the circuit.

[10]

CO2

L2,L3

A code converter is a circuit that makes the two systems compatible

even though each uses a different binary code.

• Since each code uses four bits to represent a decimal digit, there must be four input variables and

four output variables. We designate the four input binary variables by the symbols A, B, C, and D,




and the four output variables by w, x, y, and z.

• ADD 3 to BCD to get Excess -3 Code

Truth Table for Code Conversion Example

Input BCD				Output Excess 3 Code			
A	B	C	D	w	x	y	z
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	1
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	1

   Note that four binary variables may have 16 bit combinations, but only 10 are listed in the truth table. The six bit combinations not listed for the input variables are don't-care combinations.



implemented with three or more levels of gates:


$$z = D'$$

$$y = CD + C'D' = CD + (C + D)'$$

$$x = B'C + B'D + BC'D' = B'(C + D) + BC'D'$$

$$= B'(C + D) + B(C + D)'$$

$$w = A + BC + BD = A + B(C + D)$$

 

4 a. Explain a 4-bit adder subtractor with the circuit diagram?

[5+5]

CO2

L2,L3

The addition and subtraction operations can be combined into one circuit with one common binary adder by including an exclusive-OR gate with each full-adder.

The mode input M controls the operation as the following:

If $M=0 \rightarrow$ the circuit is an adder


$M=1 \rightarrow$ the circuit becomes a subtractor

Each exclusive-OR gate receives input M and one of the inputs of B.

value of B, the input carry is $C_0 = 0$ and the circuit performs $A + B$

- When $M = 1$, we have $B \text{ XOR } 1 = \bar{B}$ and $C_0 = 1$. The B inputs are all complemented and a 1 is added through the input carry. The circuit performs the operation $A + (\text{the 2's complement of } B) = A - B$

• The exclusive-OR with output V is for detecting an overflow. The binary adder-subtractor circuit with outputs C and V is shown in Fig. If the two binary numbers are considered to be unsigned, then the C bit detects a carry after addition or a borrow after subtraction. If the numbers are considered to be signed, then the V bit detects an overflow. If $V = 0$ after an addition or subtraction, then no overflow occurred and the n-bit result is correct. If $V = 1$, then the result of the operation contains n + 1 bits, but only the rightmost n bits of the number fit in the space available, so an overflow has occurred. The $(n + 1)$ th bit is the actual sign and has been shifted out of position

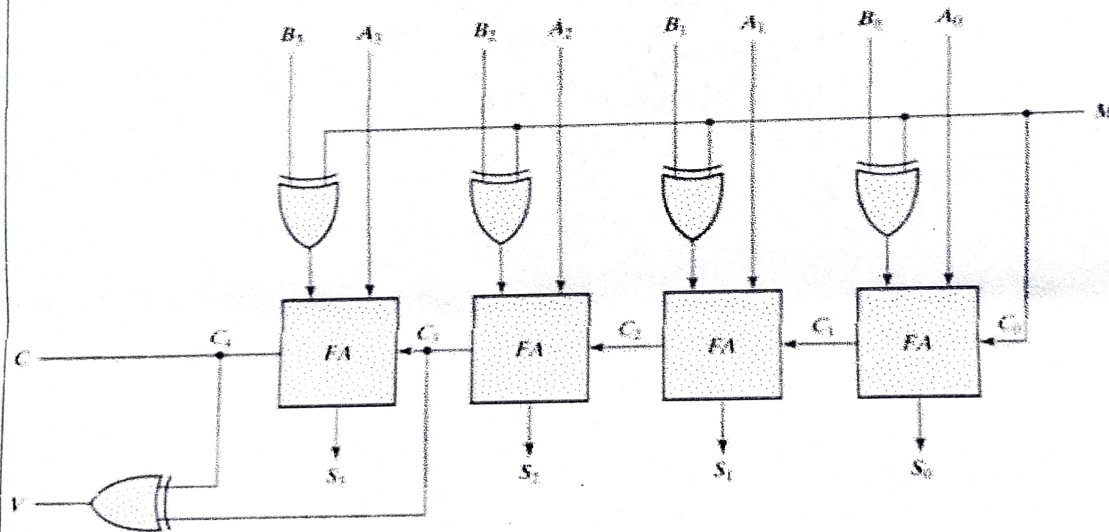

- b. Implement a full adder circuit with truth table, circuit diagram and expression for sum and carry.

Logic Diagram




Truth Table

C _i	A	B	Sum (S)	Carry (C _o)
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Circuit Diagram

USING BASIC AND XOR GATES

 

5.a What is a multiplexer? Design a 4*1 mux write truth table and draw the logic circuit and give the expression for output?

[6+4]


CO2

L1,L2

Multiplexer is a data selector, a circuit with many inputs

but only one output.

 Designing of 4 to 1 multiplexer shown below:



Truth table for 4 to 1 MUX:

A	B	Y
0	0	D ₀
0	1	D ₁
1	0	D ₂
1	1	D ₃

Working principle of 4 to 1 multiplexer:


From the above diagram, the Logic Equation for 4 to 1 multiplexer is

$$Y = A'B'D_0 + A'BD_1 + AB'D_2 + ABD_3$$

$$\text{If } A=0, B=0 \text{ then, } Y = 0'0'D_0 + 0'0D_1 + 00'D_3 + 00D_3 = 1.1.D_0 + 1.0.D_1 + 0.1.D_2 + 0.0.D_3 = D_0$$

Similarly, if A=0 and B=1 then Y=D₁, if A=1 and B=0 then Y=D₂ and

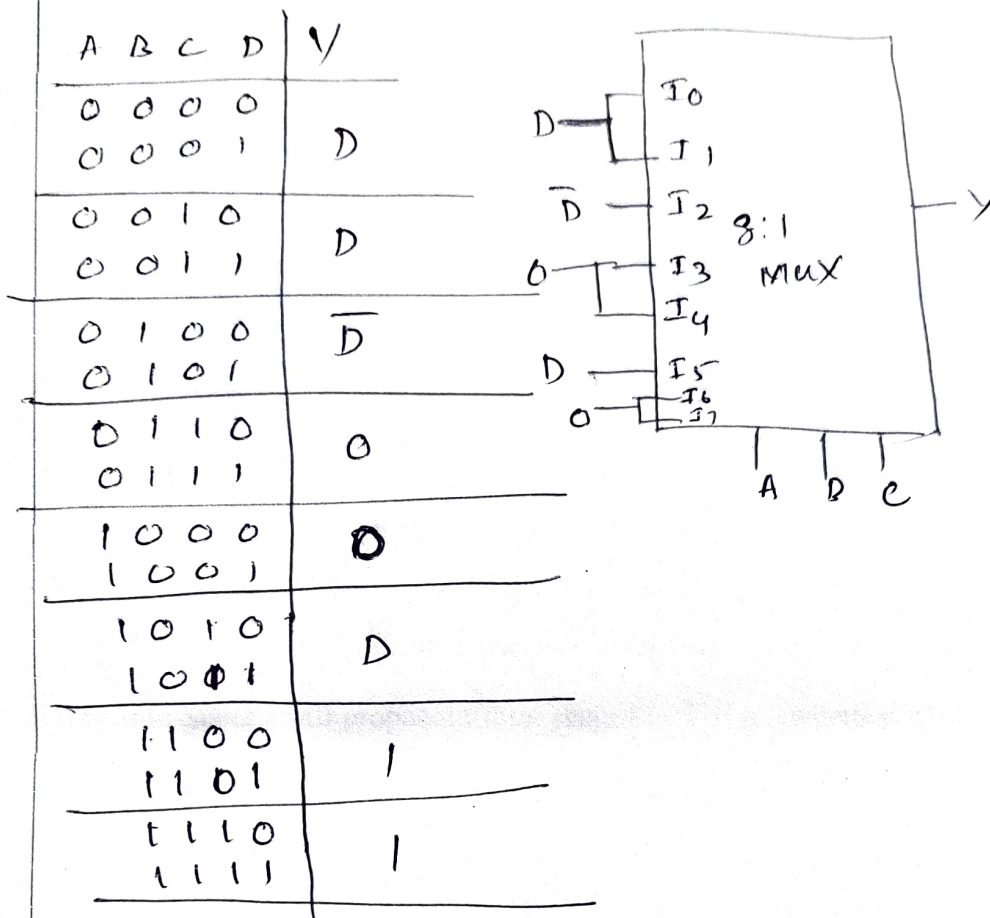Implement $F(A, B, C, D) = \sum (1, 3, 4, 11, 12, 13, 14, 15)$ using a 8:1 MUX?



6. Explain the carry look ahead adder with expressions for carry generate and carry propagate and circuit diagram?

[10]

Input carry C_0 does not settle to its final value until C_3 is available from the previous

stage.

Similarly, C_2

has to wait for C_1

and so on down to C_0


. Thus, only after the carry propagates and ripples through all stages will the last output S_3

and carry C_4

settle to their final correct value.

The problem faced by a 4 bit ripple adder is the delay There are several techniques for reducing the carry propagation time in a parallel adder.

CO2 L2,L3

 

Consider the circuit of the full adder s in If we define two new binary variables

$$P_i = A_i \oplus B_i \quad G_i = A_i B_i$$

❖ The output sum and carry can respectively be expressed as

$$S_i = P_i \oplus C_i \quad C_{i+1} = G_i + P_i C_i$$

G_i is called a carry generate, and it produces a carry of 1

when both A_i and B_i are 1, regardless of the input

carry C_i .

G_i indicates that the data into stage i generates a carry into stage $i + 1$.

P_i is called a carry propagate, because it determines whether a carry into stage i will propagate into stage $i + 1$ (i.e., whether an assertion of C_i will propagate to an assertion of C_{i+1}).

We now write the Boolean functions for the carry outputs substitute the value of each C_i from the previous equations:

$$C_0 = \text{input carry} \quad C_1 =$$

$$G_0 + P_0 C_0$$

$$C_2 = G_1 + P_1 C_1$$

$$= G_1 + P_1 (G_0 + P_0 C_0)$$


$$= G_1 + P_1 G_0 + P_1 P_0 C_0$$

$$C_3 = G_2 + P_2 C_2$$

$$= G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$$

Since the carry of the different stages depends on only C_0 we are able to execute the addition in a much faster way.

Circuit of carry look ahead adder:

 

CI

CCI/Anchor Teacher

HOD