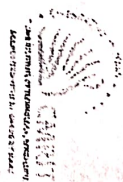


--	--	--	--	--	--	--	--	--	--




Internal Assessment Test - I

Sub:	Electronic Principles and Circuits						Code:	BEC303	
Date:	5/11/2025	Duration:	90 mins	Max Marks:	50	Sem:	3rd	Branch:	ECE

Answer Any FIVE FULL Questions


		Marks	OBE	
			CO	RBT
1.	(a) Discuss Emitter feedback bias biasing circuits. (b) Define AC Beta and AC Emitter resistance.	[7+3]	CO1	L1
	Determine the collector-emitter voltage, collector current, and collector voltage in the given figure. 2. Also, draw the load line and find the Q-point.	[10]	CO1	L3
3.	Explain Common collector amplifier with the help of circuit diagram and derive voltage gain.	[10]	CO1	L2
4.	Draw T model and π model of (i) base biased amplifier (ii) Voltage divider bias amplifier	[5+5]	CO1	L2

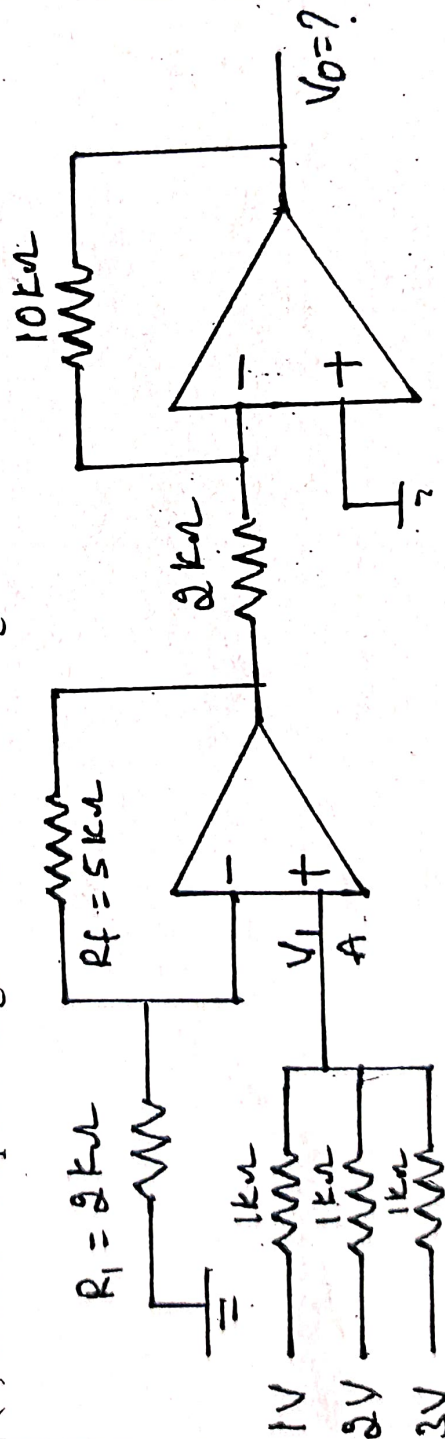5.	Explain the operation of inverting Schmitt Trigger circuit with necessary diagrams.	[10]	CO2	L2
6.	(a) Explain the operation of Hartley Oscillator. (b) Find the output voltage V_o in the following OPAMP circuit. 	[6+4]	CO2	L3
7.	(a) Explain the operation of Wein Bridge oscillator with necessary equations. (b) Explain Barkhausen Criteria for sustained oscillations.	[7+3]	CO2	L3


 CCI





 CCI

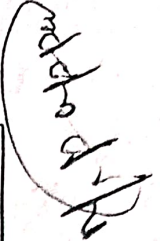
 HOD

USN

--	--	--	--	--	--	--	--	--	--

Internal Assessment Test - I

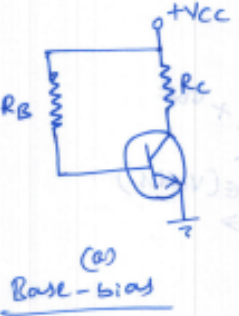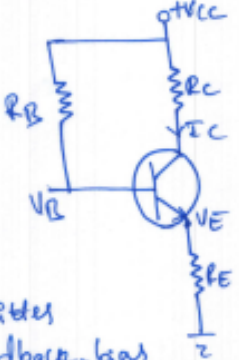Sub:	Electronic Principles and Circuits						Code:	BEC303	
Date:	5/11/2025	Duration:	90 mins	Max Marks:	50	Sem:	3rd	Branch:	ECE
Answer Any FIVE FULL Questions									
								OBE	
								CO	RBT
1.	(a) Discuss Emitter feedback bias biasing circuits. <u>Emitter - Feedback bias.</u> (i) Base-bias circuit 1-  Base-bias → Since the base current is fixed, the collector current varies when the current gain varies. → ∴ Q point moves all over the load line with transistor replacement and temperature change. → not commonly used configuration. * The first attempt at stabilizing the Q-point was emitter-feedback bias (ii)  Emitter feedback-bias * An Emitter resistor has been added to the circuit. * The basic idea is: if I_C increases, V_E increases, causing V_B to increase. * More V_B means less voltage across R_B. This results in less I_B, which opposes the original increase in I_C.						[5+5]	CO1	L1

- * It is called feedback because the change in emitter voltage is being fed back to the base circuit.
- * Also, the feedback is called negative because it opposes the original change in collector current.
- * Equations for analyzing the emitter-feedback bias.

$$I_E = \frac{V_{CC} - V_{BE}}{R_E + R_B/\beta} \rightarrow (1)$$

$$V_E = I_E R_E \rightarrow (2)$$

$$V_B = V_E + 0.7V \rightarrow (3)$$

$$V_C = V_{CC} - I_C R_C \rightarrow (4)$$

if $R_E \gg R_B/\beta$

$$\therefore I_E = \frac{V_{CC} - V_{BE}}{R_E} \rightarrow (5)$$

(b) Define AC Beta and AC Emitter resistance.

AC Beta - The ac current gain is ratio of ac collector current to the ac base current.

$$\beta_{ac} = \frac{i_c}{i_b}$$

$i_c \rightarrow$ Pule ac collector current

$i_b \rightarrow$ Pule ac base current.

AC Resistance of Emitter diode (r_e')

→ The Variable resistance or dynamic resistance of the emitter-base junction diode of a transistor is called the AC emitter resistance.

→ It is defined as the change in the base-emitter voltage divided by the change in the corresponding emitter current.

$$r_e' = \frac{V_{be}}{I_E}$$

→ Total emitter current: $I_E = I_{EQ} + i_e$.

→ Total base-emitter voltage: $V_{BE} = V_{BEQ} + v_{be}$.

$$r_e' = \frac{25mV}{I_E}$$


→ AC resistance decreases as DC emitter current increases.

$$r_e' = \frac{V_T}{I_E}$$

$$V_T = \frac{kT}{q}$$

Determine the collector-emitter voltage, collector current, and collector voltage in the given figure.

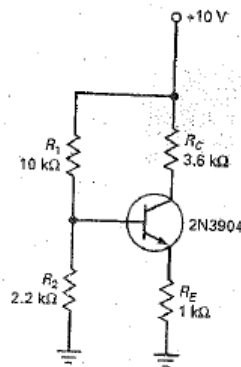
2. Also, draw the load line and find the Q-point.



[10]

CO1

L3

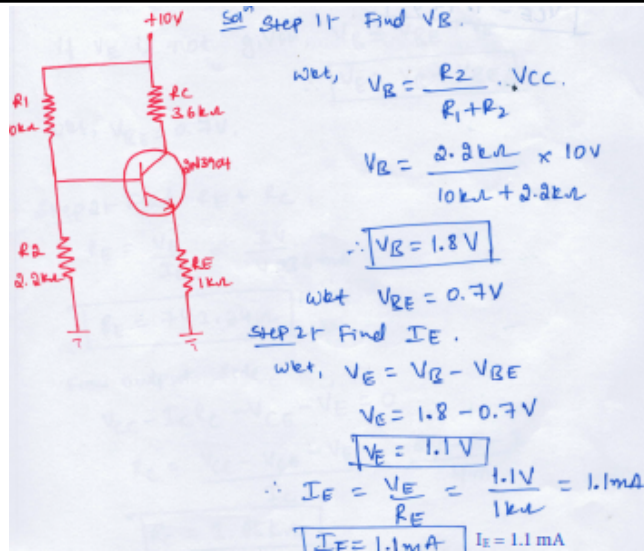

→ Since the collector current almost equals the emitter current, we can calculate the collector to ground voltage

$V_C = V - I_C R_C$ $I_C \approx I_E = 1.1mA$


$$V_C = 10 - (1.1mA)(3.6k\Omega)$$

$$V_C = 6.04V$$

The collector-emitter voltage is:

$$V_{CE} = V_C - V_E$$

$$= 6.04 - 1.1V$$
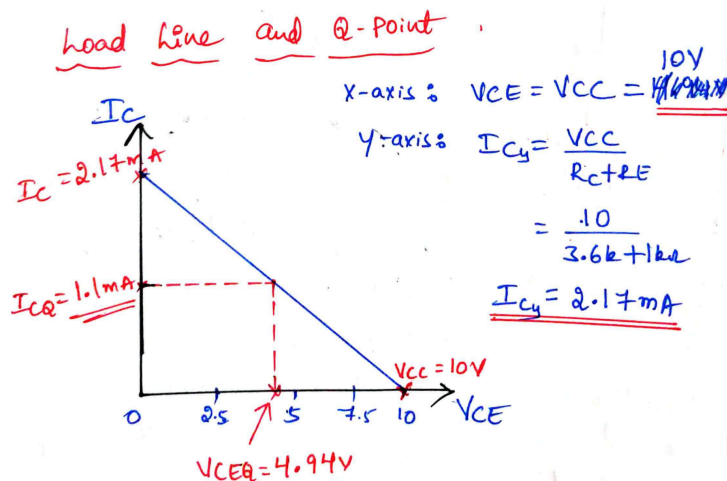
$$V_{CE} = 4.94V$$


3. Explain Common collector amplifier with the help of circuit diagram and derive voltage gain.

[10]

CO1

L2

CC Amplifier:-

Emitter follower is the circuit in which the output voltage signal at the emitter is approximately equal to the voltage signal input on the base. It is also called common-collector (CC) amplifier.


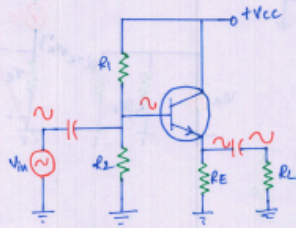


Fig: Emitter follower and waveforms.

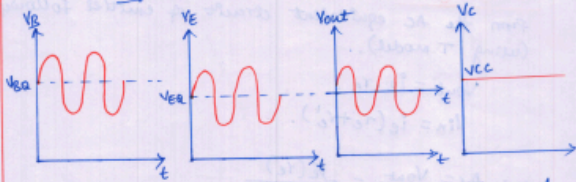

1. The output and input voltage are approximately equal and they are in phase with each other.
2. The circuit is called an emitter follower since the output voltage follows the input voltage.
3. Since there is no collector resistor, the total voltage between the collector and the ground equals the supply voltage.
4. The emitter follower uses negative feedback.
5. The voltage gain is unstable and has maximum value of 1.
6. The distortion is almost non-existent.


AC Emitter Resistance

$r_e \rightarrow$ ac emitter resistance.


$$r_e = R_E \parallel R_L$$

AC equivalent circuit:-

T model:-

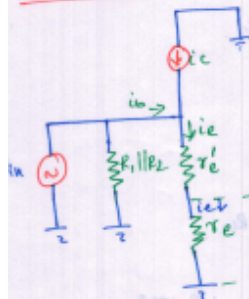

π model:-

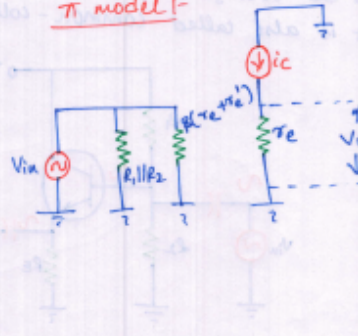

Voltage gain:-

From the AC equivalent circuit of emitter follower (using T model).

$$V_{out} = i_e \cdot r_e$$

$$V_{in} = i_e (r_e + r_e')$$

$$\therefore A_v = \frac{V_{out}}{V_{in}} = \frac{r_e (r_e)}{i_e (r_e' + r_e)}$$

$$A_v = \frac{r_e}{r_e' + r_e}$$

$$\text{Usually } r_e \gg r_e' \therefore A_v = \frac{r_e}{r_e} = 1$$

$$A_v \approx 1$$

- Since gain ≈ 1 , the output will be same as input.
- Hence it is known as Emitter follower amplifier.

input impedance of Base.

$$Z_{in(base)} = \beta(r_e + r_e')$$

$$Z_{in} \approx \beta r_e \quad \because r_e \gg r_e'$$

input impedance of Stage.

$$Z_{in(stage)} = R_1 \parallel R_2 \parallel \beta(r_e + r_e')$$

Advantage:-

- Even though, the output voltage is same as input voltage, the emitter follower can produce large o/p current.
- Emitter follower is not a voltage amplifier but a current & power amplifier.

Output impedance

$$Z_{out} = R_E \parallel \left(r_e' + \frac{R_G \parallel R_1 \parallel R_2}{\beta} \right)$$

$$\textcircled{ii} \quad Z_{out} = \frac{R_E}{\beta} \rightarrow \text{Approximate Formula.}$$

4.


Draw T model and π model of (i) base biased amplifier (ii) Voltage divider bias amplifier

[5+5]


CO1

L2

Base-Biased Amplifier.

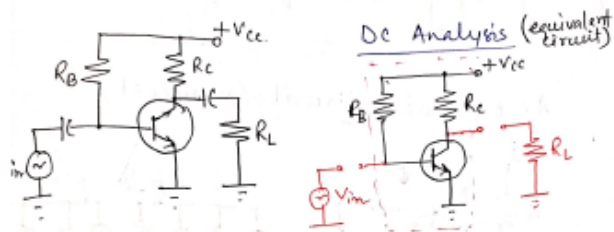


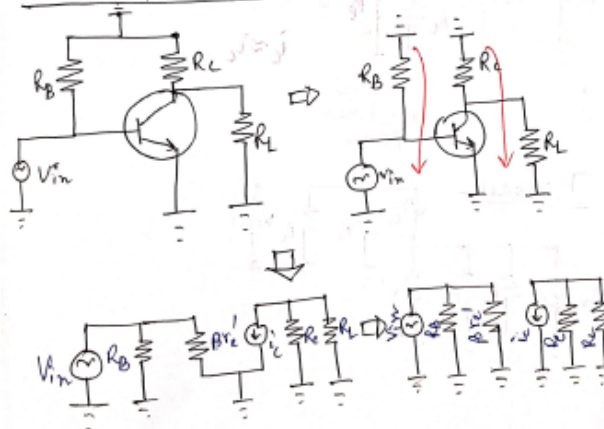AC Analysis (equivalent circuit) (π model)




VDB Amplifier:


DC Equivalent

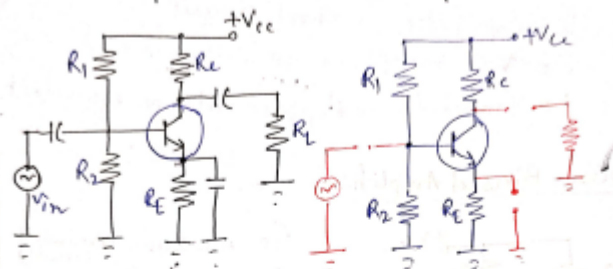

AC Equivalent Circuit: (π model)

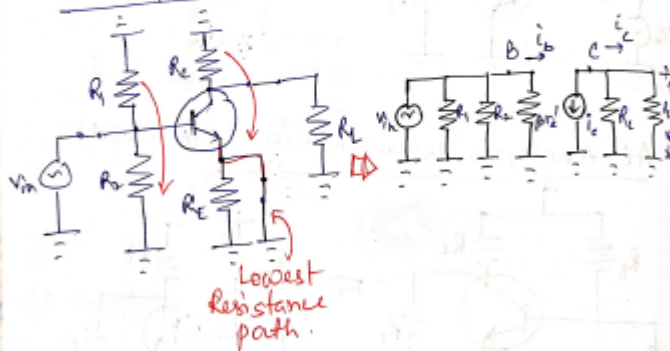

T model

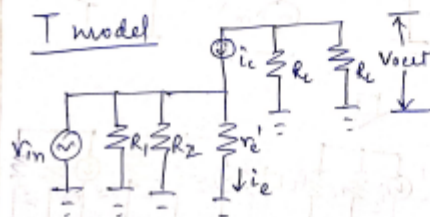

P.T.O



5. Explain the operation of inverting Schmitt Trigger circuit with necessary diagrams.

[10]

CO2

L1

Schmitt Trigger

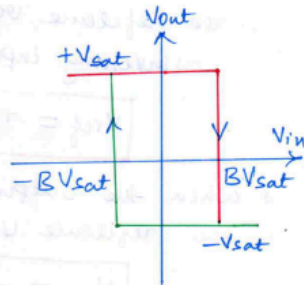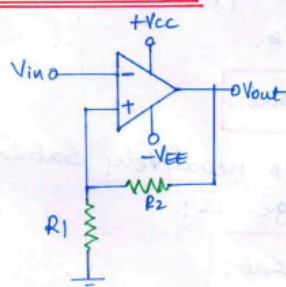

(a) Inverting Schmitt trigger.

(b) Input/output response has hysteresis.

- * The input voltage is applied to the inverting input. Because the feedback voltage is aiding the input voltage, the feedback is positive. A comparator using positive feedback is called a **Schmitt trigger**.
- * When the comparator is positively saturated, a positive voltage is fed back to the non-inverting input. This +ve voltage holds output in high state.

* Similarly, when the output voltage is negatively saturated, a negative voltage is fed back to the non-inverting input, holding the output in low state. In either case, the positive feedback reinforces the existing output state.

* The feedback fraction is,

$$B = \frac{R_1}{R_1 + R_2}$$

* When the output is positively saturated, the reference voltage applied to the non-inverting input is.

$$V_{ref} = +BV_{sat}$$

* When the output is negatively saturated, the reference voltage is:

$$V_{ref} = -BV_{sat}$$

* The output voltage will remain in a given state until the input voltage exceeds the reference voltage for that state.

* To switch states input voltage should be increased more than V_{ref} .

6.


(a) Explain the operation of Hartley Oscillator.

[10]

CO2

L3

Hartley Oscillator

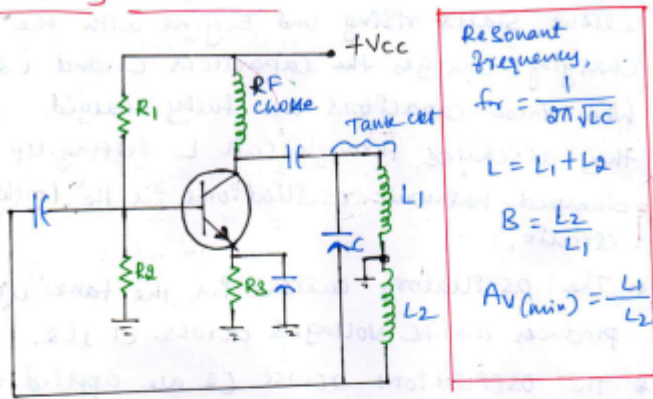

- * When the LC tank is resonant, the circulating current flows through L_1 in series with L_2 . The equivalent L is: $L = L_1 + L_2$.
- * In a Hartley oscillator, the feedback voltage is developed by the inductive voltage divider, L_1 and L_2 .
- * Since the output voltage appears across L_1 and the feedback voltage appears across L_2 , the feedback fraction is,

$$B = \frac{L_2}{L_1}$$

$$A_{vmin} = \frac{L_1}{L_2}$$


- * For oscillations to start, the voltage gain must be greater than $\frac{1}{B}$.

- * Transistor offers 180° phase shift and LC tank circuit offers another 180° phase shift. Totally 360° of phase shift fulfilled one of the essential conditions for the oscillation.

Working:-

- * When the DC supply (V_{cc}) turned on, the collector current starts rising and begins with the charging of the capacitor C . Once capacitor C is fully charged, it starts discharging through L_1 and L_2 .
- * The output of the amplifier is applied across the inductor L_1 while the feedback voltage drawn across L_2 is applied to the base of the transistor.

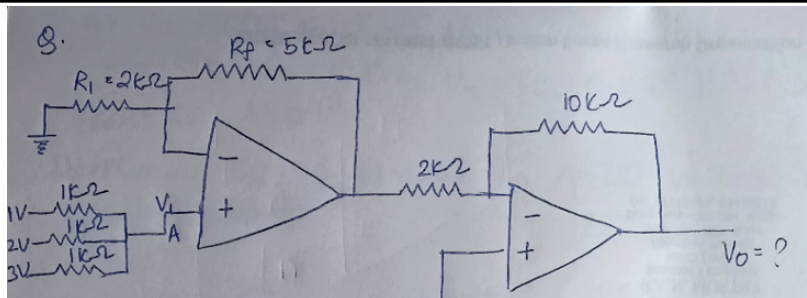(b) Find the output voltage V_o in the following OPAMP circuit.



$$V_{01} = \left(1 + \frac{R_f}{R_1}\right) \left(\frac{V_1 + V_2 + V_3}{3}\right)$$

$$V_{01} = \left(1 + \frac{5k}{2k}\right) \left(\frac{1+2+3}{3}\right)$$

$$V_{01} = (3.5)(2) = 7V \rightarrow \text{o/p of 1st stage.}$$

o/p of 2nd stage $V_0 = ?$

$$V_0 = -\frac{R_f}{R} \times V_{01}$$

$$= -\frac{10k}{2k} \times 7V$$

$$\therefore V_0 = -35V.$$


7. (a) Explain the operation of the Wein Bridge oscillator with necessary equations.

[5+5]

CO2

L3

The Wien - Bridge Oscillator.

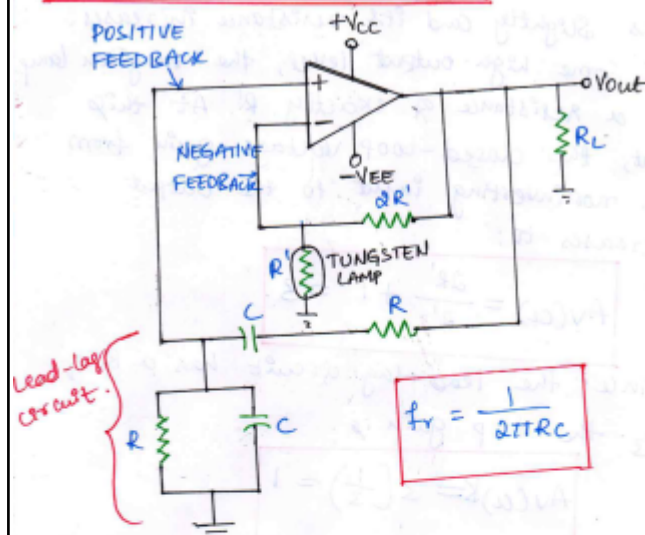

$$f_r = \frac{1}{2\pi RC}$$

- Ranges 5Hz to 1MHz.
- Used in commercial audio generators and is usually preferred for other lower frequency applications.
- Wien bridge oscillator uses a resonant feedback circuit called lead-lag circuit.

- * It uses positive and negative feedbacks.
- * When the circuit is initially turned on, there is more +ve feedback than -ve feedback. This allows the oscillations to build up.
- * After the output signal reaches a desired level, the -ve feedback becomes large enough to reduce loop gain $A_v B$ to 1.

- * As the oscillations build up, the tungsten lamp heats slightly and its resistance increases.
- * At some high output level, the tungsten lamp has a resistance of exactly R' . At this point, the closed-loop voltage gain from the noninverting input to the output decreases to:

$$A_v(\omega) = \frac{2R'}{R'} + 1 = 3$$

Since the lead-lag circuit has a B of $\frac{1}{3}$, the loop gain is:

$$A_v(\omega)B = 3\left(\frac{1}{3}\right) = 1$$

- * When the resistance of tungsten lamp equals R' , the loop gain $A_v(\omega)B$ is exactly equal to 1.
- * At this point, the oscillations become stable, and the output voltage has a constant peak-to-peak value.

(b) Explain Barkhausen Criteria for sustained oscillations.

Barkhausen Criteria

1. Initially, loop gain $A_v B$ is greater than 1 at the frequency where the loop phase shift is 0° .
2. After the desired output level is reached, $A_v B$ must decrease to 1 by reducing either A_v or B .

CI

CCI

HOD