



Third Semester B.E. Degree Examination, June/July 2025

## Network Theory

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

## Module-1

- 1 a. For the network shown in Fig.Q.1(a), convert using source transformation/shifting technique to find current 'I'.

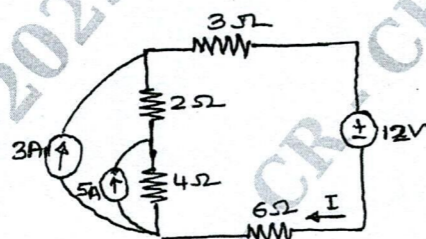


Fig.Q.1(a)

(06 Marks)

- b. Using Star-Delta transformation, find equivalent resistance of network shown in Fig.Q.1(b) between terminal AB.

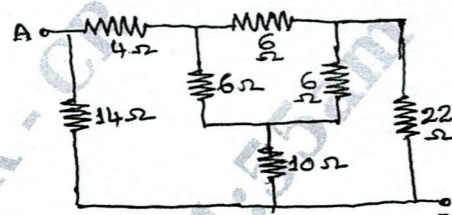


Fig.Q.1(b)

(07 Marks)

- c. For the network shown in Fig.Q.1(c), using super mesh concept to determine current I.

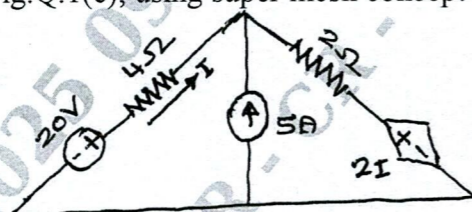


Fig.Q.1(c)

(07 Marks)

OR

- 2 a. Find the voltages of three non-reference nodes of the network shown in Fig.Q.2(a).

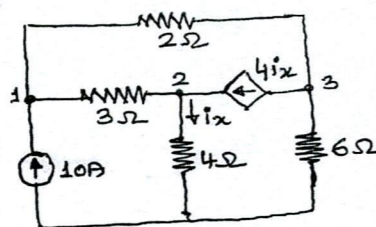


Fig.Q.2(a)

(06 Marks)

1 of 5

- b. Using mesh analysis determine all the loop current for the network shown in Fig.Q.2(b).

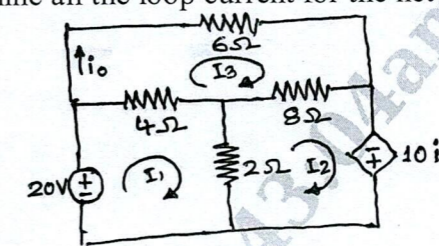


Fig.Q.2(b)

(07 Marks)

- c. Using supernode concept, determine all non reference node voltages for the network shown in Fig.Q.2(c).

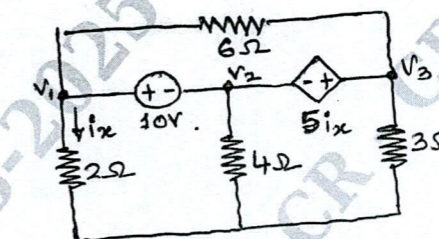


Fig.Q.2(c)

(07 Marks)

## Module-2

- 3 a. State and prove "Super position theorem".  
b. Refer to the circuit shown in Fig.Q.3(b). Use Millman's theorem to find current through  $(5 + j5)\Omega$ .

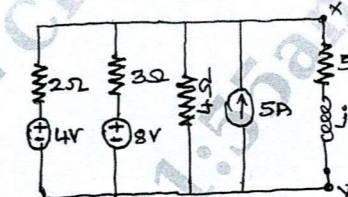


Fig.Q.3(b)

(07 Marks)

- c. Find the Thevenin's equivalent network for circuit shown in Fig.Q.3(c).

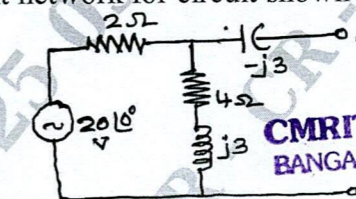


Fig.Q.3(c)

(07 Marks)

OR

- 4 a. Find the Norton's equivalent between terminals PQ of network shown in Fig.Q.4(a).

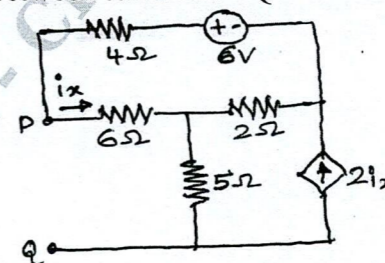


Fig.Q.4(a)

(07 Marks)

2 of 5

- b. Refer to the circuit shown in Fig.Q.4(b). Find " $\gamma_x$ " using superposition theorem.

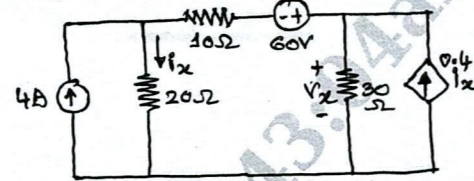


Fig.Q.4(b)

(06 Marks)

- c. Find the value of load " $Z_L$ " for which maximum power is delivered to the load of network shown in Fig.Q.3(c). (07 Marks)

**Module-3**

- 5 a. Explain the behavior of R, L and C elements for transients, mention their representation at the instant of switching. (06 Marks)
- b. In the circuit shown in Fig.Q.5(b), the switch is closed at  $t = 0$ ; find  $i_1, i_2, \frac{di_1}{dt}$  and  $\frac{di_2}{dt}$  at  $t = 0^+$

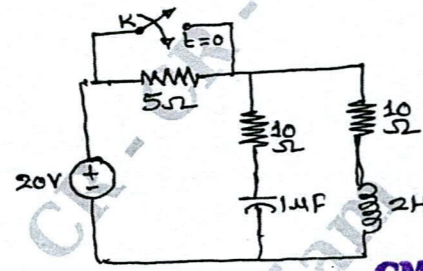


Fig.Q.5(b)

CMRIT LIBRARY  
BANGALORE - 560 037

(07 Marks)

- c. For the network shown in Fig.Q.5(c). The switch K is closed at  $t = 0$ . Steady state having been reached before switching. Calculate  $i, di/dt$  and  $d^2i/dt^2$  at  $t = 0^+$

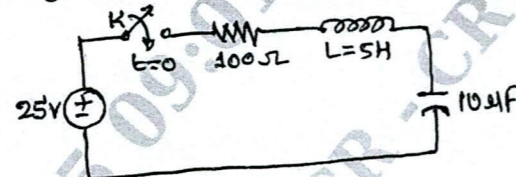


Fig.Q.5(c)

(07 Marks)

**OR**

- 6 a. Explain the significance of study of initial condition theory, list the procedures for evaluating initial conditions. (06 Marks)
- b. In the circuit shown in Fig.Q.6(b), a steady state is reached with switch 'K' open. AT  $t = 0$  the switch is closed. For elements given values, determine value of  $\gamma_a(0^-)$  and  $\gamma_a(0^+)$ .

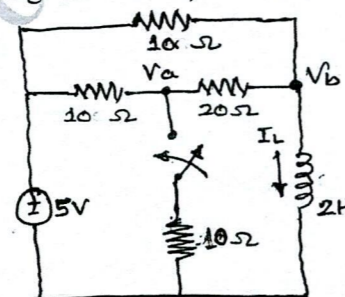


Fig.Q.6(b)

(07 Marks)

3 of 5

- c. How is time constant of RL circuit defined? Explain its importance in transient analysis, with suitable examples. (07 Marks)

**Module-4**

- 7 a. What are three important singularity functions? Write brief note on each with necessary mathematical expression with sketches. (06 Marks)
- b. List the various properties of Laplace transforms and prove the below properties: (07 Marks)
- i) Linearity ii) Time shifting
- c. Consider the RC circuit shown in Fig.Q.7(c). The input is the rectangular pulse shown in Fig.Q.7(c), find  $i(t)$  by assuming circuit is initially relaxed.

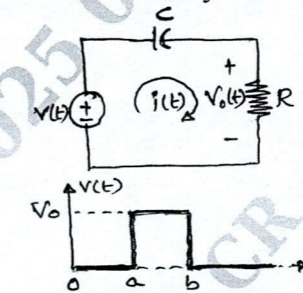


Fig.Q.7(c)

(07 Marks)

**OR**

- 8 a. Find the Laplace transform of periodic signal  $x(t)$  shown in Fig.Q.8(a). (10 Marks)

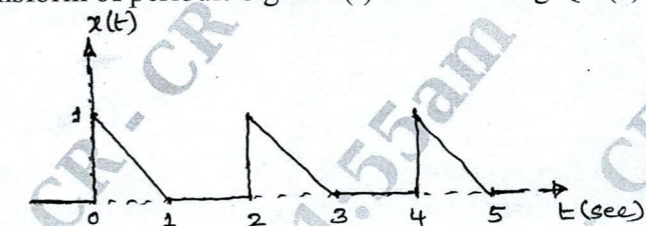


Fig.Q.8(a)

- b. Refer the circuit shown in Fig.Q.8(b). Find  $i(0)$  and  $i(\infty)$  using initial and final value theorem. (10 Marks)

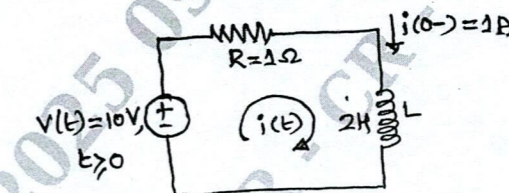


Fig.Q.8(b)

CMRIT LIBRARY  
BANGALORE - 560 037**Module-5**

- 9 a. Refer the network shown in Fig.Q.9(a), find open circuit parameter for the network and take  $\gamma_s = 10V$ .

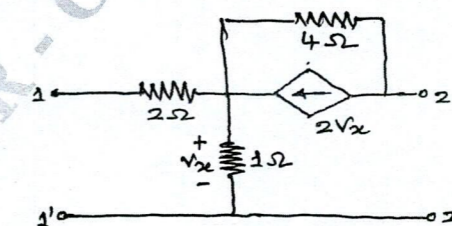


Fig.Q.9(a)

(10 Marks)

4 of 5

- b. Refer to the network shown in Fig.Q.9(b). Find h-parameters. Find also calculate short circuit parameter using h-parameter results. (10 Marks)

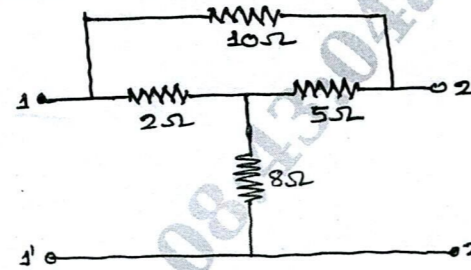


Fig.Q.9(b)

OR

CMRIT LIBRARY  
BANGALORE - 560 037

- 10 a. Derive for series resonant circuit, the resonant frequency  $f_0 = \sqrt{f_1 f_2}$ , where  $f_1$  and  $f_2$  are half power frequencies. (06 Marks)
- b. A parallel resonant circuit has fixed capacitor and variable inductor having constant quality factor of 4. Find the value of inductor and capacitance for circuit impedance of  $1000\Omega$  at resonating frequency of 2.4 MHz. What is the bandwidth of circuit? (07 Marks)
- c. Sketch the variation of current and impedance with frequency of series resonant circuit and give brief note on same. (07 Marks)

\*\*\*\*\*