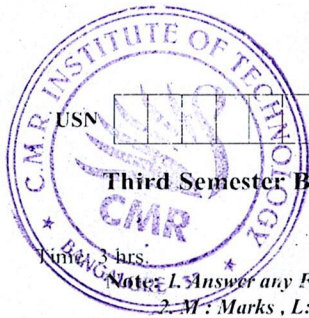




CBCS SCHEME

BEC304

Third Semester B.E/B.Tech. Degree Examination, June/July 2025




Networks Analysis

Time: 3 hrs.

Max. Marks: 100

1. Answer any FIVE full questions, choosing ONE full question from each module.





2. M: Marks, L: Bloom's level, C: Course outcomes.

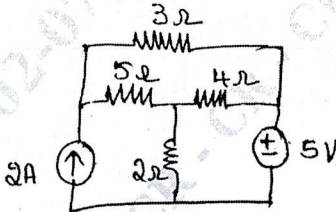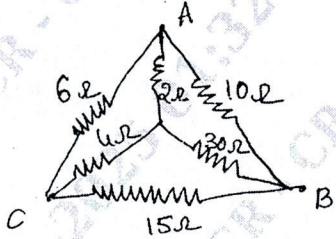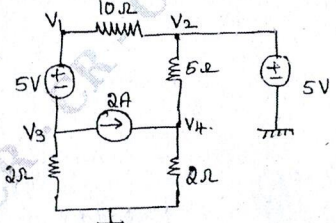Module - 1			M	L	C
1	a.	Using source transformation and source shifting techniques, find voltage across 2Ω resistor as shown in Fig.Q1(a).	7	L3	CO1
 Fig.Q1(a)					
	b.	For the circuit shown in Fig.Q1(b), determine the equivalent resistance between A and B.	6	L3	CO1
 Fig.Q1(b)					
	c.	For the network shown in Fig.Q1(c), compute all node voltages V_1, V_2, V_3 and V_4 using node analysis.	7	L3	CO1
 Fig.Q1(c)					

1 of 4

BEC304

OR

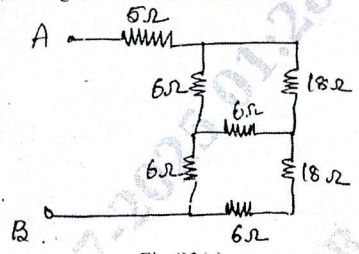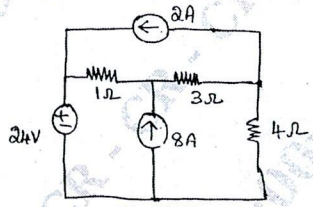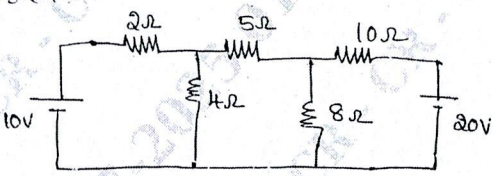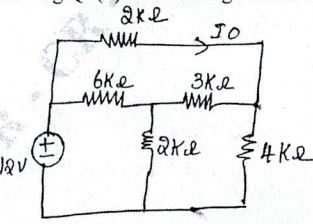2	a.	Determine the equivalent resistance between terminal A and B, in the network shown in Fig.Q2(a). Using star to Delta transformation.	7	L3	CO1
 Fig.Q2(a)					
	b.	In the circuit shown in Fig.Q2(b), use the loop analysis to find the power delivered to the 4Ω resistor.	7	L3	CO1
 Fig.Q2(b)					
	c.	Using node voltage analysis, find the current in the each branch for the circuit shown in Fig.Q2(c).	6	L3	CO1
 Fig.Q2(c)					
Module - 2					
3	a.	State the explain Thevenin's theorem.	8	L2	CO2
	b.	Find I_0 in the network of Fig.Q3(b) below using Norton's theorem.	12	L3	CO2
 Fig.Q3(b)					

2 of 4

OR

4	a.	State and explain maximum power transfer when load impedance consisting of variable resistance and variable reactance.	8	L2	CO2
	b.	Using Millman's theorem, find the current flowing through $R_L = 10\Omega$ of the circuit as shown in Fig.Q4(b).	12	L3	CO2

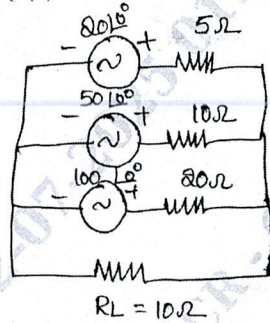


Fig.Q4(b)

Module – 3

5	a.	Explain the initial and final conditions in basic elements.	6	L2	CO3
	b.	Obtain the expression for transient response $i(t)$ of series R – C circuit when excited by DC supply.	6	L2	CO3
	c.	In the networks Fig.Q5(c), the switch K is opened at $t = 0$. At $t = 0^+$, solve for V , $\frac{dV}{dt}$ and $\frac{d^2V}{dt^2}$.	8	L3	CO3

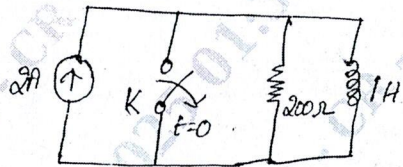


Fig.Q5(c)

OR

6	a.	Obtain the expression for transient response, $i(t)$ of series RL circuit when excited by AC supply.	6	L2	CO3
	b.	For the circuit shown in Fig.Q6(b), $V_C(0) = 0$. Find $i(0^+)$, $\frac{di}{dt}(0^+)$ and $\frac{d^2i}{dt^2}(0^+)$.	8	L3	CO3

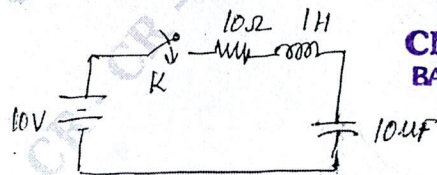


Fig.Q6(b)

CMRIT LIBRARY
BANGALORE - 560 037

Module – 4

7	a.	State and prove initial and final value theorem.	10	L3	CO3
	b.	Find the Laplace transform of the periodic signal $x(t)$ as shown in Fig.Q7(b).	10	L3	CO3

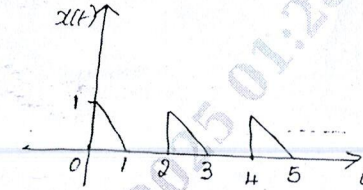


Fig.Q7(b)

OR

8	a.	Find the Laplace transform of $f(t)$ shown in Fig.Q8(a).	10	L3	CO3
	b.	A voltage pulse of 10V and 2 sec duration is applied to the RC network shown in Fig.Q8(b). Find the current $i(t)$.	10	L3	CO3

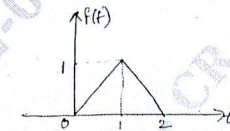


Fig.Q8(a)

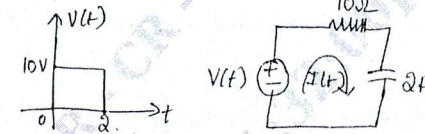


Fig.Q8(b)

Module – 5

9	a.	Derive Y-parameters interms of Z-parameters.	4	L2	CO4
	b.	Determine h-parameters of the circuit shown in Fig.Q9(b).	8	L3	CO4

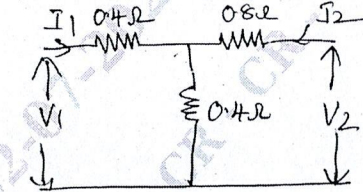


Fig.Q9(b)

CMRIT LIBRARY
BANGALORE - 560 037

	c.	Prove the following expression in series resonance. $f_r = \sqrt{f_1 f_2}$.	8	L2	CO4
--	----	--	---	----	-----

OR

10	a.	Obtain an expression for resonance frequency in a parallel resonant circuit.	4	L2	CO4
	b.	Define ABCD parameters and obtain ABCD parameters interms of h-parameters.	8	L3	CO4
	c.	A series RLC circuit has $R = 50\Omega$, $L = 0.2H$ and $C = 10\mu F$ with an applied voltage of 20V. Determine : i) F_0 ii) Q_0 iii) BW.	8	L3	CO4
