



Second Semester B.E/B.Tech. Degree Examination, June/July 2025

Introduction to Electrical Engineering

Max. Marks:100

Note: 1. Answer any FIVE full questions, choosing ONE full question from each module.

2. M : Marks , L: Bloom's level , C: Course outcomes.

3. VTU Formula Hand Book is permitted.

Module – 1				M	L	C
1	a.	State and explain Kirchoff's laws.		6	L1	CO2
	b.	A resistance R is connected in series with a parallel circuit comprising of two resistance $12\ \Omega$ and $8\ \Omega$. The total power in the circuit is 70 W, when the applied voltage of 20 V. Calculate R.		7	L3	CO2
	c.	With block diagram, explain the nuclear power generations.		7	L1	CO1
OR						
2	a.	With neat diagram, explain the general structure of electrical power systems using single line diagram.		8	L1	CO1
	b.	State and explain ohm's law and mention its limitations.		6	L1	CO2
	c.	If the total power dissipated in the circuit shown below in Fig. Q2 (c) is 18 W. Determine (i) Value of R and its current (ii) Power consumed by $8\ \Omega$ resistor.		6	L3	CO2
Fig. Q2 (c)						
Module – 2						
3	a.	Show that, the power consumed by a pure capacitor is zero, when connected across A.C. supply.		7	L1	CO1
	b.	A resistance of $20\ \Omega$ is connected in series with a pure inductance of 0.05 H and the circuit is connected to a 230 V, 50 Hz, sinusoidal supply. Calculate (i) Circuit current (ii) Phase angle (iii) Power factor (iv) Power		8	L3	CO2
	c.	Write a short note on advantages of 3 phase system.		5	L1	CO1
OR						
4	a.	A balanced three phase load of $(8+j6)\ \Omega$ per phase is connected to a three phase 230 V supply. Find the line current, power factor, reactive power and total power in the circuit when the load is connected in star.		7	L3	CO1

	b.	With the help of circuit diagram and phasor diagram, analyze the R-C series circuit and show that current leads the voltage.	7	L1	CO1
	c.	Define RMS value, Average value, Form factor.	6	L1	CO2
Module – 3					
5	a.	With usual notation, derive the EMF equation of a DC generator.	6	L2	CO3
	b.	With a neat sketch, explain the construction of various parts of DC generator.	8	L1	CO3
	c.	Derive an expression for the torque developed by a DC motor.	6	L2	CO3
OR					
6	a.	A 4 pole, 500 V shunt motor has 720 wave connected conductors on its armature. The full load armature current is 60 A and the flux per pole is 0.03 Wb. The armature resistance is 0.2 Ω and the contact drop is 1 V per brush. Calculate the full load speed.	7	L3	CO3
	b.	Explain the working principle of DC motor with suitable diagrams.	8	L1	CO3
	c.	Explain characteristics of DC shunt motor.	5	L1	CO3
Module – 4					
7	a.	Explain the working principle of single phase transformer.	6	L2	CO3
	b.	A 10 pole induction motor supplied by a 6 pole alternator which is driven at 1200 rpm. If the motor runs at a slip of 3%, what is its speed and frequency of rotor induced emf.	6	L2	CO3
	c.	Explain the concept of rotating magnetic field in case of stator field of 3-phase induction machine with a neat diagram.	8	L3	CO3
OR					
8	a.	Derive an EMF equation of transformer with usual notations.	7	L2	CO4
	b.	A 10 KVA, 400/200 V, single phase transformer has a maximum efficiency of 98% at 90% of the full load at 0.8 p.f. Find its efficiency at full load and 0.6 p.f.	7	L2	CO4
	c.	Define slip. Derive the expression for frequency of rotor current.	6	L2	CO4
Module – 5					
9	a.	What is Domestic wiring and explain casing and capping?	7	L1	CO5
	b.	What is earthing? With a neat diagram, explain pipe earthing.	7	L1	CO5
	c.	Explain the working principle of Fuse and MCB.	6	L1	CO5
OR					
10	a.	Define Tariff. Explain briefly the two part tariff with its advantages and disadvantages.	7	L1	CO5
	b.	What is electric shock? Give the list of preventive measures against the shock.	7	L1	CO5
	c.	With neat circuit diagram, and switching table, explain two-way and three-way control of lamps.	6	L1	CO5
