

Third Semester B.E./B.Tech. Degree Examination, Dec.2025/Jan.2026 Network Theory

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Derive the expression for Delta to Star transformation and Star to Delta transformation. (10 Marks)
- b. For the network shown in Fig.Q1(b) find the node voltages V_c and V_d .

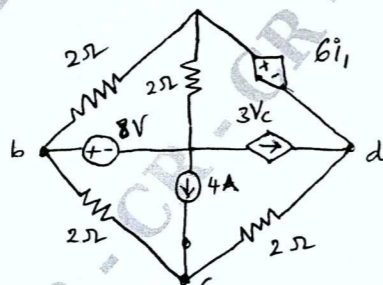


Fig.Q1(b)

(10 Marks)

OR

- 2 a. Explain the classification of electrical networks by providing an example. (08 Marks)
- b. Reduce the network shown in Fig.Q2(b) to a single voltage source in series with a resistance using source shifting and source transformations.

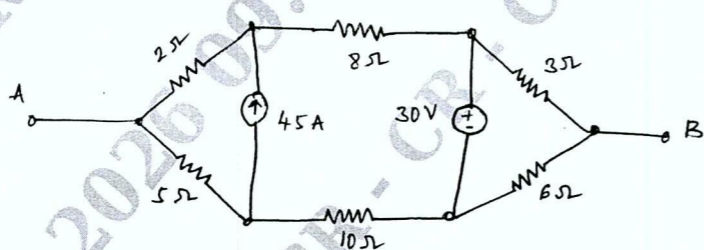


Fig.Q2(b)

(07 Marks)

- c. Find the equivalent resistance at terminals AB in Fig.Q2(c).

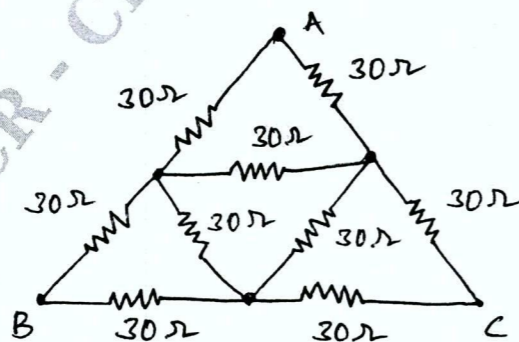


Fig.Q2(c)

(05 Marks)

1 of 5

Module-2

- 3 a. State and prove Thevenin's Theorem. (08 Marks)
- b. In the circuit shown in Fig.Q3(b), find the value of the current through 667Ω resistor using Norton's theorem.

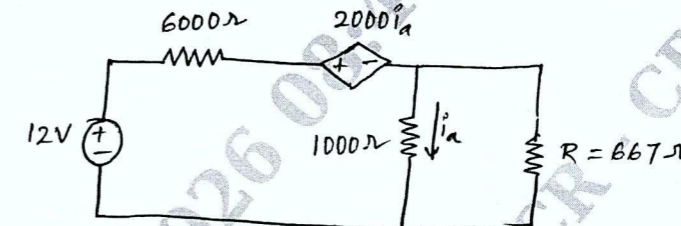


Fig.Q3(b)

(06 Marks)

- c. For the circuit shown in Fig.Q3(c), find the current i using super position theorem.

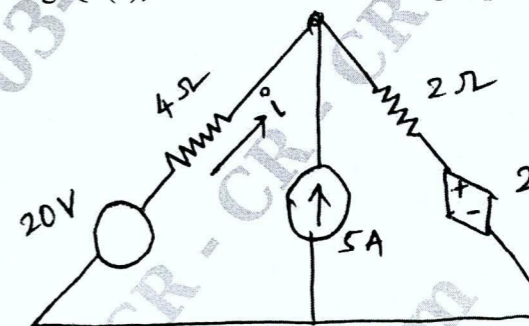


Fig.Q3(c)

(06 Marks)

OR

- 4 a. State and prove maximum power transfer theorem. (08 Marks)
- b. Find the current flowing through $(2 + j3)\Omega$ impedance using Millman's theorem for the circuit shown in Fig.Q4(b).

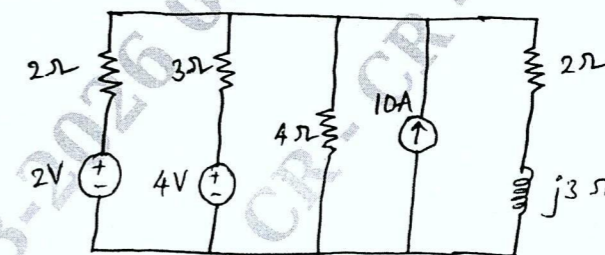


Fig.Q4(b)

(06 Marks)

- c. For the network shown in Fig.Q4(c), obtain Thevenin's equivalent as seen from terminals A and B.

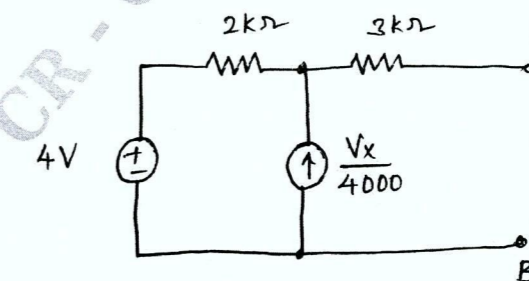


Fig.Q4(c)

(06 Marks)

2 of 5

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

CMRIT LIBRARY
BANGALORE - 560 837

Module-3

- 5 a. For the given network shown in Fig.Q5(a), K is closed at $t = 0$ with zero current in the inductor. Find the values of i , $\frac{di}{dt}$, $\frac{d^2i}{dt^2}$ at $t = 0^+$ if $R = 8\Omega$ and $L = 0.2H$.

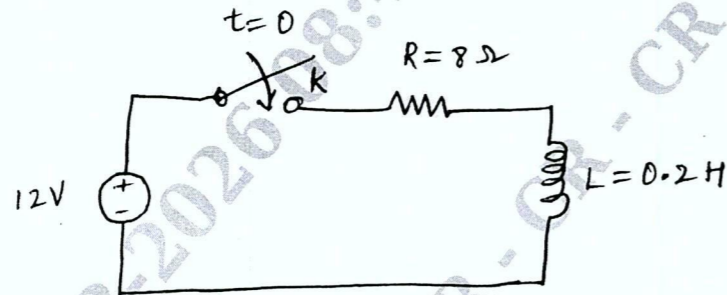


Fig.Q5(a)

(08 Marks)

- b. For the Fig.Q5(b). The switch K is opened at $t = 0$. At $t = 0^+$, solve for the values of V , $\frac{dv}{dt}$ and $\frac{d^2V}{dt^2}$ if $I = 2A$, $R = 200\Omega$ and $L = 1 H$.

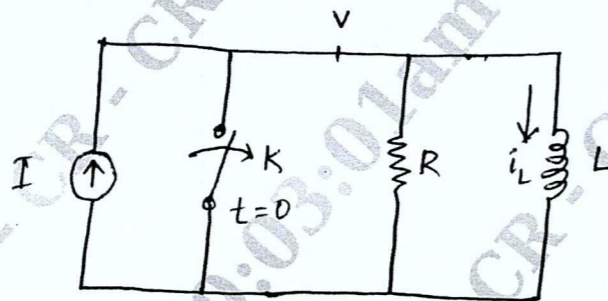


Fig.Q5(b)

(08 Marks)

- c. In how many seconds after $t = 0$ has the current $i(t)$ become one half of its initial value in the given circuit shown in Fig.Q5(c).

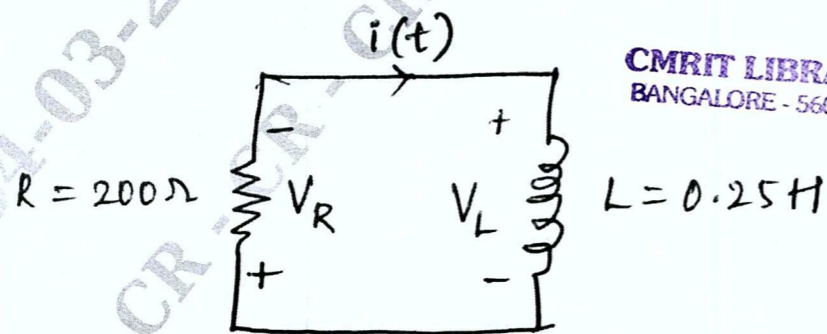


Fig.Q5(c)

(04 Marks)

OR

- 6 a. In the circuit shown in Fig.Q6(a), determine the complete solution for current, when switch K is closed at $t = 0$. Applied voltage $V(t) = 100 \cos(10^3t + \pi/2)$.

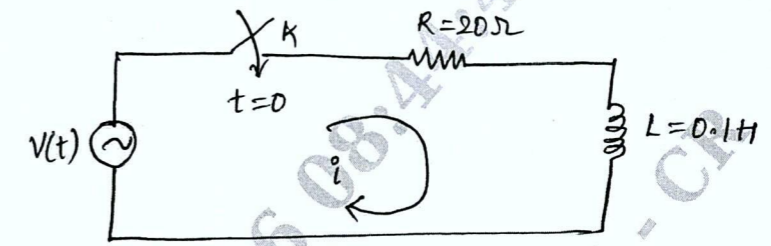


Fig.Q6(a)

(10 Marks)

- b. In the Fig.Q6(b), switch K is closed at $t = 0$. Find value of $i_1, i_2, \frac{di_1}{dt}, \frac{di_2}{dt}, \frac{d^2i_1}{dt^2}, \frac{d^2i_2}{dt^2}$ at $t = 0^+$.

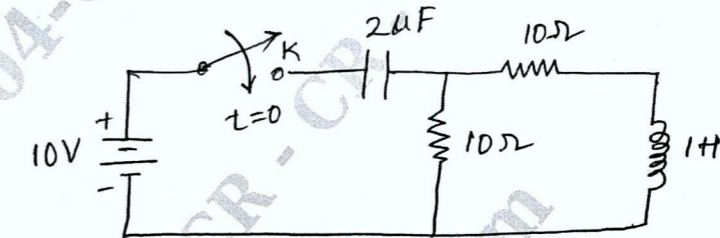


Fig.Q6(b)

(10 Marks)

Module-4

- 7 a. State and prove initial and final value theorem.
b. Obtain the Laplace transform of sawtooth waveform shown in Fig.Q7(b).

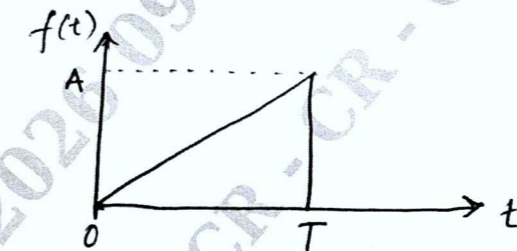


Fig.Q7(b)

(06 Marks)

- c. Obtain the Laplace transform of squarewave train shown in Fig.Q7(c).

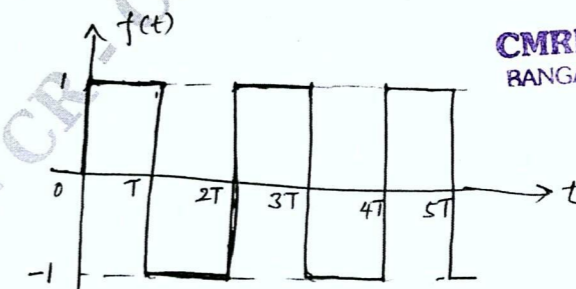


Fig.Q7(c)

(06 Marks)

OR

- 8 a. Obtain the Laplace transform of step, ramp and impulse functions. (06 Marks)
 b. Find the Laplace transform of the periodic signal shown in Fig.Q8(b).

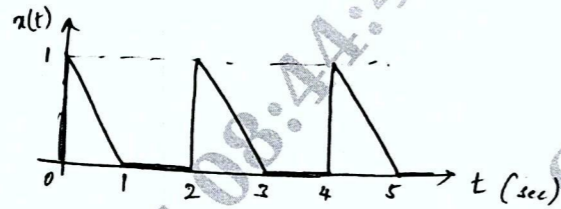


Fig.Q8(b)

(06 Marks)

- c. Obtain the Laplace transform of $f(t)$ of the waveform shown in Fig.Q8(c).

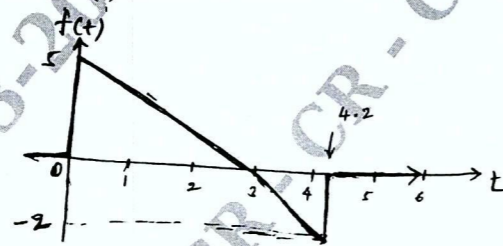


Fig.Q8(c)

(08 Marks)

Module-5

- 9 a. Derive Z-parameters in terms of h-parameters and ABCD - parameters. (10 Marks)
 b. The bridged T-RC network is as shown in Fig.Q9(b). For the values given, find y and z parameters.

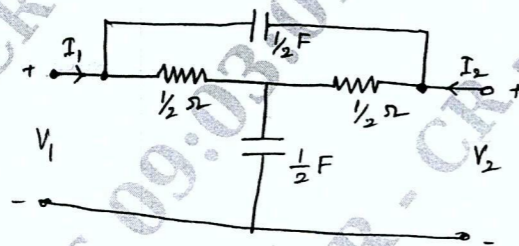


Fig.Q9(b)

(10 Marks)

OR

- 10 a. Prove that $f_0 = \sqrt{f_1 f_2}$ where f_1 and f_2 are the two half power frequencies of a resonant circuit. (08 Marks)
 b. Find the value of R such that the given circuit in Fig.Q10(b) is resonant.

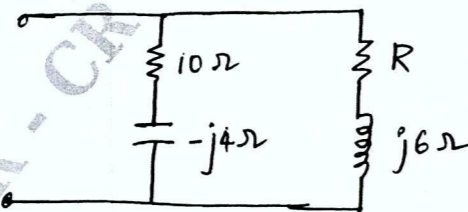


Fig.Q10(b)

(04 Marks)

- c. A series RLC circuit has $R = 4\Omega$, $L = 1 \text{ mH}$ and $C = 10 \mu\text{F}$. Calculate Q-factor, bandwidth, resonant frequency and half power frequencies f_1 and f_2 . (08 Marks)
