

USN	I	C	R						
-----	---	---	---	--	--	--	--	--	--

Internal Assessment Test - II

Sub	Basic Electronics					Code:	18ELN14
Date:	05/12/2018	Duration:	90 mins	Max Marks:	50	Sem:	I
						SEC:	I,J,K,L,M,N,O

Answer Any FIVE FULL Questions


	Marks	OBE		
		CO	RBT	
1 For an op-amp (i) List the characteristics of an ideal op-amp and (ii) Draw the three input inverting summer circuit and derive an expression for its output voltage.	[10]	CO1	L3	
2 Explain the operation of Full wave bridge rectifier with neat and clean diagram. Also derive the I_{DC} , I_{RMS} , P_{AC} , P_{DC} and Efficiency for this rectifier.	[10]	CO2	L2	
3(a) Design an adder circuit using an op-amp to obtain an output voltage of $V_o = -[2V_1 + 3V_2 + 5V_3]$ Given $R_f = 10k\Omega$	[05]	CO1	L3	
(b) With a neat diagram, explain how an op-amp can be used as a differentiator.	[05]	CO1	L2	
4(a) Write a short note on the following: (i) Photo diode (ii) Light emitting diode	[05]	CO1	L1	
(b) A non-inverting amplifier circuit has an input resistance of $10k\Omega$ and feedback resistance $60k\Omega$, with load resistance of $47k\Omega$. Draw the circuit. Calculate the output voltage, voltage gain, load current when the input voltage is 1.5V.	[05]	CO1	L3	



6 (a) Design a Zener Voltage Regulator to meet the following specification Output voltage = 5V, Load current = 10 mA, Zener Wattage = 100 mW, input voltage = $10V \pm 2V$, $I_z \text{ min} = 5\text{mA}$.

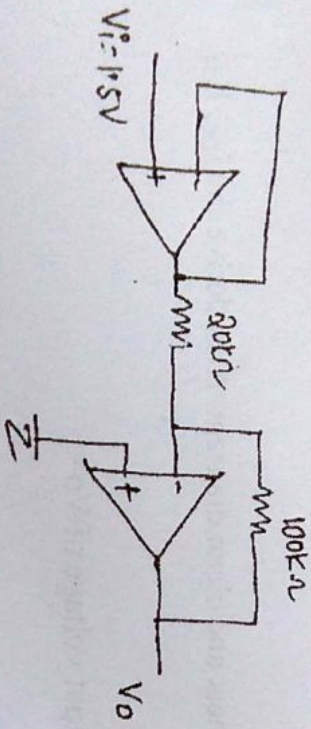(b) Explain Full wave rectifier with capacitor filter in detail with necessary waveforms

7 (a) Find the output V_o of following op-amp circuit



[05]	C0	L3
[05]	C0	L2
[05]	C0	L3

(b) What is Zener diode? With neat circuit diagram, explain load and Line regulation using Zener diode.

8(a) Draw and Explain the working of an inverting op-amp. Derive the expression for its voltage gain.

(b) The input to the basic differentiator circuit is a sinusoidal voltage of peak value of 10mV and frequency 1.5KHz. Find the output if, $R_f = 100K\Omega$ and $C_1 = 1\mu F$.

[05]	C	L2
[05]	C	L3
[05]	C	L3

5 Mark

Ans-1 (i) opamp ideal characteristics :-

① CMRR (Common Mode Rejection Ratio)
Ideally $CMRR = \infty$

② A_{OL} (Open Loop Gain) → Ideally $A_{OL} = \infty$

③ Input Impedance (Ideally ∞)

④ Output Impedance (Ideally 0)


⑤ PSRR (Power supply Rejection Ratio) Ideally = 0

⑥ Bandwidth (Ideally infinite).

⑦ NO effect of Temperature.

⑧ Zero Input offset voltage.

(ii)

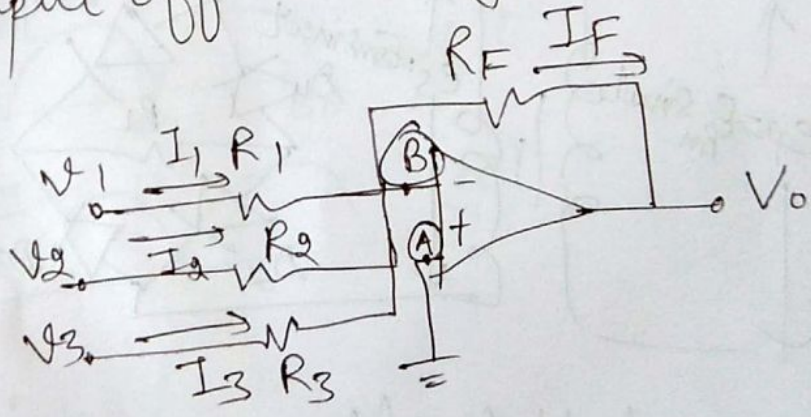

$V_A = 0$

$V_B = V_A = 0V$ (By Virtual Ground Concept)

Applying KCL at node B,

$I_1 + I_2 + I_3 = I_F$

Eqn.

$$\frac{V_1 - V_0}{R_1} + \frac{V_2 - V_0}{R_2} + \frac{V_3 - V_0}{R_3} = \frac{0 - V_0}{R_F}$$


$$\Rightarrow V_0 = -R_F \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right)$$

$$V_0 = -\frac{R_F}{R_1} V_1 - \frac{R_F}{R_2} V_2 - \frac{R_F}{R_3} V_3$$

When $R_F = R_1 = R_2 = R_3 = R$

$$\Rightarrow \boxed{V_0 = -(V_1 + V_2 + V_3)} \rightarrow \text{Adder/Summer output Voltage.}$$


Ans 2

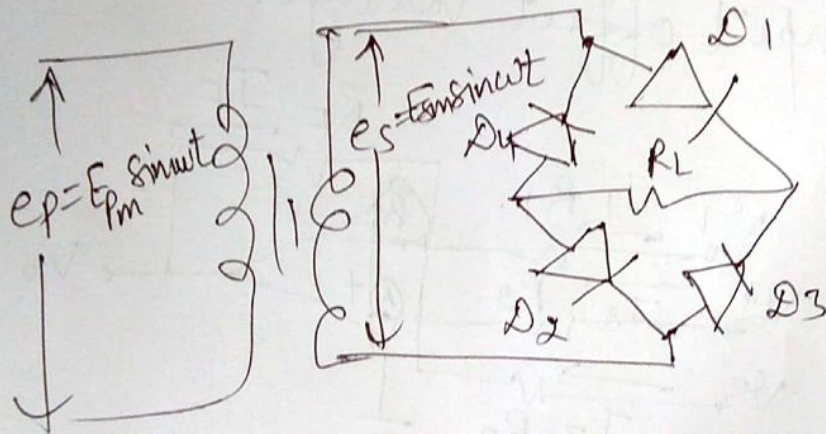

1 Mark diagram

All D_1, D_2, D_3, D_4 are ideal diodes.


Case-I +ve half cycle

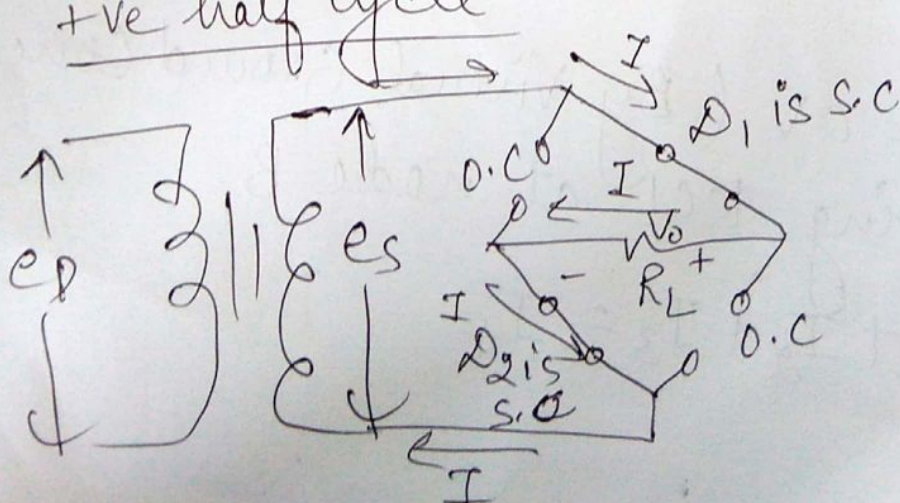

1 Mark

D_1 and D_2 are forward biased so short circuited. D_3 and D_4 are replaced with open circuit. so, v_o is obtained.


Case II -ve Half cycle.

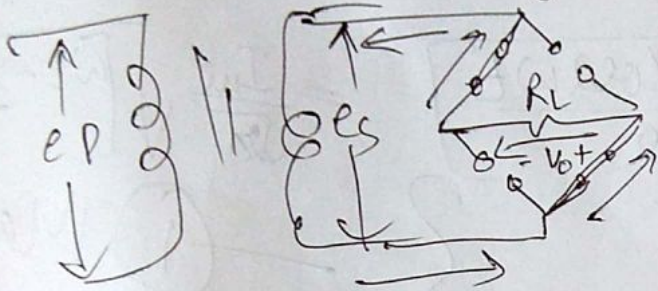

$D_1, D_2 \rightarrow$ open circuited
 $D_3, D_4 \rightarrow$ short circuited

1 Mark

so v_o is obtained across R_L .

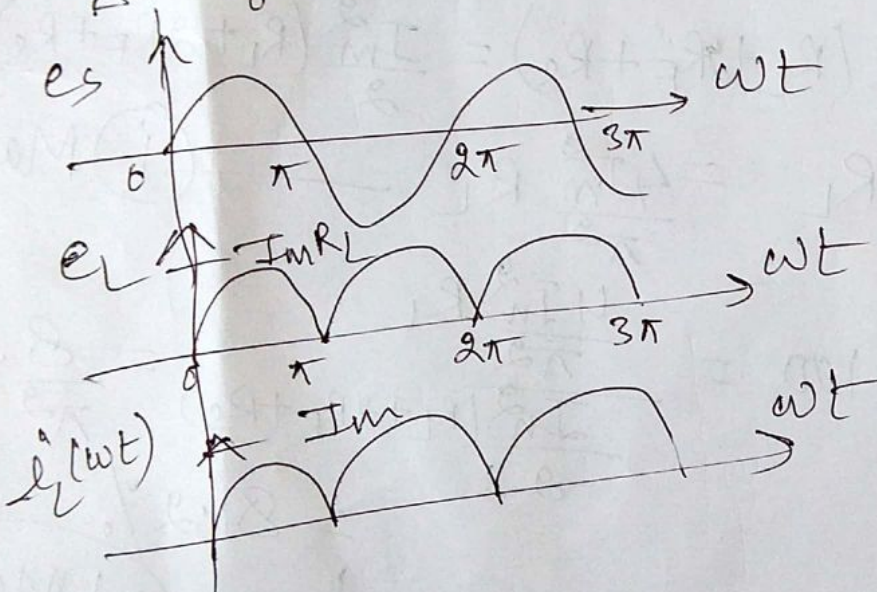

1 Mark
 waveform.

Derivations :-

$$I_{dc} = \frac{1}{T} \int_0^T i_L(\omega t) d(\omega t)$$

$$= \frac{1}{\pi} \int_0^{\pi} I_m \sin \omega t d(\omega t)$$

$$= \frac{I_m}{\pi} (-\cos \omega t)_0^{\pi} = \frac{I_m}{\pi} [-\cos \pi + \cos 0] = \frac{2I_m}{\pi}$$

1 Mark



$$\begin{aligned}
 \textcircled{2} \quad I_{\text{rms}} &= \sqrt{\frac{1}{T} \int_0^T i_L^2(\omega t) d(\omega t)} \\
 &= \sqrt{\frac{1}{\pi} \int_0^{\pi} I_m^2 \sin^2 \omega t d(\omega t)} \\
 &= \frac{I_m}{\sqrt{\pi}} \sqrt{\int_0^{\pi} \frac{1 - \cos 2\omega t}{2} d(\omega t)} = \frac{I_m}{\sqrt{\pi}} \sqrt{\left[\omega t - \frac{\sin 2\omega t}{2} \right]_0^{\pi}} \\
 I_{\text{rms}} &= \frac{I_m}{\sqrt{2}} \quad \text{--- (1) Mark}
 \end{aligned}$$

$$\textcircled{3} \quad P_{\text{ac}} = I_{\text{rms}}^2 (R_L + 2R_F + R_S) = \frac{I_m^2}{2} (R_L + 2R_F + R_S) \quad \text{--- (1) Mark}$$

$$P_{\text{dc}} = I_{\text{dc}}^2 R_L = \frac{4I_m^2}{\pi^2} R_L \quad \text{--- (1) Mark}$$

$$\eta \% = \frac{P_{\text{dc}}}{P_{\text{ac}}} \times 100 = \frac{\frac{4I_m^2}{\pi^2} R_L}{\frac{I_m^2}{2} (R_L + 2R_F + R_S)} = \frac{8}{\pi^2} \times 100$$

$$= 81.2\% \quad \text{--- (1) Mark}$$


Ans-3
(a)

$$V_o = -[2V_1 + 3V_2 + 5V_3] \quad \text{if } R_F = 10\text{K}\Omega$$

$$V_o = -\frac{R_F}{R_1} V_1 - \frac{R_F}{R_2} V_2 - \frac{R_F}{R_3} V_3 \quad \text{--- (1) Mark}$$


$$\Rightarrow \frac{R_F}{R_1} = 2, \quad \frac{R_F}{R_2} = 3, \quad \frac{R_F}{R_3} = 5 \quad \text{--- (1) Mark}$$

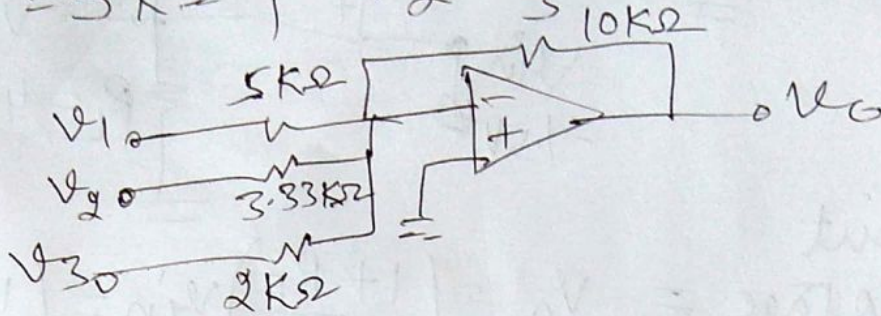$R_F = 10\text{K}\Omega$
 $\Rightarrow R_1 = 5\text{K}\Omega, R_2 = \frac{10}{3} = 3.33\text{K}\Omega, R_3 = 2\text{K}\Omega$



1 Mark

Ques 3
b

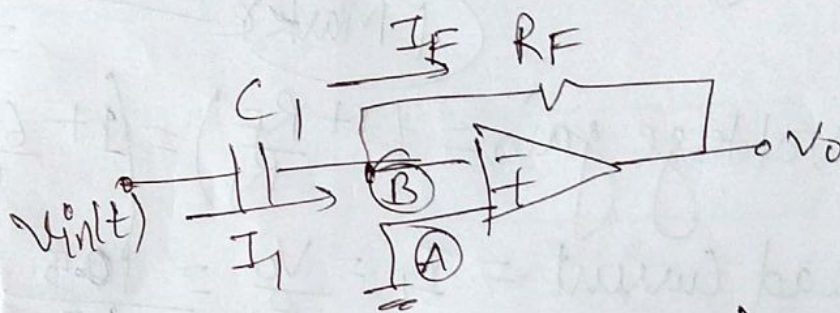

2 Mark

$V_A = 0\text{V}$
 $V_B = V_A = 0\text{V}$ (Virtual Ground)
 KCL at node B,


$I_1 = I_F$
 $C_1 \frac{dv_{in}(t)}{dt} = \frac{0 - V_0}{R_F}$

3 Mark

$\Rightarrow V_0 = -C_1 R_F \frac{dv_{in}(t)}{dt}$

So when $v_{in}(t)$ is applied V_0 's differentiation of input signal.

Ans-4 (b)

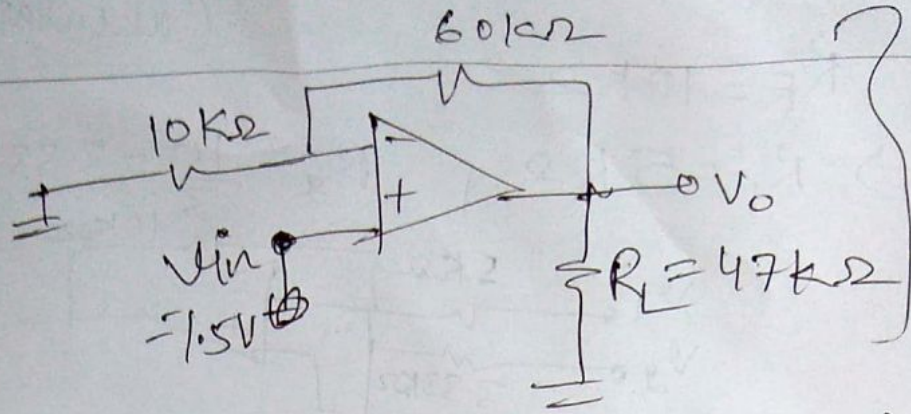


1 Mark

① output voltage = $V_o = \left(1 + \frac{R_F}{R_1}\right) V_{in} = \left(1 + \frac{60}{10}\right) 1.5$
 = $7 \times 1.5 = 10.5V$ (1 Mark)

② voltage gain = $\left(1 + \frac{R_F}{R_1}\right) = \left(1 + \frac{60}{10}\right) = 7$ (1 mark)

③ Load current = $I_L = \frac{V_o}{R_L} = \frac{10.5}{47 \times 10^3} = 0.223 \text{ mA}$ (2 Mark)

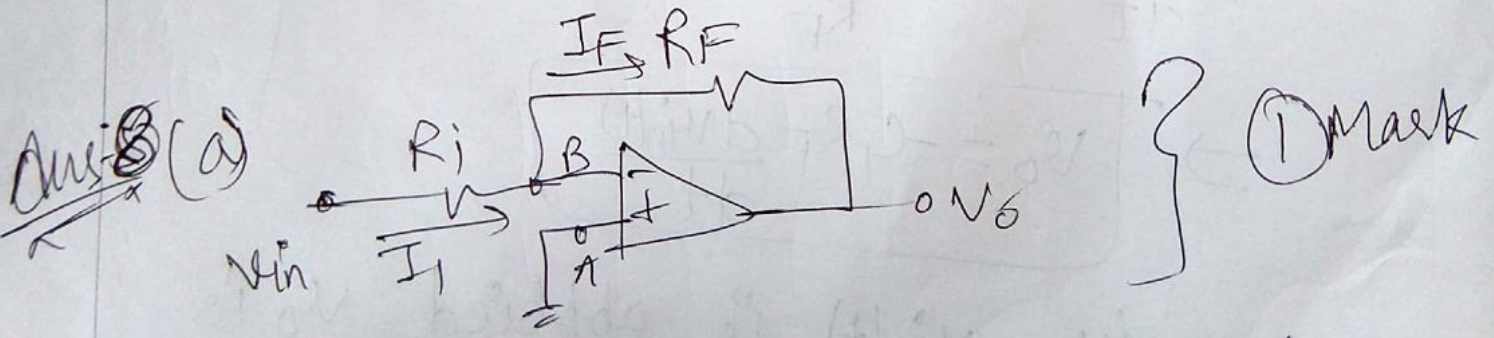Ans-4 (a) Note on LED and Photodiode (2.5 Mark)



1 Mark

$V_A = 0V$
 $V_B = V_A = 0V$ (Virtual ground)
 KCL at node B

$$I_1 = I_F$$

$$\frac{v_{in} - 0}{R_1} = \frac{0 - v_o}{R_F}$$



$$\Rightarrow v_o = -\frac{R_F}{R_1} v_{in}$$

3 Mark

$$\text{Gain} = \frac{R_F}{R_1}$$

When $R_F = R_1$

$$v_o = -v_{in}$$

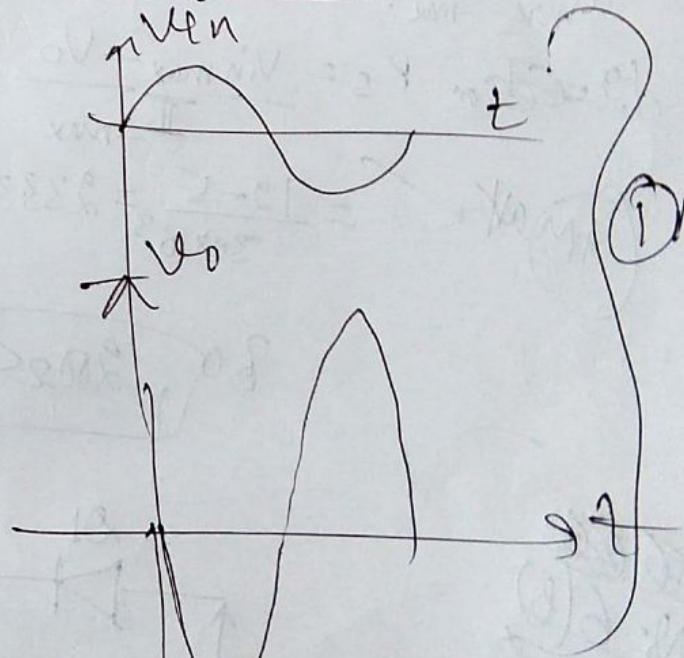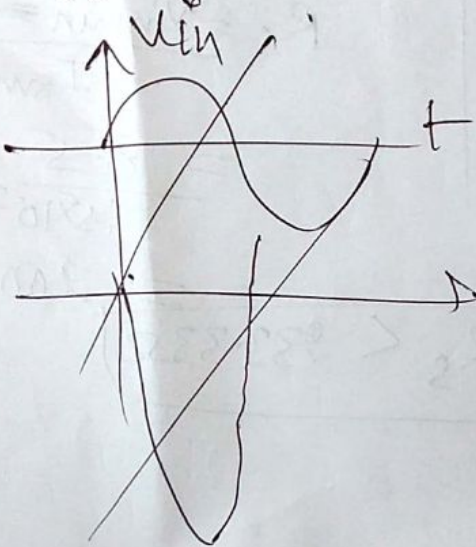

1 Mark

Ans. 8(b)

$$\text{i/p} \rightarrow v_{in}(t) = 10 \times 10^3 \sin(2\pi \times 1.5 \times 10^3 t)$$


$$v_o = -R_F C_1 \frac{dv_{in}(t)}{dt} = -100 \times 10^3 \times 1 \times 10^{-6} \frac{d(10^3 \sin(3\pi \times 10^3 t))}{dt}$$

$$= -10^{-8} \cos(3\pi \times 10^3 t) \times 3\pi \times 10^3$$

$$v_o = -3\pi \cos(3\pi \times 10^3 t)$$

$$v_o = -3\pi \cos(3\pi \times 10^3 t)$$

CMR
Ans-6(a)

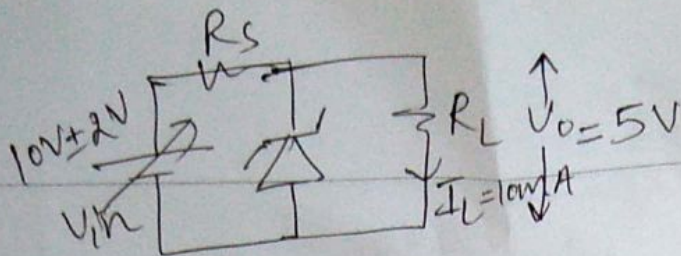

$I_L = 10\text{mA}$

$I_{z\text{min}} = 5\text{mA}$
 $I_{z\text{max}} = ?$

$P_z = 100\text{mW} = I_{z\text{max}} V_z$
 $I_{z\text{max}} = \frac{100 \times 10^{-3}}{5} = 20\text{mA}$ (1 Mark)

$R_L = \frac{V_o}{I_L} = \frac{5}{10 \times 10^{-3}} = 500\Omega$ (1 Mark)

$I_{s\text{min}} = I_{z\text{min}} + I_L$
 $I_{s\text{min}} = 5 + 10 = 15\text{mA}$

$I_{s\text{max}} = I_{z\text{max}} + I_L$
 $I_{s\text{max}} = 20\text{mA} + 10 = 30\text{mA}$ (1 Mark)

$V_{in\text{max}} = I_{s\text{max}} R_s + V_o$

$V_{in\text{min}} = I_{s\text{min}} R_s + V_o$

$R_s = \frac{V_{in\text{min}} - V_o}{I_{s\text{min}}}$



$= \frac{8 - 5}{15 \times 10^{-3}} = \frac{3}{15 \times 10^{-3}}$

$= 200\Omega$ (1 Mark)

$R_s = \frac{V_{in\text{max}} - V_o}{I_{s\text{max}}}$
 $= \frac{12 - 5}{30 \times 10^{-3}} = 233.3\Omega$ (1 Mark)

So, $200\Omega \leq R_s < 233.33\Omega$

Ans-6(B)

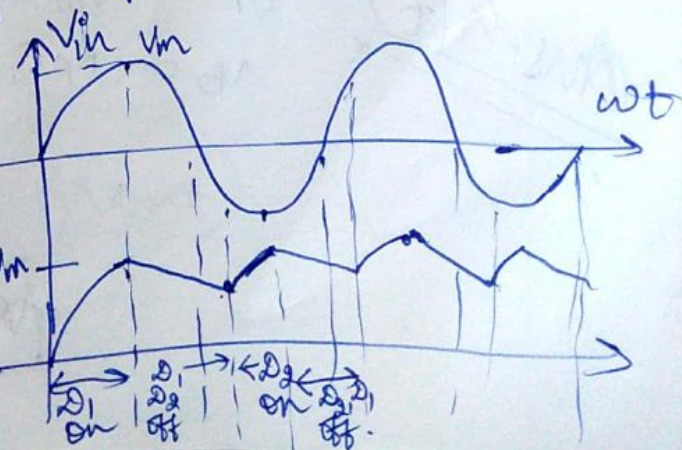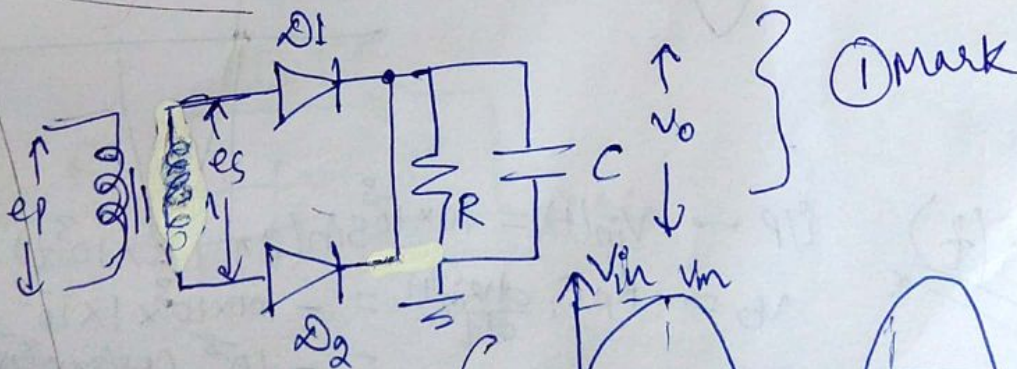

Explanation - (2 Mark)

(2 Mark)