
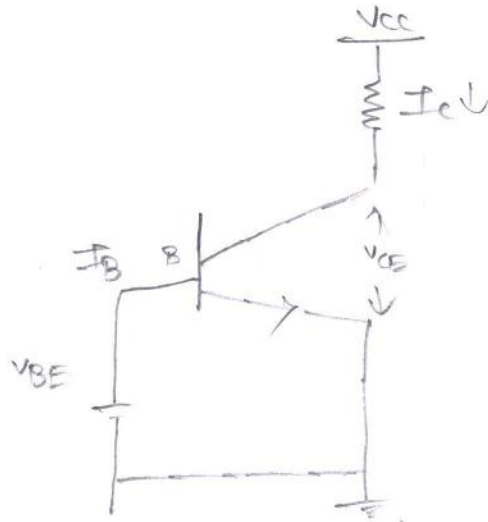


IAT-3


The operation of BJT as an switch:-

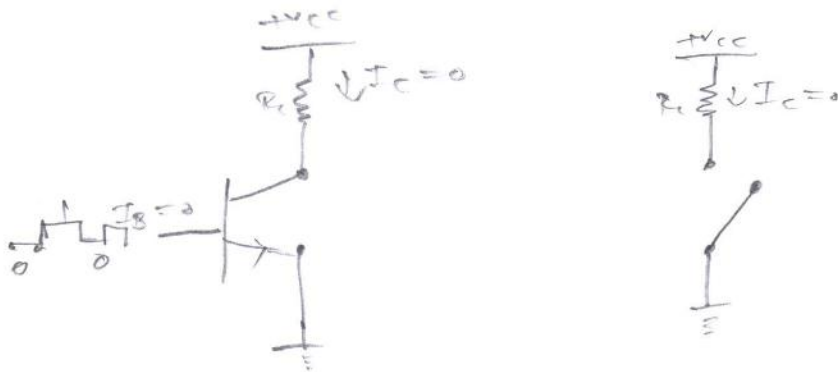

* In this we are giving the square wave signal
 * when we are giving current is also $I_C = 0$ then the output then it acts as open switch.




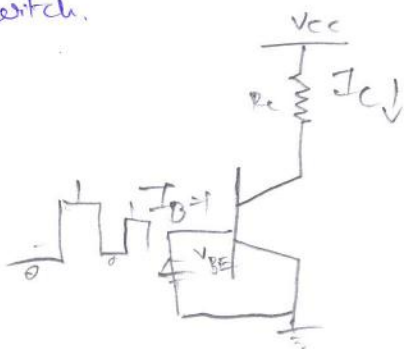* In this when we are given the value that means $I_B = 1$ then the output is there then it acts as closed switch.




$$V_{CC} = I_C R_C + V_{BE}$$


$$I_C = \frac{V_{CC} - V_{BE}}{R_C}$$

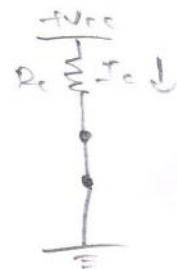

BJT as an amplifier:-

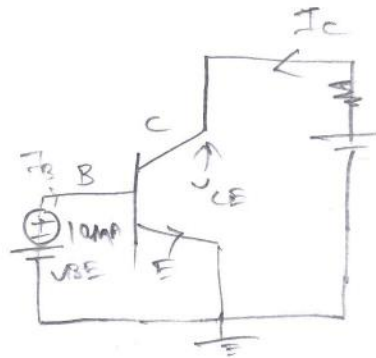

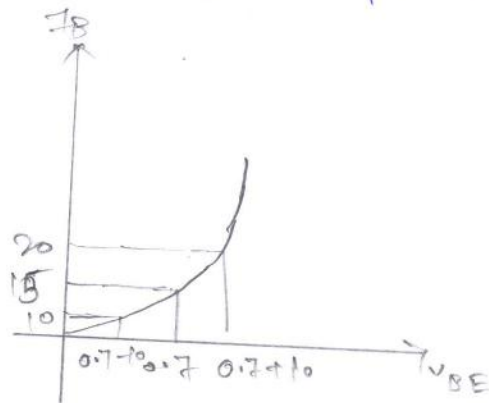Consider an npn transistor and that will be given
 BE is in forward bias and CB is connected in reverse
 bias and we are given β has 100 mA .



construct a graph that will be $I_B (V)$ vs V_{BE}
 from this graph

At $0.7-10$, $V_B = 10 \mu\text{A}$

At $0.7+10$, $V_B = 20 \mu\text{A}$

$$\Delta V_B = 20 - 10 \mu\text{A} = 10 \mu\text{A}$$

$$\begin{aligned} \text{By graph, } \Delta V_C &= (0.7+10) - (0.7-10) \\ &= 20 \text{ mA} \end{aligned}$$


w.k.T

$$\Delta V = \frac{\Delta V_B}{\Delta V_C} = \frac{10 \mu\text{A}}{20 \text{ mA}} = 50$$

Now we can say that it is amplified.

27

Barkhausen's criterion

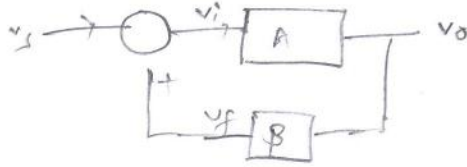

$$\beta = \frac{v_f}{v_o} \Rightarrow v_f = -\beta v_o \rightarrow \textcircled{1}$$

$$A = \frac{v_o}{v_i} \Rightarrow v_o = A v_i \rightarrow \textcircled{2}$$

$$v_i = v_f \quad (\text{here source } v_s \text{ is zero})$$

Substituting $\textcircled{2}$ in $\textcircled{1}$

$$v_f = -\beta(A v_i)$$

$$v_f = -\beta A v_f$$

$$A\beta = -1$$

-ve sign indicates phase shift

$$|A\beta| = 1$$


Criteria 1:-

Magnitude is product of the amplifier A and β feed back factor is unity.

Criteria 2:-

If it is connected to the input signal with the feedback factor there will be phase of 360° (or) 0°

Operation of RC phase :-

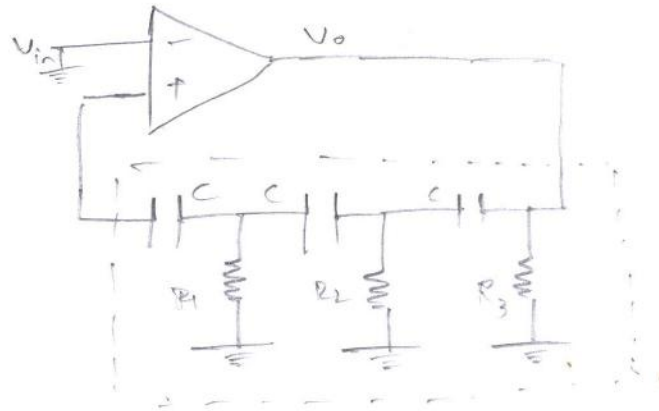

$$f = \frac{1}{2\pi \sqrt{6} RC}$$

Here 1 capacitor RC indicates 60° phase shift
 2 RC indicates 180° phase shift
 3 RC indicates the 0° (or) 360° phase shift
 (by criteria 2).




37

FET:-

It has 3 parts Gate, Drain, Source
It is similar to the Transistor.



Construction of n-channel JFET:-

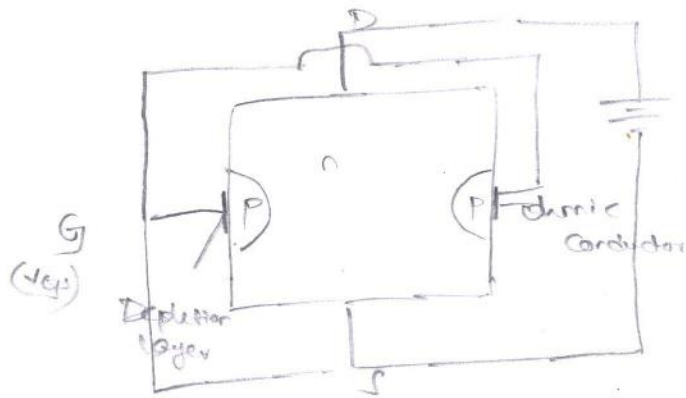

In this n-channel JFET it has two cases



$\therefore V_{GS} = 0$
 $\therefore V_{GS} < 0$

Here $V_{DS} > 0$
 (Positive)



Here in this n-channel JFET we taking pnp
 on the side depletion layer and other is connected to
 Ohmic conductor and G is connected to the Ohmic
 and source also connected to the Gate and Drain
 connects to the source to get V_{DS}

Working :-
Case i :-


$$V_{GS} = 0, V_{DS} > 0$$

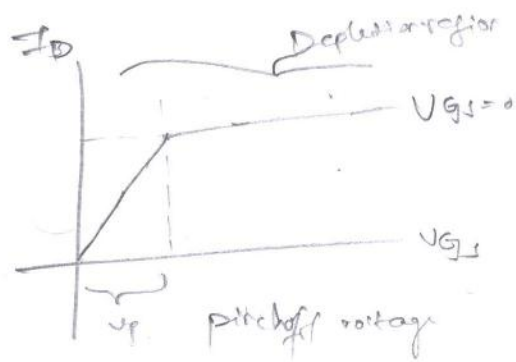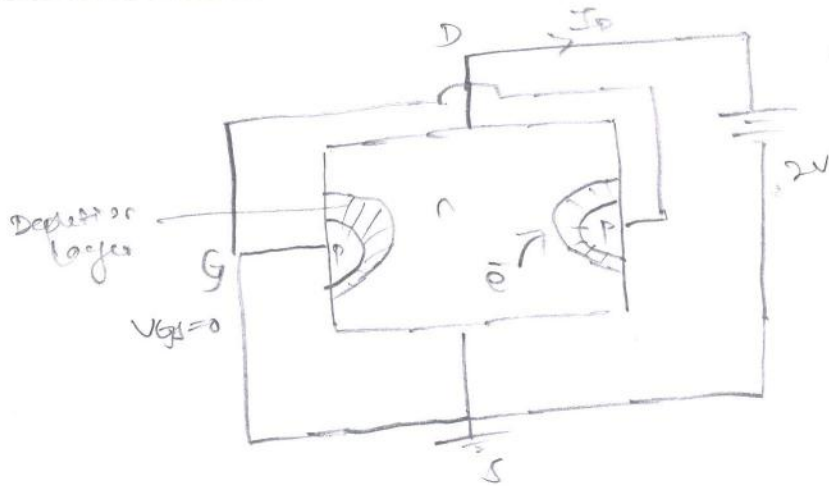

Case ii: $V_{GS} < 0, V_{DS} > 0$

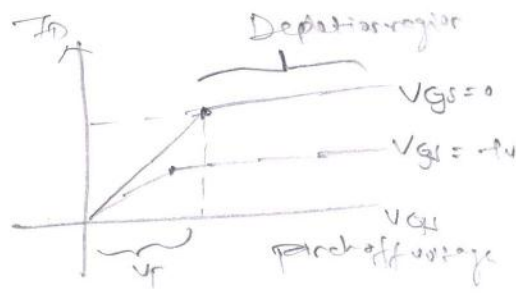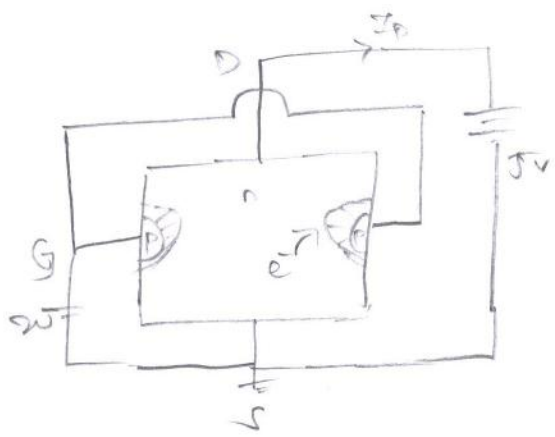

Drain characteristics:-

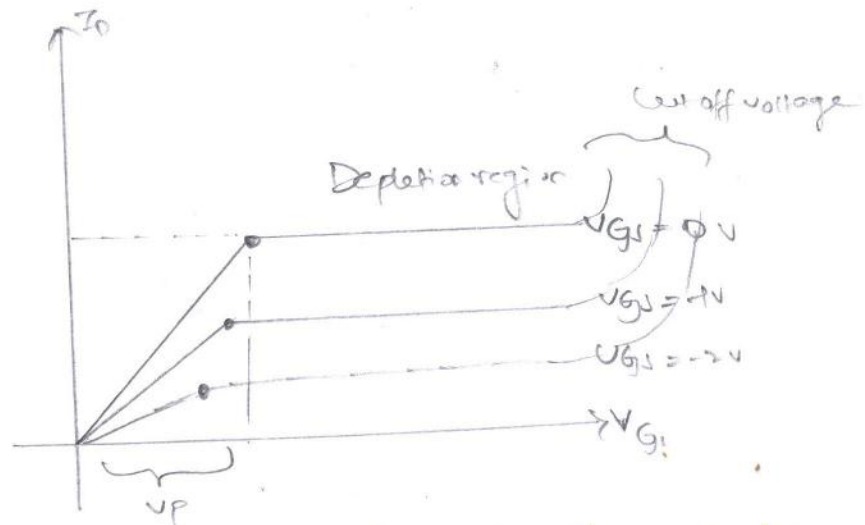


By taking the graph of I_D and V_{GS}

$$I_D = I_{DSS} \left[1 - \frac{V_{GS}}{V_P} \right]^2$$

This is the Drain characteristic formula.

Transfer characteristics:-

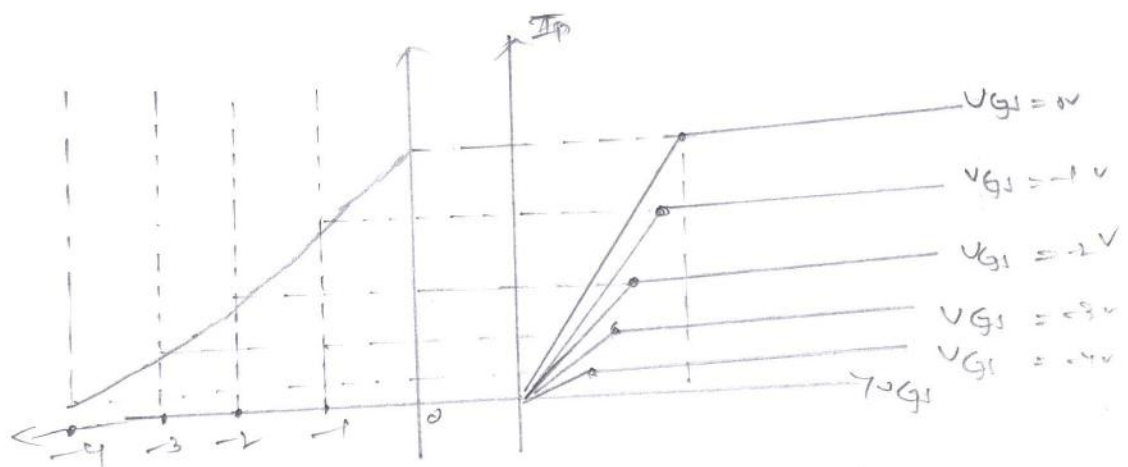

Q7 A Certain JFET has of $2 \text{ nA} = I_{g1}$

$$V_{GS} = -20 \text{ V}$$

By Ohm's law


$$V = IR$$

$$R = \frac{-20 \text{ V}}{-2 \text{ nA}}$$

$$= \frac{+20}{2 \times 10^{-9}}$$

$$R = 10^{10} \Omega$$

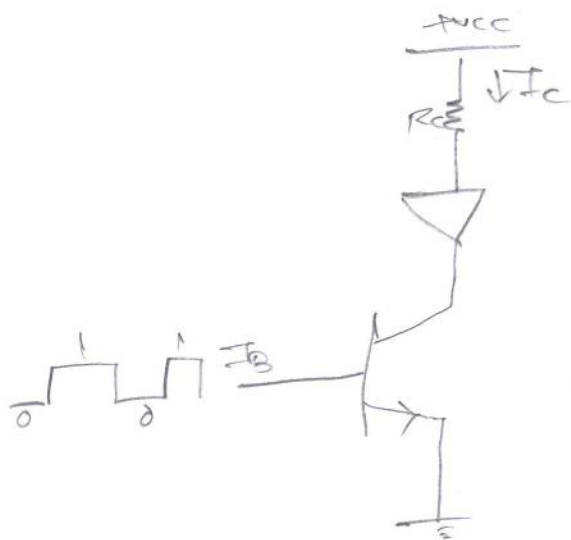Q7 transistor switch circuit to turn on/off an LED:-



In this  we are taking the square wave signal.

* when we are giving $I_B = 0$ and there is no I_C . $I_C = 0$ and it acts as open switch the LED will be off.

* when we are giving $I_B = 1$ and there is I_C . $I_C = \frac{V_{CC} - V_{LED}}{R_{ce}}$ and it acts as closed switch the LED will be on for ~~that~~ and it will off



Q7



Oscillators:-

Oscillators is works on the positive feedback, and In this there is no input voltage is given to the circuit. the voltage already present in that acts as noise.

$$\text{for oscillator } \frac{A}{1-AB}$$

Wien bridge oscillator:-

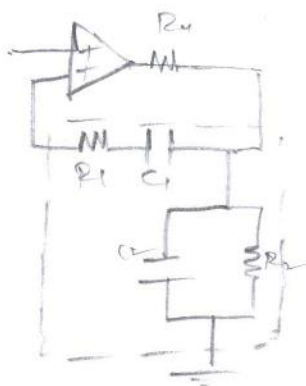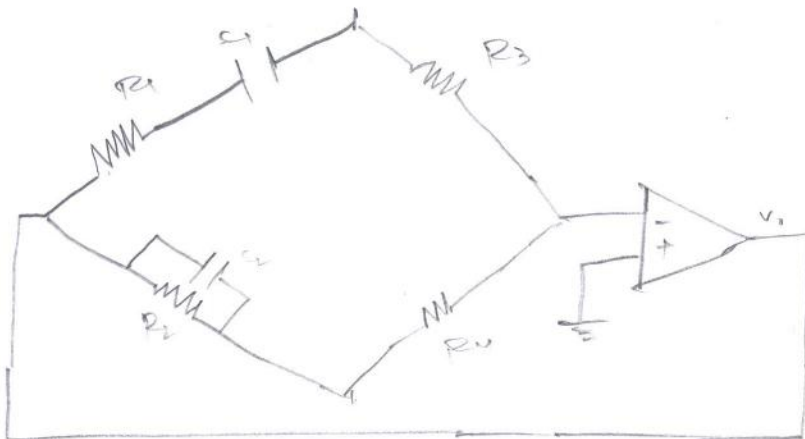

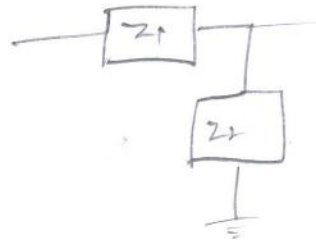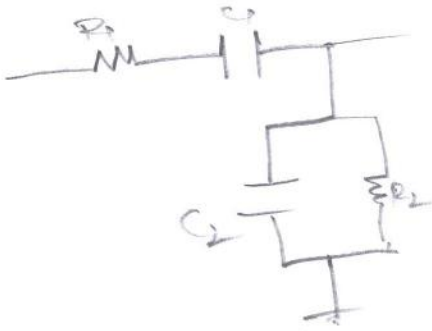

$$Z_1 = R_1 + \frac{1}{j\omega C_1}$$

$$\frac{1}{Z_2} = \frac{1}{R_2} + \frac{1}{1/j\omega C_2}$$

$$= \frac{1}{R_2} + \frac{j\omega C_2}{1}$$

$$\frac{1}{Z_2} = \frac{1 + j\omega C_2 R_2}{R_2} \Rightarrow Z_2 = \frac{R_2}{1 + j\omega C_2 R_2}$$

$$V_0 = \frac{Z_2 V_{in}}{Z_1 + Z_2}$$

$$\frac{V_0}{V_{in}} = \frac{Z_2}{Z_1 + Z_2}$$

$$= \frac{R_2}{1 + j\omega C_2 R_2}$$

$$R_1 + \frac{1}{j\omega C_1} + \frac{R_2}{1 + j\omega C_2 R_2}$$

$$= \frac{R_2}{1 + j\omega C_2 R_2}$$

$$\frac{R_1 j\omega C_1 + 1}{j\omega C_1} + \frac{R_2}{1 + j\omega C_2 R_2}$$

$$= \frac{R_2}{1 + j\omega C_2 R_2}$$

$$\frac{(R_1 + j\omega R_1 R_2)(1 + j\omega R_1 C_1) + R_2(j\omega C_1)}{j\omega C_1(1 + j\omega C_2 R_2)}$$

$$= \frac{R_2(j\omega C_1)(1 + j\omega C_2 R_2)}{R_2(j\omega C_1) + (1 + j\omega C_2 R_2)(1 + j\omega R_1 C_1)}$$

$$= \frac{j\omega C_1 R_2}{\omega^2 R_1 C_1 R_2 C_2 + 1 + j\omega(R_1^2 C_1^2 + R_2 C_2)}$$

By taking Real part is zero

$$\omega^2 R_1 C_1 R_2 C_2 - 1 = 0$$

$$\omega^2 R_1 C_1 R_2 C_2 = 1$$

$$\omega^2 = \frac{1}{R_1 C_1 R_2 C_2}$$

$$\omega = \frac{1}{\sqrt{R_1 C_1 R_2 C_2}}$$

$$2\pi f = \frac{1}{\sqrt{R_1 C_1 R_2 C_2}}$$

$$f = \frac{1}{2\pi \sqrt{R_1 C_1 R_2 C_2}}$$

if $R_1 = R_2 = R$
 $C_1 = C_2 = C$

$$f = \frac{1}{2\pi RC}$$