

USN

--	--	--	--	--	--	--	--	--	--



Internal Assessment Test 1 – Sept. 2018

Sub:	Analog Electronics	Sub Code:	17EC33	Branch:	ECE
Date:	08-09-18	Duration:	90 min's	Max Marks:	50
		Sem / Sec:	3 rd / A, B, C		

Answer all FIVE FULL Questions

		MARKS	CO	RBT
1	Derive an expression for input impedance, output impedance, voltage gain and current gain for voltage divider bias CE amplifier using r_e model. (OR) Derive an expression for input impedance, output impedance, voltage gain and current gain of an un-bypassed R_E CE amplifier using r_e model.	[10]	CO1	L2
2	Derive an expression for input impedance, output impedance, voltage gain and current gain for Fixed bias Configuration using approximate hybrid model. (OR) Derive an expression for current gain, voltage gain, input impedance and output impedance of transistor amplifier using h-parameters. (Complete Hybrid model)	[10]	CO1	L2
3	For the network shown in Fig.1 determine, (with $r_o = \infty \Omega$) i) r_e ii) Z_i iii) Z_o iv) A_v v) A_i	[10]	CO1	L3

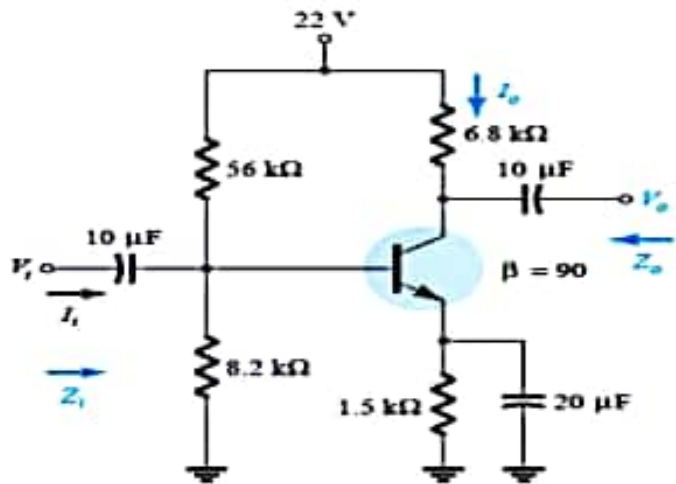


Fig: 1

4	Find input impedance, output impedance, voltage gain and current gain of emitter follower configuration where $V_{CC}=10V$, $R_B=100K\Omega$, $R_E=1K\Omega$, $h_{ie}=1.1K\Omega$, $h_{fe}=100$. Use approximate hybrid equivalent model.	[10]	CO1	L3
---	--	------	-----	----

- 5 (a) Calculate DC bias voltages and currents for the Darlington configuration shown in Fig.2 [05]

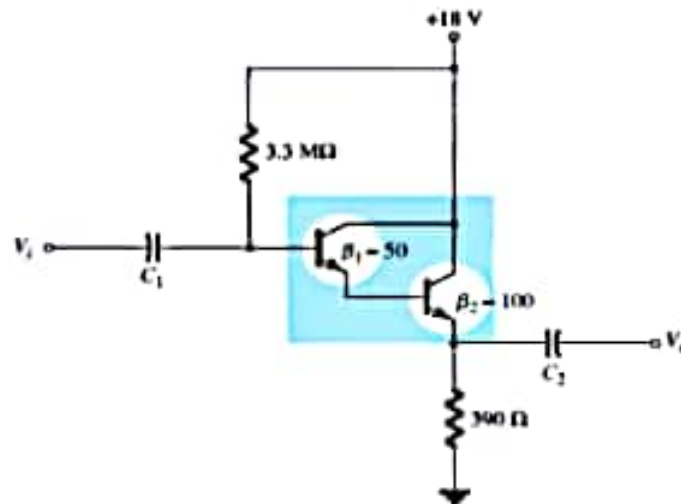


Fig: 2

- (b) Calculate the output voltage (V_o) and Zener current in the regulator circuit shown in Fig.3 for $R_L = 1 \text{ k}\Omega$. [05]

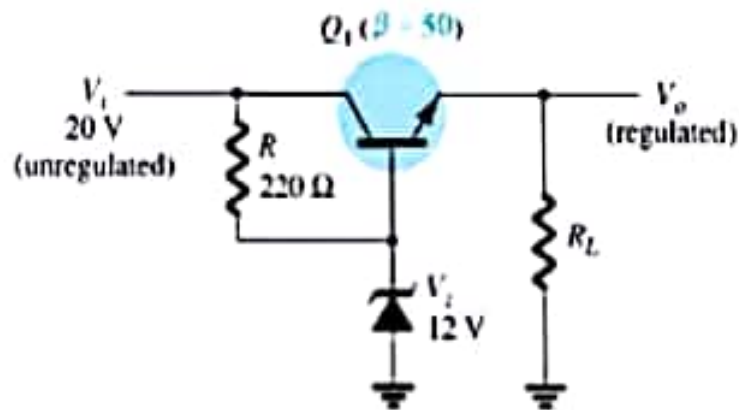


Fig: 3

*** ALL THE BEST ***

E.C.F

AE - 1AT-1 Solutions

Date: 11/09/18

Q3

(i) r_e using approximate approach

$$V_{th} = \frac{V_{cc} \times R_2}{R_1 + R_2} = \frac{22 \times 8.2k}{56k + 8.2k} = 2.81V$$

$$R_{th} = 8.2k \parallel 56k = 7.15k\Omega$$

$$I_B = \frac{V_{th} - V_{BE}}{R_{th} + (1 + \beta) R_E} = \frac{2.81 - 0.7}{7.15k + (1 + 90) 1.5k} = 14.69 \mu A$$

$$I_E = (1 + \beta) I_B = (1 + 90) \times 14.69 \times 10^{-6} = 1.34 mA$$

$$r_e = \frac{26mV}{I_E} = \frac{26mV}{1.34mA} = 19.40 \Omega$$


$$V_B = \frac{V_{cc} \times R_2}{R_1 + R_2} = \frac{22 \times 8.2k}{56k + 8.2k} = 2.81V$$

$$V_E = V_B - V_{BE} = 2.81 - 0.7 = 2.11V$$

(OR)

$$I_E = \frac{V_E}{R_E} = \frac{2.11}{1.5k} = 1.41 mA$$
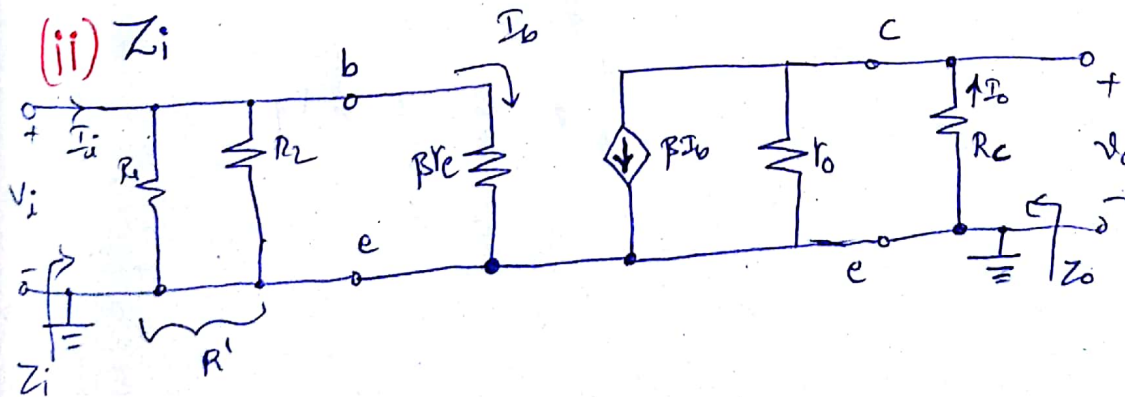
$$r_e = \frac{26mV}{I_E} = 18.44 \Omega$$



Q3

$$R' = R \parallel R_2 = 7.15 \text{ k}\Omega$$

$$Z_i = R' \parallel \beta r_e = 7.15 \text{ k}\Omega \parallel (90)(18.44)$$
$$= 7.15 \text{ k}\Omega \parallel 1.66 \text{ k}\Omega = 1.35 \text{ k}\Omega$$

$$Z_i = 1.35 \text{ k}\Omega$$

(iii) $Z_o = R_c = 6.8 \text{ k}\Omega$

(iv) A_v

$$A_v = -\frac{R_c \parallel r_o}{r_e}$$

$$= -\frac{6.8 \text{ k}\Omega \parallel \infty}{r_e}$$

$$\approx -\frac{6.8 \text{ k}\Omega}{18.44 \Omega} = -368.763$$

$$A_v \approx -368.76$$

$$= 7.15 \text{ k}\Omega \parallel (90)(19.44)$$
$$= 7.15 \text{ k}\Omega \parallel 1.74 \text{ k}\Omega$$

$$Z_i = 1.39 \text{ k}\Omega$$

$$r_e = 19.44 \Omega$$

$$A_v = -\frac{6.8 \text{ k}\Omega}{19.44 \Omega} = -350.51$$

$$A_v \approx -350.51$$

✓ A_i ($r_o = \infty$)

Method 1

$$A_i \approx \frac{\beta R'}{R' + \beta r_e} \quad (\because r_o > 10R_c)$$

$$\approx \frac{90 \times 7.15K}{7.15K + 1.66K}$$

$$\approx 73.04$$

(OR)

Method 2

$$A_i = -A_v \cdot \frac{Z_i}{R_c}$$

$$= - \frac{(-368.76 \times 1.35K)}{6.8K}$$

$$= 73.20$$

finally:

$$r_e = 18.44\Omega$$

$Z_i = 1.35K\Omega$
$Z_o = 6.8K\Omega$
$A_v = -368.76$
$A_i = 73.04$

$$A_i \approx \frac{\beta R'}{R' + \beta r_e}$$

$$\approx \frac{90 \times 7.15K}{7.15K + 1.74K}$$

$$\approx 72.38$$

(OR)

$$A_i = - \frac{350.51 \times 1.39K}{6.8K}$$

$$= 71.64$$

$$r_e = 19.40\Omega$$

$Z_i = 1.39K\Omega$
$Z_o = 6.8K\Omega$
$A_v = -350.51$
$A_i = 72.38$

Q4

Ans:

Given data


$$V_{CC} = 10V$$

$$R_B = 100k\Omega$$

$$R_E = 1k\Omega$$

$$h_{ie} = 1.1k\Omega$$

$$h_{fe} = 100$$

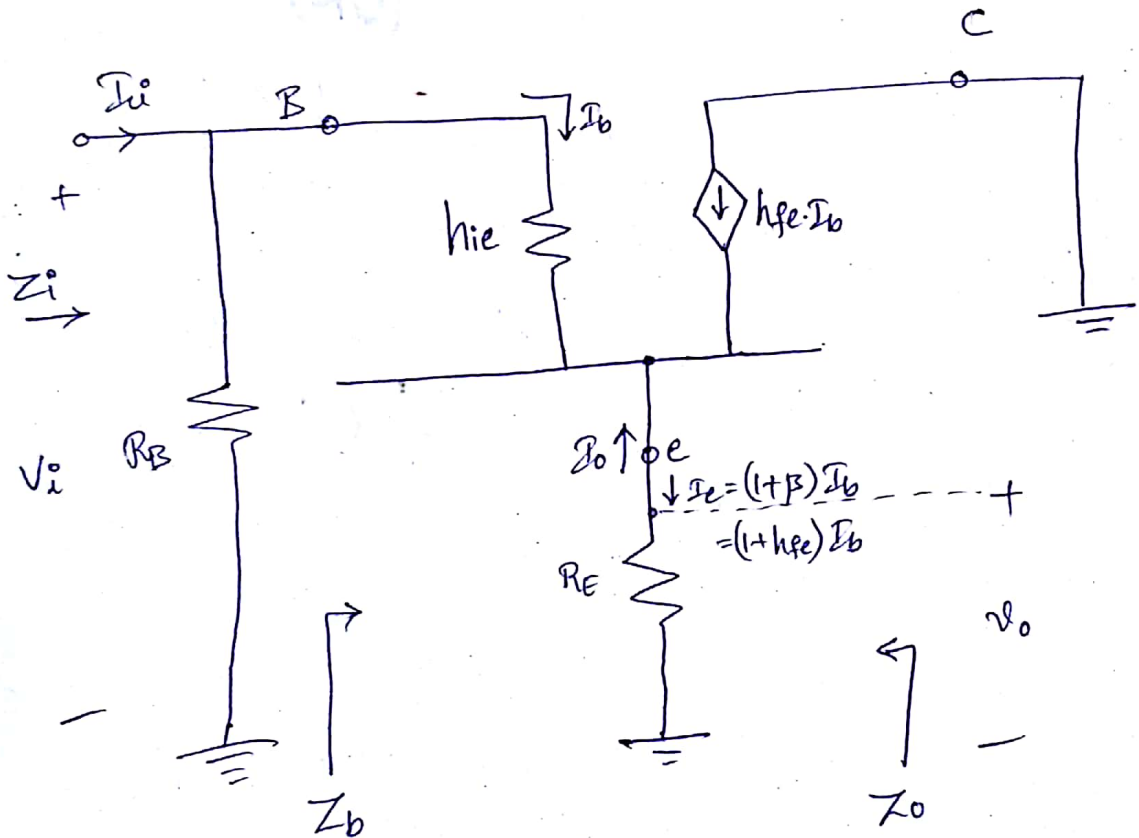

Z_i:

$$Z_b \approx h_{fe} \cdot R_E \quad [\because R_E \gg h_{ie}]$$

$$\approx 100 \times 1K$$

$$\approx 100k\Omega$$

$$Z_i = R_B \parallel Z_b = 100k \parallel 100k = 50k\Omega$$

$$Z_i = 50k\Omega$$

Z_o:

$$Z_o = R_E \parallel \frac{h_{ie}}{1+h_{fe}}$$

$$Z_o \approx R_E \parallel \frac{h_{ie}}{h_{fe}}$$

[∵ 1+h_{fe} ≈ h_{fe}]

$$\approx 1k \parallel \frac{1.1k\Omega}{100}$$

$$\approx 1k \parallel 11$$

$$\approx 10.88\Omega$$

$Z_o \approx 10.88\Omega$

A_v:

$$A_v \approx \frac{R_E}{R_E + h_{ie}/h_{fe}} \approx \frac{1k}{1k + 11} \approx 0.989$$

$A_v = 0.989$

A_i:

$$A_i \approx -\frac{h_{fe} \cdot R_B}{R_B + Z_b} = -\frac{100 \times 100k\Omega}{100k + 100k} = -50$$

$A_i = -50$

(OR)

$$A_i = -A_v \cdot \frac{Z_i}{R_E} = -0.989 \times \frac{50k}{1k} = -49.45$$

Q5

(a)

Ans:

for Complete Ans. Refer page No: 310 Example 5.17

ED & Circuit theory, Robert L Boylestad, 11th Edition

$$\beta_D = 50 \times 100 = 5000 \quad \frac{1}{2} M$$

$$I_{B1} = 3.16 \mu A \quad 1 M$$

$$I_{C2} \approx I_{E2} = \beta_D \cdot I_{B1} = 15.80 mA \quad 1 M$$

$$V_{C1} = V_{C2} = 18 V \quad \text{[Red mark]}$$

$$V_{E2} = 6.16 V \quad \frac{1}{2} M$$

$$V_{B1} = 7.56 V \quad 1 M$$

$$V_{CE2} = 11.84 V \quad \frac{1 M}{5 M}$$

Q5

(b)

Ans:

for Complete Ans Refer page No: 814 Example 15.8

ED & Circuit theory, Robert L Boylestad, 11th Edition.

$$V_o = V_z - V_{BE} = 11.3 V \quad (1 M)$$

$$V_{CE} = V_i - V_o = 8.7 V \quad (1 M)$$

$$I_R = 36.4 mA \quad (1 M)$$

$$I_L = 11.3 mA \quad \frac{1}{2} M$$

$$(1 M) \left\{ \begin{array}{l} I_L = I_C = I_E \\ I_B = \frac{I_C}{\beta} = \frac{11.3 mA}{50} = 226 \mu A \end{array} \right.$$

$$\left(\frac{1}{2} M \right) I_z = I_R - I_B = 36.4 mA - 226 \mu A \approx 36 mA$$

5 M