

Internal Assessment Test - I

Sub:	DIGITAL SYSTEM DESIGN						Code:	15EE35		
Date:	20/ 09/ 2017	Duration:	90 mins	Max Marks:	50	Sem:	7th	Branch:	EEE	
Answer Any FIVE FULL Questions										
								Marks	OBE	
									CO	RBT
1	Design a logic circuit which takes two,2-bit binary numbers as its input and generates an output equal to 1,when sum of two numbers is odd, use K-map to simplify.						10	C305.2	L3	
2	Find a minimum SOP solution using Quine-McCluskey method $F(a,b,c,d)=\sum m(1,3,4,5,6,7,10,12,13) +d(2,9,15)$.						10	C305.1	L3	
3	Simplify $f(a,b,c,d)=\sum m(2,3,4,5,13,15)+dc(8,9,10,11)$ using MEV technique taking least significant bit as map entered variable.						10	C305.1	L3	
4	Implement the function using active low output dual 2:4 decoder line decoder IC 74139 i) $F_1(A,B,C)=\sum m(0,1,2,5)$ ii) $F_2(A,B,C)=\pi M(1,3,4,7)$						10	C305.1	L3	
5	Design a priority encoder for a system with a 3 inputs, the middle bit with highest priority encoding to 10,the MSB with next priority encoding to 11,while the LSB with least priority encoding to 01.						10	C305.1	L3	
6	Realize the following Boolean function $Y=f(w,x,y,z)=\sum(0,1,5,6,7,10,15)$ using : i) 16 to 1 MUX ii)8:1 MUX iii)4:1 MUX.						10	C305.1	L3	

Internal Assessment Test - I

Sub:	DIGITAL SYSTEM DESIGN						Code:	15EE35		
Date:	20/ 09/ 2017	Duration:	90 mins	Max Marks:	50	Sem:	7th	Branch:	EEE	
Answer Any FIVE FULL Questions										
								Marks	OBE	
									CO	RBT
1	Design a logic circuit which takes two,2-bit binary numbers as its input and generates an output equal to 1,when sum of two numbers is odd, use K-map to simplify.						10	C305.2	L3	
2	Find a minimum SOP solution using Quine-McCluskey method $F(a,b,c,d)=\sum m(1,3,4,5,6,7,10,12,13) +d(2,9,15)$.						10	C305.1	L3	
3	Simplify $f(a,b,c,d)=\sum m(2,3,4,5,13,15)+dc(8,9,10,11)$ using MEV technique taking least significant bit as map entered variable.						10	C305.1	L3	
4	Implement the function using active low output dual 2:4 decoder line decoder IC 74139 i) $F_1(A,B,C)=\sum m(0,1,2,5)$ ii) $F_2(A,B,C)=\pi M(1,3,4,7)$						10	C305.1	L3	
5	Design a priority encoder for a system with a 3 inputs, the middle bit with highest priority encoding to 10,the MSB with next priority encoding to 11,while the LSB with least priority encoding to 01.						10	C305.1	L3	
6	Realize the following Boolean function $Y=f(w,x,y,z)=\sum(0,1,5,6,7,10,15)$ using : i) 16 to 1 MUX ii)8:1 MUX iii)4:1 MUX.						10	C305.1	L3	

Digital System Design IAT-1


①

	A	B	C	D	Y
0+0	0	0	0	0	0
0+1	0	0	0	1	1
	0	0	1	0	0
	0	0	1	1	1
	0	1	0	0	1
	0	1	0	1	0
	0	1	1	0	1
	0	1	1	1	0
	1	0	0	0	0
	1	0	0	1	1
	1	0	1	0	0
	1	0	1	1	1
	1	1	0	0	1
	1	1	0	1	0
	1	1	1	0	1
	1	1	1	1	0

		AB			
		00	01	11	10
CD	00	0	1	1	0
	01	1	0	0	1
11	1	0	0	1	
10	0	1	1	0	

$\frac{0100}{1100}{0110}{1110}$
 $\frac{010}{110}$
 $B'D$
 $\frac{0001}{0011}{1001}{1011}$
 $B'D$

$$Y = BD' + B'D$$

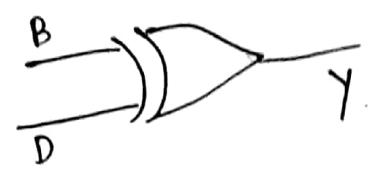

② $F(a,b,c,d) = \sum m(1,3,4,5,6,7,10,12,13) + d(2,9,15)$

		a,b			
		00	01	11	10
c,d	00	0 ₀	1 ₁	1 ₃	0 ₂
	01	1 ₄	1 ₅	1 ₇	X ₉
11	1 ₆	1 ₄	X ₅	0 ₁₁	
10	X ₂	1 ₁	0 ₁₄	1 ₁₀	

Annotations: $a'bd'$ points to cell (00,11); abc' points to cell (01,11); $a'dc$ points to cell (11,01); $b'cd'$ points to cell (10,10).

Minterms

m_1

m_3

m_4

m_5

m_6

m_7

m_{10}

m_{12}

m_{13}

m_{15}

0001 ✓
 0010 ✓
 0011 ✓
 0100 ✓
 0101 ✓
 0110 ✓
 0111 ✓
 1001 ✓
 1010 ✓
 1100 ✓
 1101
 1111

m_1

d_2

m_4

m_3

m_5

m_6

d_9

m_{10}

m_{12}

m_7

m_{13}

d_{15}

0001 ✓
 0010 ✓
 0100 ✓
 0011 ✓
 0101 ✓
 0101 ✓
 0110 ✓
 1001 ✓
 1010 ✓
 1100 ✓
 0111 ✓
 1101 ✓
 1111 ✓

(1,3) 00-1 ✓

(1,5) 0-01 ✓

(1,9) -001 ✓

(2,3) 001- ✓

(2,6) 0-10 ✓

(2,10) -010

(4,5) 010-

(4,6) 01-0

(4,12) -100

(3,7) 0-11 ✓

(5,7) 01-1 ✓

(6,7) 01-0 ✓

(9,13) 1-01 ✓

(12,13) 110-

(7,15) -111 ✓

(13,15) 11-1 ✓

(1,3,5,7) 0--1

~~(1,3,5,7)~~

~~(1,5,3,7) 0--1~~

(1,5,9,13) --01

(2,3,6,7) 0-1-

~~(2,6,3,7) 0-1-~~

(5,7,13,15) -1-1


	m_1	m_2	m_3	m_4	m_5	m_6	m_7	d_9	m_{10}	m_{12}	m_{13}	m_{15}
✓ (1, 3, 5, 7)	✓		✓		✓		✓					
(1, 5, 9, 13)	✓				✓			✓				✓
(2, 3, 6, 7)		✓	✓			✓	✓					
(5, 7, 13, 15)					✓		✓					✓
✓ (2, 10)		✓						✓				
(4, 5)				✓	✓							
✓ (4, 6)				✓		✓						
(4, 12)				✓						✓		
✓ (12, 13)										✓	✓	

(2, 10)	- 010	a	$b'cd'$
(1, 3, 5, 7)	0--1		$a'd$
(4, 6)	01-0		$a'bd'$
(12, 13)	110-		abc'

$$Y = b'cd' + a'd + a'bd' + abc'$$


$f(a,b,c,d) = \sum m(2,3,4,5,13,15) + d(8,9,10,11)$

a	b	c	d	Y	MEV map entry
0	0	0	0	0	0
0	0	0	1	0	
0	0	1	0	1	1
0	0	1	1	1	
0	1	0	0	1	1
0	1	0	1	1	
0	1	1	0	0	0
0	1	1	1	0	
1	0	0	0	X	X
1	0	0	1	X	
1	0	1	0	X	X
1	0	1	1	X	
1	1	0	0	0	d
1	1	0	1	1	
1	1	1	0	0	d
1	1	1	1	1	

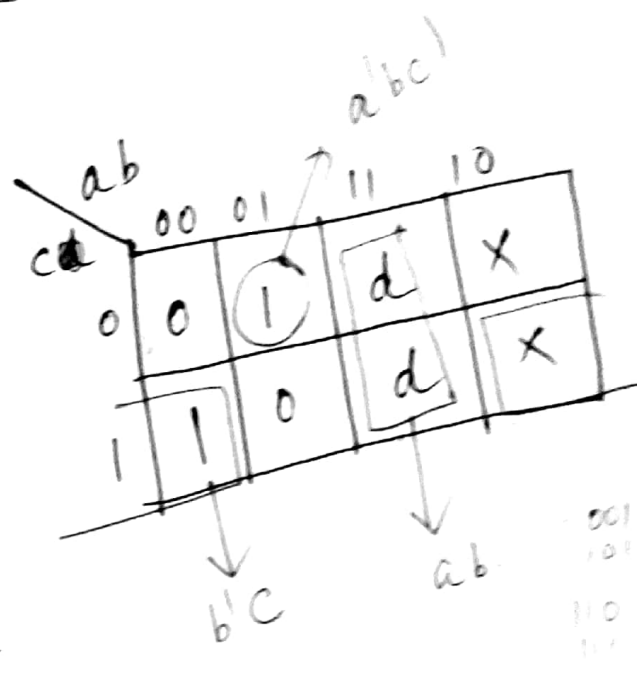

$Y = b'c + abd + a'bc'$

K-map

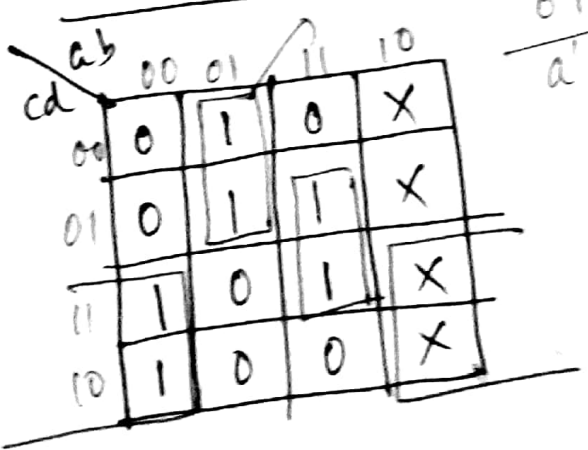


$$\begin{array}{r} 0100 \\ 0101 \\ \hline a'bc' \end{array}$$

$$\begin{array}{r} 0011 \\ 0010 \\ 1011 \\ 1010 \\ \hline bc \end{array}$$


Verified

(i)

$$F_1(A, B, C) = \sum M(0, 1, 2, 5)$$

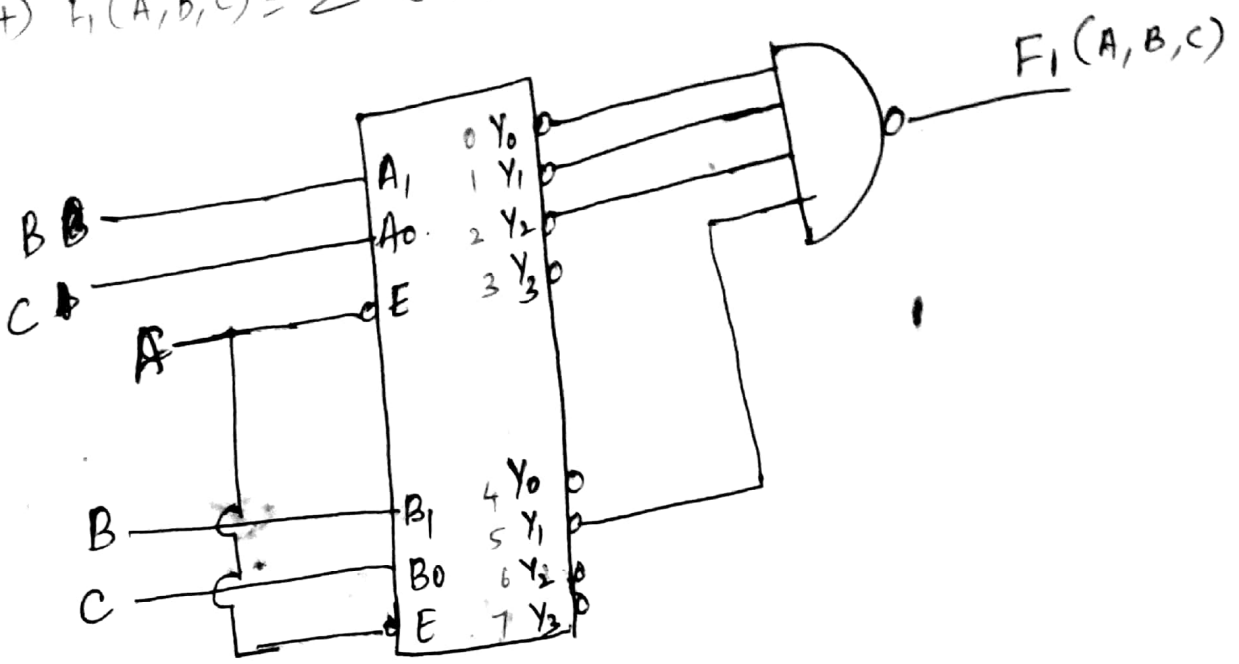

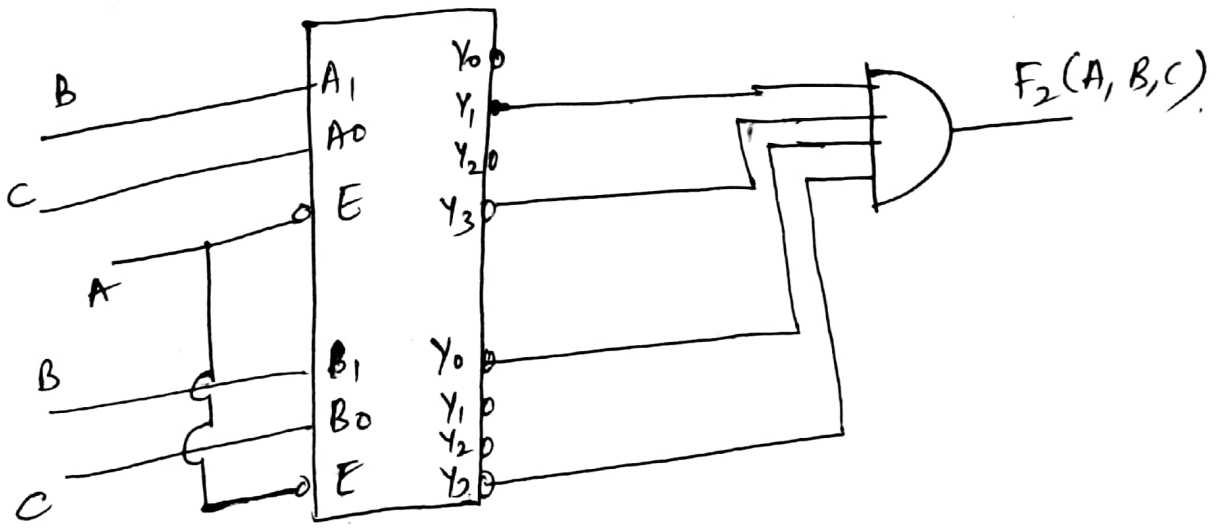(ii)
$$F_2(A, B, C) = \prod M(1, 3, 4, 7)$$




⑤

A	B	C	X	Y
0	0	0	0	0
0	0	1	1	1
0	1	0	1	0
0	1	1	1	0
1	0	0	0	1
1	0	1	0	1
1	1	0	0	1
1	1	1	0	1

$$X = \sum m(1, 2, 3)$$


$$Y = \sum m(1, 4, 5, 6, 7)$$

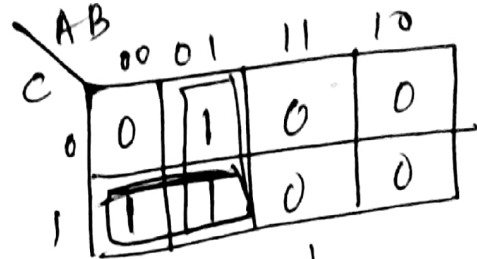

$$\begin{array}{r} 001 \\ 011 \\ \hline A'C \end{array}$$

$$\begin{array}{r} 110 \\ 100 \\ 111 \\ 101 \end{array}$$
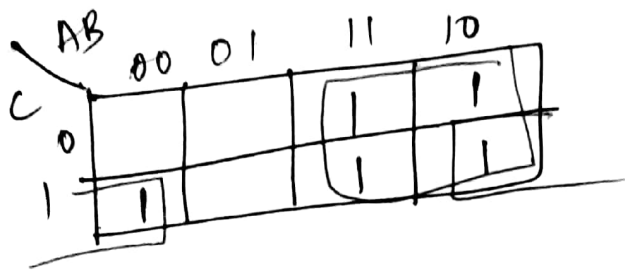
$$\begin{array}{r} 001 \\ 101 \\ \hline B'C \end{array}$$





$$A + B'C$$


circuit

⑥ $Y = f(W, X, Y, Z) = \sum (0, 1, 5, 6, 7, 10, 15)$

- (i) 16:1 (ii) 8:1 (iii) 4:1

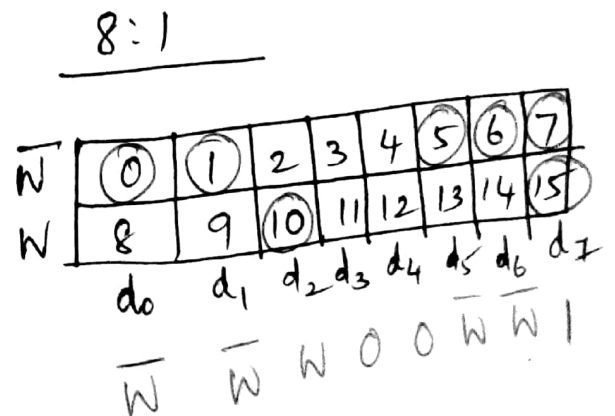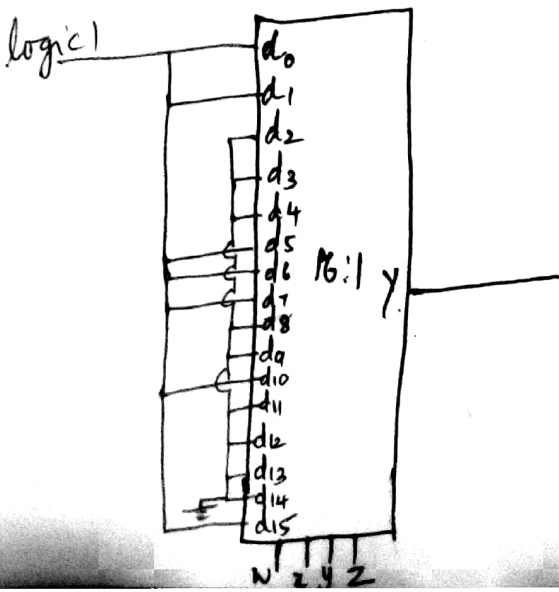

8:1

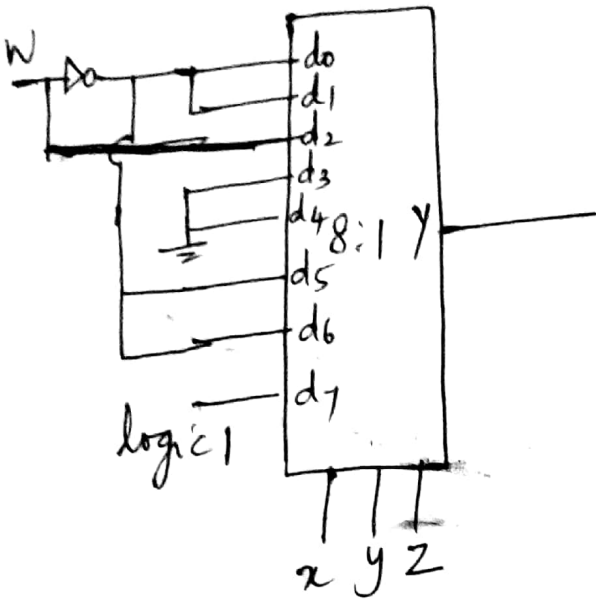

4:1

	d_0	d_1	d_2	d_3
$w'x'$	0	1	2	3
$w'x$	4	5	6	7
wx'	8	9	10	11
wx	12	13	14	15
		$w'x'$		

$$d_1 \rightarrow w'x' + w'x = w'(x' + x)$$

$$d_2 = w'x + wx'$$

$$d_3 = w'x + wx = x(w + w') = x$$

