
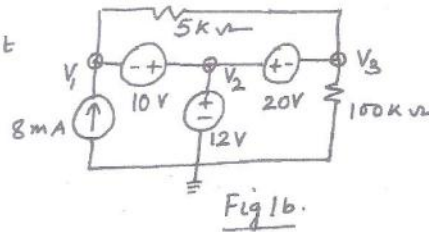


Internal Assessment Test - I

Sub:	ELECTRIC CIRCUIT ANALYSIS				Code:	15EE32	
Date:	18/09/2017	Duration:	90 mins	Max Marks:	50	Sem:	III
Note: Answer any FIVE questions. Sketch figures as necessary. Each Question is for 10 marks.(5x10=50M)				Branch:	EEE		


- 1 (a) Calculate i_o using mesh analysis in the circuit shown in fig1a.
 (b) Find node voltages V_1, V_2, V_3 in the circuit shown in fig1b.

Marks	OBE	
	CO	RBT
[07]	CO1	L2
[03]	CO1	L3

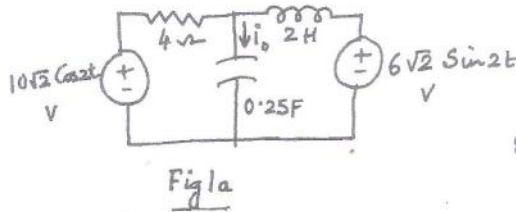




- 2 (a) Using node and supernode method find power delivered by 20V source in the network shown in fig2a.
 (b) Obtain the equivalent resistance R_{ab} for the circuit shown in fig2b.

[06]	CO4	L2
[04]	CO4	L2

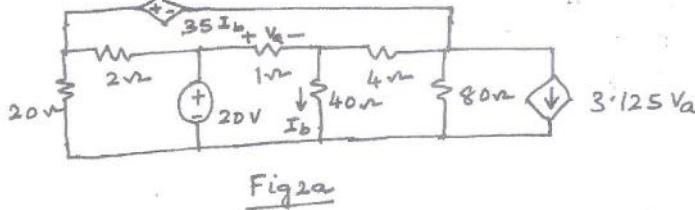

- 3 (a) Using mesh and supermesh analysis, calculate I_x shown in fig3a.
 (b) Using source shifting and source transformation method, determine the voltage V shown in fig3b.

[04]	CO3	L2
[06]	CO4	L5

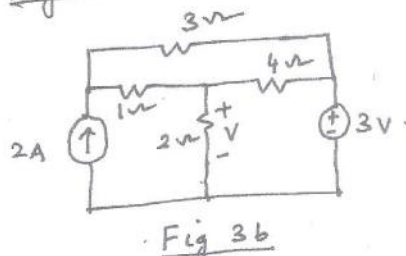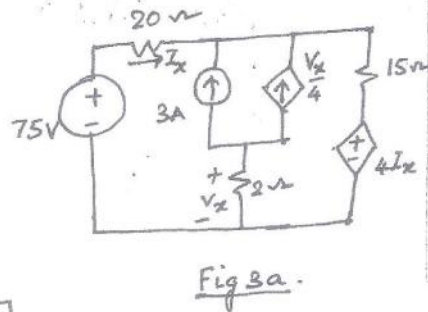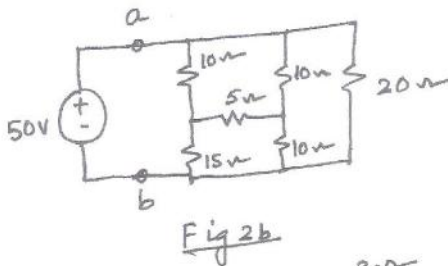

- 4 (a) Referring the network shown in fig4a, find the power delivered by the dependent voltage source in the network. [05]

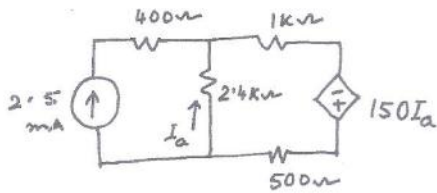


Fig 4a

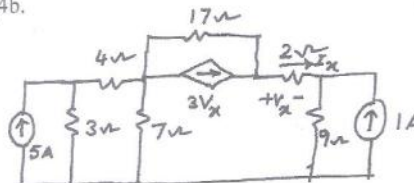


Fig 4b.

- 5 (a) Obtain expression to convert delta connected impedances into equivalent star connected impedances. [05]

- (b) Find the equivalent resistance R_{ab} for the fig5b. [05]

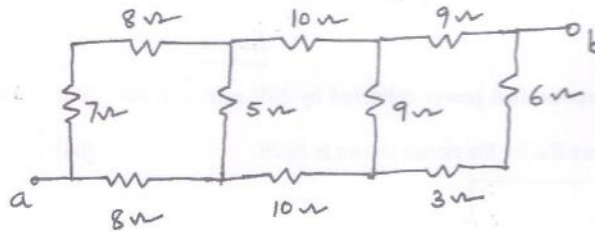


Fig 5b

6. For the network shown in fig6, write mesh equations for the meshes indicated in time domain. Draw dual network and write it's node equations. [10]

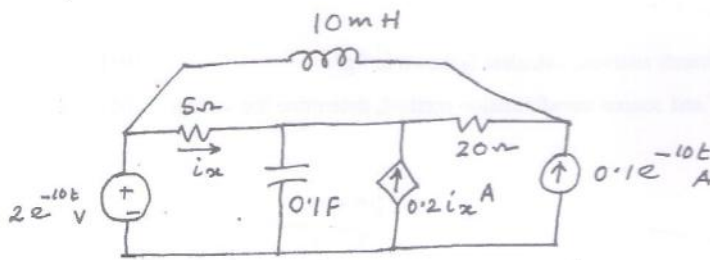


Fig 6

[05]	CO4	L4
[05]	CO2	L1
[05]	CO1	L3
[05]	CO4	L3
[10]	CO4	L4

- end -


Tain
C.C.R / 13/07/17

Solution of IAT-1.

Subject - Electric Circuit Analysis.

Sub-Code - 15EE32.

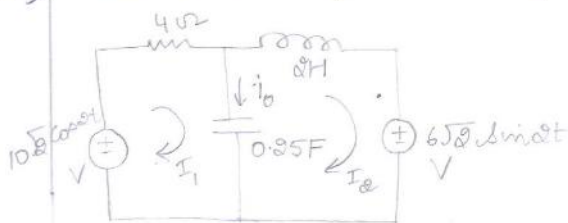1a) Calculate I_0 using mesh analysis in the circuit shown in fig



Applying KVL to the first mesh

$$10\sqrt{2} \angle 0^\circ - I_1 \cdot 4 - (-2j)(I_1 - I_2) = 0$$

$$4I_1 - (2j)I_1 + 2jI_2 = 10\sqrt{2} \angle 0^\circ$$

$$I_1(4 - 2j) + 2jI_2 = 10\sqrt{2} \angle 0^\circ \quad \text{--- (1)}$$

KVL to mesh 2

$$-6 \angle 0^\circ - (2j)(I_2 - I_1) - (4j)I_2 = 0$$

$$(-2j)(I_2 - I_1) + (4j)I_2 = 6 \angle 0^\circ$$

$$2jI_1 + jI_2 - 2jI_2 = 6 \angle 0^\circ$$

$$2jI_1 + 2jI_2 = 6 \angle 0^\circ \quad \text{--- (2)}$$

$$\begin{bmatrix} 4-2j & 2j \\ 2j & 2j \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 10\sqrt{2} \angle 0^\circ \\ 6 \angle 0^\circ \end{bmatrix}$$

$$I_1 = \frac{\begin{bmatrix} 10\sqrt{2} \angle 0^\circ & 2j \\ 6 \angle 0^\circ & 2j \end{bmatrix}}{\Delta} =$$

Δ

$$I_1 = 1.01 + j 1.01$$

$$I_2 = -1.01 - j 4.01$$

$$I_0 = I_1 - I_2 = 2.02 + j 5.01$$

$$\omega = 2$$

$$2\pi f = 2$$

$$f = \frac{2}{2\pi} = 0.3184$$

$$-jX_C = j \frac{1}{2\pi f C} = j$$

$$= 2j$$

$$jX_L = j(2\pi f L)$$

$$j(2 \times \pi \times 0.3184 \times 2)$$

$$= 4j$$


$$\Delta = \begin{vmatrix} 4-2j & 2j \\ 2j & 2j \end{vmatrix}$$

$$= 8j - 4j^2 - 4j^2$$

$$= 8j - 8j^2 = 8 + 8j$$


2/8

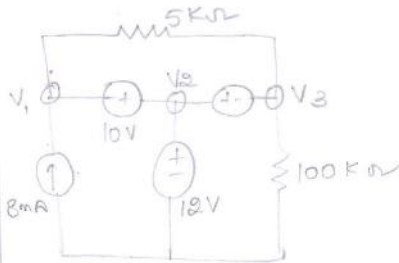b) Find node voltages V_1, V_2, V_3 in the circuit shown



$$\begin{aligned} V_2 &= 12V \\ V_2 - V_3 &= 20 \\ V_3 &= -8V \\ V_2 - V_1 &= 10V \\ V_1 &= 2V \end{aligned}$$

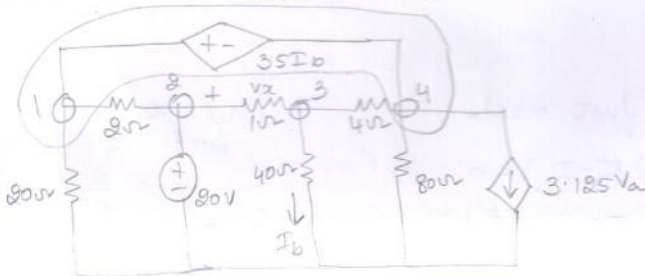a) Using node & supernode method find power delivered by 20V source in the network shown.



Constraint eqⁿ at Supernode

$$V_1 - V_4 = 35I_b = 35 \times \frac{V_3}{40} \quad \text{--- (1)}$$

$$V_2 = 20 \quad \text{--- (2)}$$

At supernode KCL

$$-I_1 - I_2 + I_4 - I_5 - 3.125V_a = 0$$

$$V_a = V_2 - V_3$$

$$-\frac{V_1 - 0}{20} - \frac{V_1 - V_2}{2} + \frac{V_3 - V_4}{4} - \frac{V_4 - 0}{80} - 3.125(V_2 - V_3) = 0 \quad \text{--- (3)}$$

At node 3 KCL

$$I_3 - I_b - I_4 = 0$$

$$\frac{V_2 - V_3}{40} - \frac{V_3 - 0}{40} - \left(\frac{V_3 - V_4}{4} \right) = 0 \quad \text{--- (4)}$$

$$V_1 - V_4 = 0.875V_3 \quad \text{--- (1)}$$

$$V_2 = 20V$$

$$-4V_1 - 40V_1 + 40V_2 + \frac{20V_3 - 20V_4 - V_4 - 250(V_2 - V_3)}{80} = 0$$

$$-44V_1 - 210V_2 + 270V_3 - 21V_4 = 0$$

$$-44V_1 - 4200 + 270V_3 - 21V_4 = 0 \quad \text{--- (2)}$$

$$40V_2 - 40V_3 - \frac{V_3 - 10V_3}{40} - 10V_3 + 10V_4 = 0$$

$$800 - 51V_3 + 10V_4 = 0 \quad \text{--- (5)}$$

$$V_1 = -20.25 \text{ V}$$

$$V_2 = 20 \text{ V}$$

$$V_3 = 10 \text{ V}$$

$$V_4 = -29 \text{ V}$$

$$I_2 = \frac{V_1 - V_2}{2} = \frac{-20.5 - 20}{2} = -20.25 \text{ A}$$

$$I_3 = \frac{V_2 - V_3}{1} = \frac{20 - 10}{1} = 10 \text{ A}$$

At node 2, KCL


$$I_2 - I - I_3 = 0$$

$$I = I_2 + I_3$$

$$I = -30.25 \text{ A}$$

$$P = 80 \times 30.25 = 605 \text{ W}$$

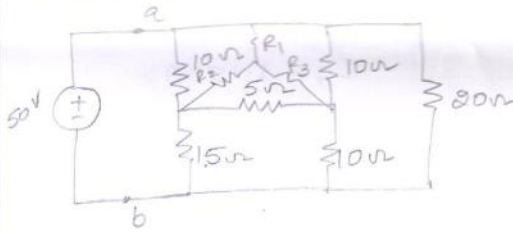b) Obtain the equivalent resistance R_{ab} for the circuit







$$R_1 = \frac{10 \times 10}{10 + 5 + 10} = 4 \Omega$$

$$R_2 = \frac{10 \times 5}{10 + 5 + 10} = 2 \Omega$$


$$R_3 = \frac{5 \times 10}{10 + 5 + 10} = 2 \Omega$$

$$R_{AB} = 7.10 \Omega$$

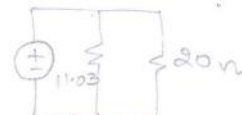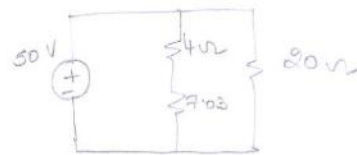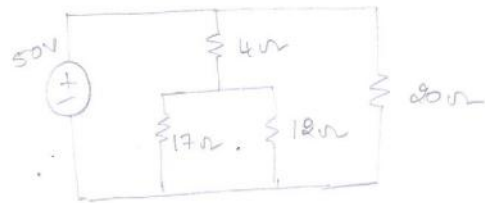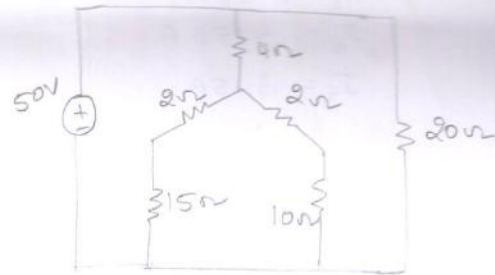

4/8

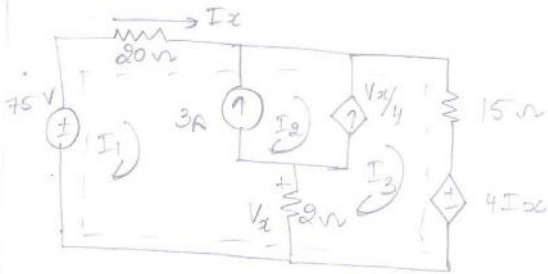3a) Using mesh and supermesh analysis calculate I_x



$$I_2 - I_1 = 3 \quad \text{--- (1)}$$

$$I_3 - I_2 = \frac{V_x}{4} = \frac{1}{2}(I_1 - I_3) \quad \text{--- (2)}$$

$$V_x = 2(I_1 - I_3)$$

$$I_x = I_1$$

$$2I_3 - 2I_2 = I_1 - I_3$$

$$3I_3 - 2I_2 - I_1 = 0$$

$$75 - 20I_1 - 15I_3 - 4I_1 = 0$$

$$75 - 24I_1 - 15I_3 = 0$$

$$I_1 = 1.153 \text{ A}$$

$$I_2 = 4.153 \text{ A}$$







$$I_3 = 3.15 \text{ A}$$

$$V_x = 2(1.153 - 3.15)$$

$$= -3.994 \text{ V}$$


$$I_x = 1.153 \text{ A}$$

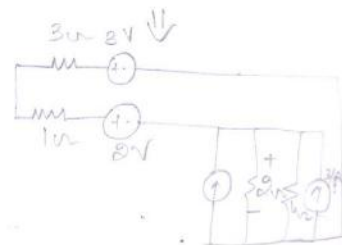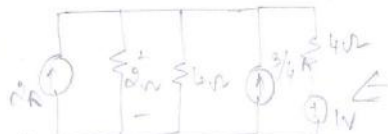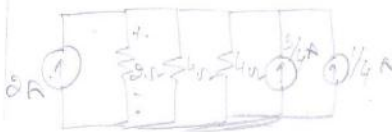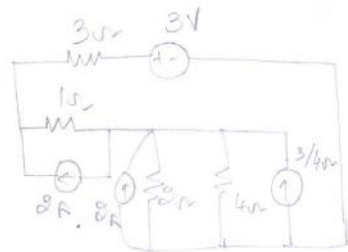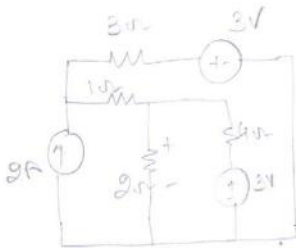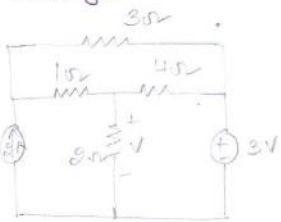b) Using source shifting & source transformation, determine the voltage.



Voltage $V = 3\text{V}$

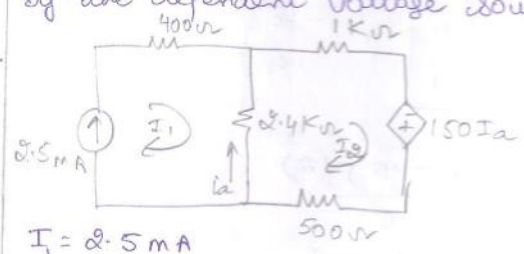4a) Referring the network shown in fig 4a find the power delivered by the dependent voltage source in the network



$I_1 = 2.5 \text{ mA}$

Applying KVL to mesh

$$-(1K)I_2 + (150I_a) - 500(I_2) - (2.4K)(I_2 - I_1) = 0$$

$$1KI_2 - 500I_2 - (2.4K)I_2 + 150I_a + (2.4K)I_1 = 0$$

$$-1.9KI_2 + 2.4K(2.5 \text{ mA}) + 150I_a = 0$$

$$-1.9KI_2 + 150I_a = 6$$

$$150I_a - (1.9K)I_2 = 6 \quad \text{--- (1)}$$

$I_a = I_2 - I_1$

$I_a - I_2 = -I_1$

$I_2 - I_a = 2.5 \text{ mA} \quad \text{--- (2)}$





$I_a = -6.4 \text{ mA}$

$I_2 = -3.64 \text{ mA}$




$V = 150(I_a) = 150(-6.4 \text{ mA}) = -0.981 \text{ V}$

$P = VI = 3.35 \text{ mW}$

b) Find V_x , I_x in the circuit diagram

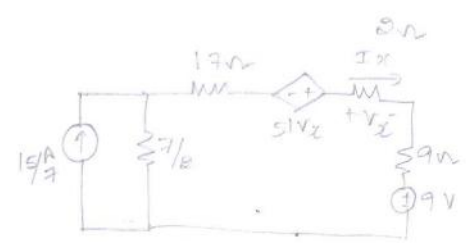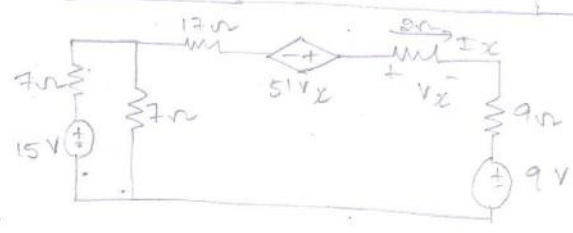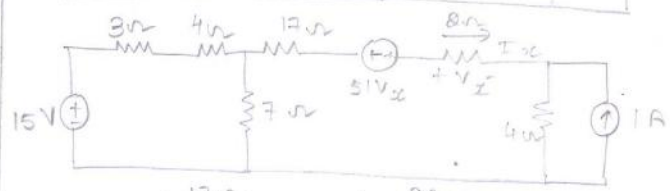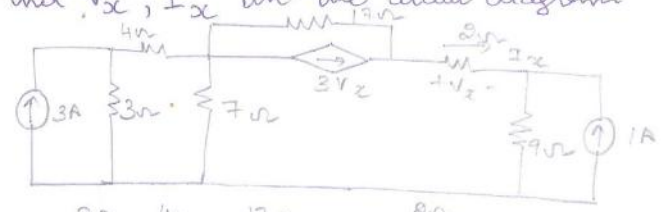

6/8

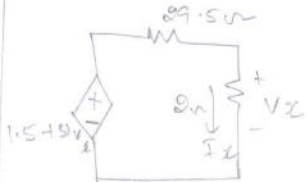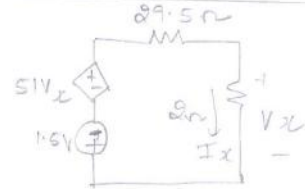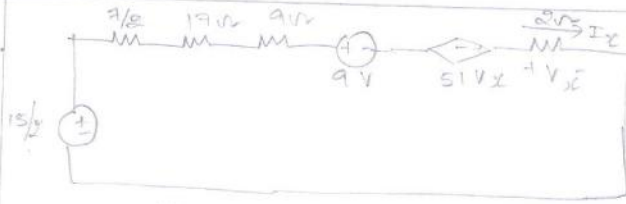

$$V_x = \frac{(5I_x - 1.5)}{31.5} \quad (2)$$



$$31.5V_x = 102V_x - 3$$

$$31.5V_x - 102V_x = -3$$

$$V_x = 0.0425V$$

$$I_x = 21.1\mu A$$

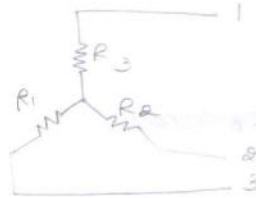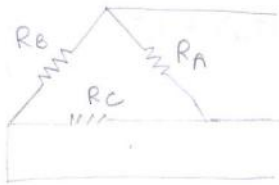5 a) Obtain experience to convert delta connected impedances into equivalent star connected impedances.



The resistance across 1 & 2

$$R_{12} = R_A \parallel (R_B + R_C)$$

$$R_{12} = \frac{R_A (R_B + R_C)}{R_A + R_B + R_C}$$

$$R_{12} = \frac{R_A (R_B + R_C)}{R_A + R_B + R_C}$$

$$R_{12} = R_3 + R_2$$

$$R_3 + R_2 = \frac{R_A (R_B + R_C)}{R_A + R_B + R_C} \quad (1)$$

The resistance 2 & 3

$$R_{23} = R_C \parallel (R_A + R_B)$$

$$R_{23} = \frac{R_C (R_A + R_B)}{R_A + R_B + R_C}$$

$$R_{23} = \frac{R_C (R_A + R_B)}{R_A + R_B + R_C}$$

$$R_1 + R_2 = \frac{R_C R_A + R_C R_B}{R_A + R_B + R_C} \quad (2)$$

The resistance across 3 & 1

$$R_{31} = R_B \parallel (R_A + R_C)$$

$$R_{31} = \frac{R_B (R_A + R_C)}{R_A + R_B + R_C}$$

$$R_{31} = \frac{R_B (R_A + R_C)}{R_A + R_B + R_C}$$

$$R_{31} = R_1 + R_3$$

$$R_1 + R_3 = \frac{R_A R_B + R_B R_C}{R_A + R_B + R_C} \quad (3)$$

Subtract (3) from (1)

$$R_3 + R_2 - R_1 - R_3 = \frac{R_A R_B + R_A R_C - R_A R_B - R_B R_C}{R_A + R_B + R_C}$$



$$R_2 - R_1 = \frac{R_A R_C - R_B R_C}{R_A + R_B + R_C} \quad (4)$$

Adding (4) to (2)


$$2R_2 = \frac{2R_A R_C}{\Sigma R}$$

$$R_2 = \frac{R_A R_C}{\Sigma R} \quad R_1 = \frac{R_B R_C}{\Sigma R} \quad R_3 = \frac{R_A R_B}{\Sigma R}$$

b) Find the equivalent resistance R_{AB}

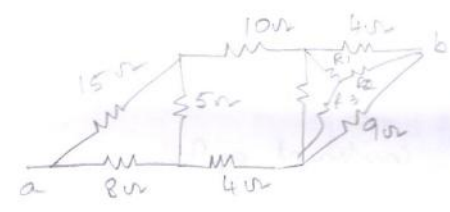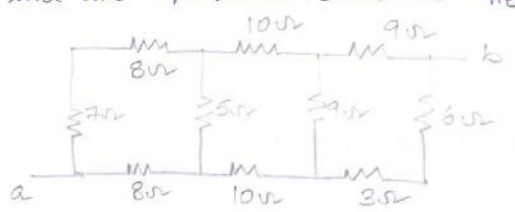

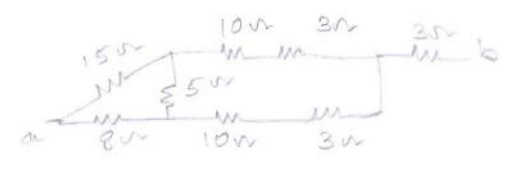
$$R_1 = R_2 = R_3 = \frac{9 \times 9}{9 + 9 + 9} = 3\Omega$$





$$R_A = \frac{15 \times 5}{8 + 15 + 5} = 2.67\Omega$$

$$R_C = 4.18\Omega$$

$$R_B = 1.428\Omega$$


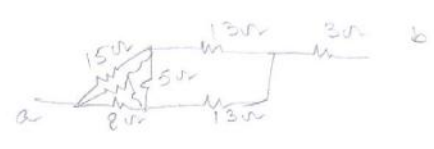


$$R_{AB} = 14.19\Omega$$

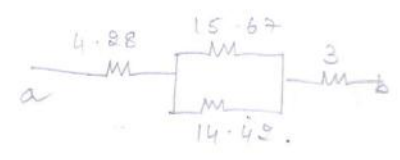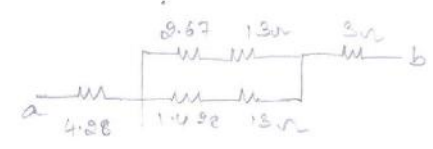

8/8

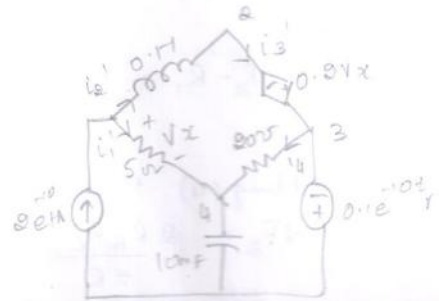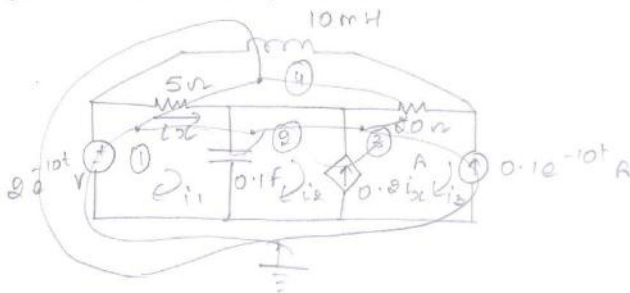6) For the network shown, write mesh equation for the mesh indicated in time domain.



KVL mesh 1

$$2e^{-10t} - 5(i_1 - i_4) - \frac{1}{0.1} \int (i_1 - i_2) dt = 0$$

$$2e^{-10t} - 5V_1 - \frac{1}{0.1} \int (V_1 - V_2) dt = 0$$

At node 1, KCL

$$2e^{-10t} - i_1' - i_2' = 0$$

$$2e^{-10t} - 5(V_1 - V_4) - \frac{1}{0.1} \int (V_1 - V_2) dt = 0$$

Constraint eqn

$$i_3 - i_2 = 0.2i_2 = 0.2(i_1 - i_4) \quad \text{--- (3)}$$

$$i_3 = -0.1e^{-10t} \quad \text{--- (4)}$$

KVL, mesh 4

$$-10 \times 10^{-3} \frac{di_4}{dt} - 20(i_4 - i_3) - 5(i_4 - i_1) = 0$$

KCL at node 1

$$2e^{-10t} - i_1' - i_2' = 0$$

$$2e^{-10t} - 5(V_1 - V_4) - \frac{1}{0.1} \int (V_1 - V_2) dt = 0$$

$$(V_3 - V_2) = 0.2(V_1 - V_4) \quad / \quad i_2 = i_1 - i_4$$

$$V_3 = -0.1e^{-10t} \text{ volts} \quad V_x = V_1 - V_4$$

At node 4; KCL

$$i_1' + i_4' - i_5' = 0$$

$$5(V_1 - V_4) + 20(V_4 - V_3) - 10 \times 10^{-3} \frac{dV_4}{dt} = 0$$