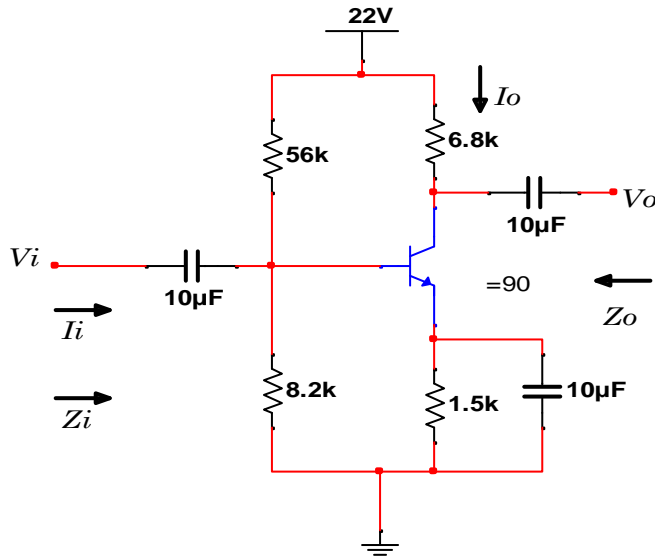


Internal Assessment Test - I

Sub:	Analog Electronics	Code:	15EC32
Date:	18 / 09 / 2017	Duration:	90 mins
		Max Marks:	50
		Sem:	3rd
		Branch:	ECE (C)
Answer Any FIVE FULL Questions			

- 1 (a) Analyze the Common base configuration with a circuit diagram.
(b) Obtain Z_i , Z_o , A_v and A_i for CB configuration using h-parameters.
- 2 Apply the complete hybrid equivalent model, to determine the input impedance, output impedance, voltage gain and current gain of transistor amplifier in terms of h-parameters.
- 3 Explain the BJT amplifier transistor modeling in detail.
- 4 Draw the emitter follower configuration. Derive its input impedance, output impedance, voltage gain and current gain using h-parameters.
- 5 Explain the Darlington Connection with a neat diagram. Analyze the Darlington connection DC bias condition using emitter follower configuration.
- 6 For the network shown in the figure, calculate r_e , Z_i , Z_o ($r_o = \infty$) and A_v ($r_o = \infty$).

Marks	OBE	
	CO	RBT
[05]	CO1	L4
[05]	CO1	L4
[10]	CO1	L3
[10]	CO1	L4
[10]	CO1	L3
[10]	CO1	L4




[10]	CO1	L3
------	-----	----

IAT-1 (Analog Electronics)


Solutions

1)

(a) Common-Base Configuration:

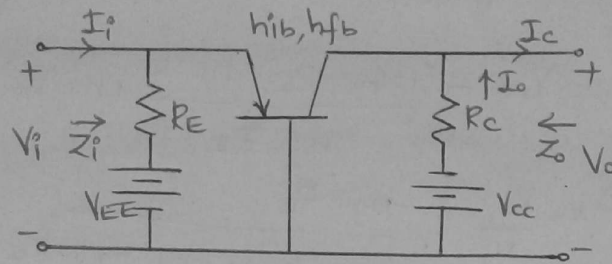

(b) CB configuration using h-parameters:

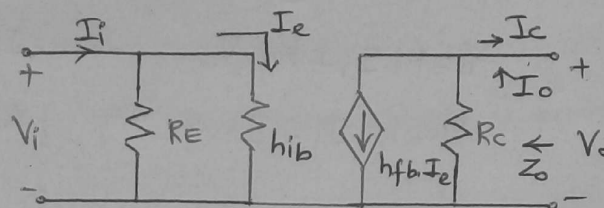


Input impedance, $Z_i = R_E \parallel h_{ib}$

Output impedance, $Z_o = R_C \parallel 1/h_{ob} \approx R_C$

Voltage gain, $A_v = \frac{V_o}{V_i} = -\frac{R_C \cdot h_{fb}}{h_{ib}}$

Current gain, $A_i = \frac{I_o}{I_i} = -h_{fb} = -1$

2) Complete Hybrid Equivalent Model:

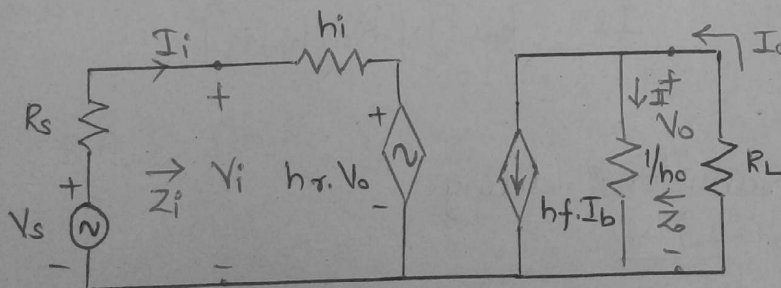

current gain, $A_i = \frac{I_o}{I_i}$ Apply KCL to the output

$$I_o = h_f \cdot I_b + I$$

$$I_o = h_f \cdot I_b - h_o \cdot I_o \cdot R_L$$

$$A_i = \frac{I_o}{I_i} = \frac{h_{fe}}{1 + h_o \cdot R_L}$$

Voltage gain, $A_v = \frac{V_o}{V_i}$

$$V_i = h_i I_i + h_r V_o$$

$$I_i = (1 + h_o R_L) / I_o h_f, I_o = -V_o / R_L$$

$$V_i = - \frac{(1 + h_o R_L) \cdot h_i \cdot V_o}{h_f R_L} + h_r V_o$$

$$A_v = \frac{V_o}{V_i} = \frac{-h_f R_L}{h_i + (h_i h_o - h_f h_r) R_L}$$

Input impedance, $Z_i = \frac{V_i}{I_i}$

$$V_i = h_i I_i + h_r V_o \quad V_o = -I_o R_L$$

$$V_i = h_i I_i - I_o R_L h_r \quad A_i = \frac{I_o}{I_i}$$

$$V_i = h_i I_i - A_i I_i h_r R_L$$

$$Z_i = \frac{V_i}{I_i} = \frac{h_i - h_f h_r R_L}{1 + h_o R_L}$$


Output impedance, $Z_o = \frac{V_o}{I_o}$

when $V_s = 0$, $I_i = \frac{-h_r V_o}{R_s + h_i}$

$$I_o = h_f I_i + h_o V_o$$

$$Z_o = \frac{V_o}{I_o} = \frac{1}{h_o - [h_f h_r / (h_i + R_s)]}$$

3. BJT Amplifier Transistor Modeling:


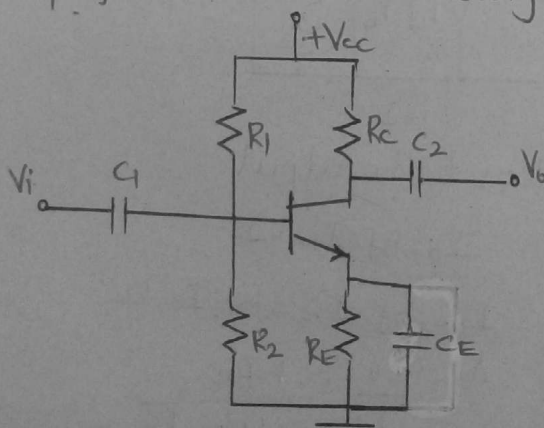


- Modeling - approximates the actual behavior of semiconductor.
- 3 types
- (1) hybrid equivalent - approximation based on datasheet.
 - (2) r_e model - actual operating conditions.
 - (3) hybrid pi model - feedback effect.

- The ac equivalent of a transistor network

- (1) setting all dc sources to zero
- (2) Replacing all capacitors by a short circuit.
- (3) Redraw the network.

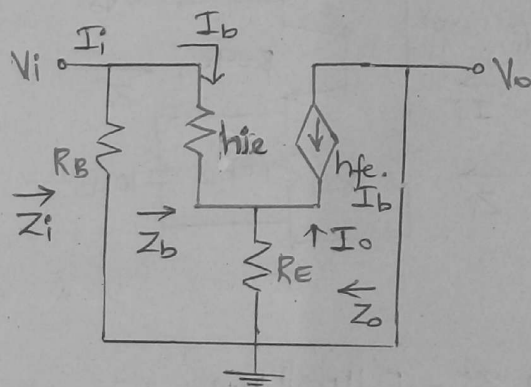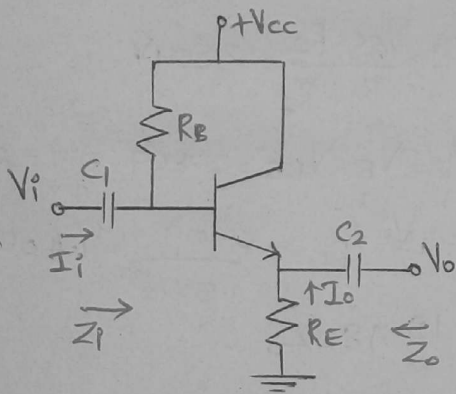4) Emitter-follower Configuration using h-parameters




Input impedance, $Z_i = R_B \parallel Z_b$ $Z_b = h_{ie} + h_{fe} \cdot R_E$
 $Z_b \approx h_{fe} \cdot R_E$


Output impedance, $Z_o = R_E \parallel h_{ie}/h_{fe}$

Voltage Gain, $A_v = \frac{V_o}{V_i} = \frac{R_E}{r_e + R_E}$

Current Gain, $A_i = \frac{I_o}{I_i} = h_{fe} \cdot \frac{R_B}{R_B + Z_b}$

5) Darlington Connection:

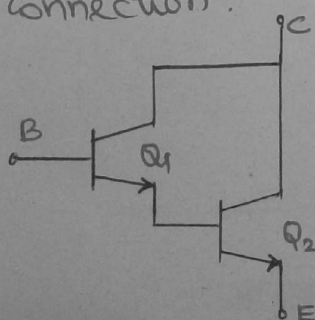

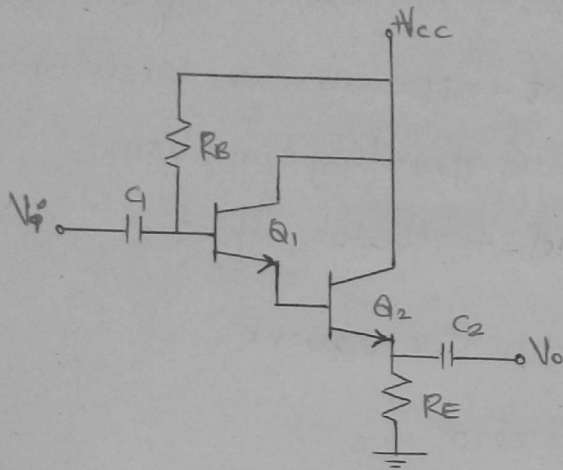

$$V_{CC} - I_{B1} \cdot R_B - V_{BE1} - V_{BE2} - I_{E2} \cdot R_E = 0$$

$$I_{E1} = \beta_1 \cdot I_{B1} = I_{B2}$$


$$I_{E2} = \beta_2 \cdot I_{B2} = \beta_2 \cdot \beta_1 \cdot I_{B1} = \beta_D \cdot I_{B1}$$

$$V_{CC} - V_{BE1} - V_{BE2} = I_{B1} [R_B + \beta_D \cdot R_E]$$

$$I_{B1} = \frac{V_{CC} - V_{BE1} - V_{BE2}}{R_B + \beta_D \cdot R_E}$$

$$V_{CE2} = V_{CC} - I_{E2} \cdot R_E$$

6) Solution:

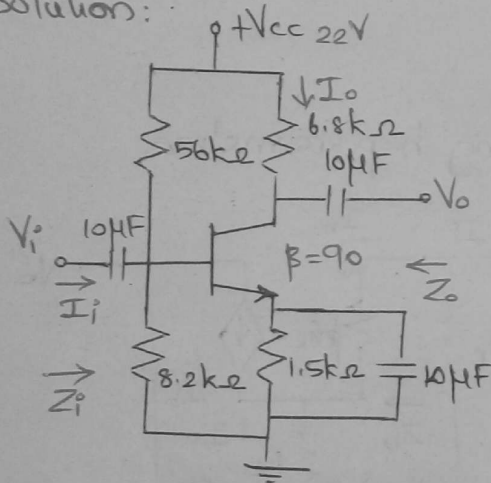

$$a) r_e = \frac{26mV}{I_E}$$

$$V_B = \frac{V_{CC} \cdot R_2}{R_1 + R_2} = 2.809V$$

$$V_E = V_B - V_{BE} = 2.809 - 0.7 = 2.109V$$

$$I_E = \frac{V_E}{R_E} = \frac{2.109}{1.5 \times 10^3} = 1.406mA$$

$$r_e = 18.48 \Omega$$

$$b) Z_i = R_1 \parallel R_2 \parallel \beta r_e = 1.349k\Omega$$

$$\beta r_e = 1663.53$$

$$c) Z_o = R_c = 6.8k\Omega$$

$$d) A_v = \frac{V_o}{V_i} = -\frac{R_c}{r_e} = -\frac{6.8k\Omega}{18.48} = -366.972$$