

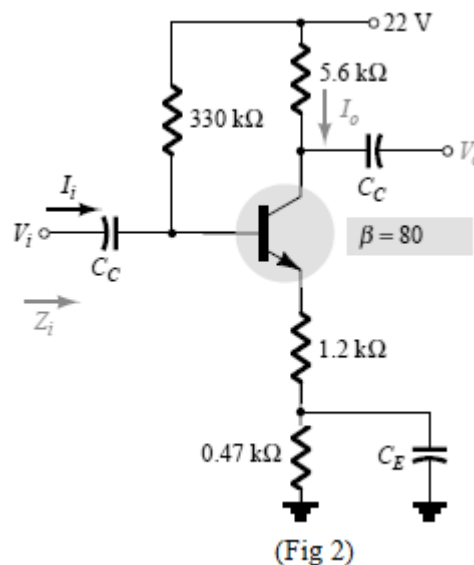


Internal Assessment Test – I


Sub:	ANALOG ELECTRONICS					Code:	15EC32
Date:	18/09/2017	Duration:	90 mins	Max Marks:	50	Sem:	III
Answer Any FIVE FULL Questions						Branch:	TCE (A)

		Marks	OBE	
			CO	RBT
1	Derive an expression for input impedance, output impedance, voltage gain and current gain of transistor amplifier using complete hybrid-Model.	[10]	CO1	L2
2	Calculate the following for the network shown in (Fig 1) with and without C_E and compare the voltage gain. (a) r_e (b) Z_i (c) Z_o (d) A_V (e) A_i	[10]	CO1	L3
3	For the network shown in (Fig 2). Determine r_e, Z_i, Z_o, A_V, A_i	[10]	CO1	L3
4 (a)	Calculate the DC bias voltages and Currents for the given circuit (Fig 3).	[05]	CO1	L3
(b)	Draw and explain the hybrid- π model of transistor in CE configuration mentioning significance of each component in Model.	[05]	CO2	L5
5	Calculate the input impedance, output impedance, voltage gain and current gain for the given circuit (Fig 4).	[10]	CO1	L3
6 (a)	Determine the input impedance, output impedance, voltage gain and current gain for the circuit shown below (Fig 5).	[05]	CO1	L3
(b)	Analyze the r_e parameter model for emitter follower circuit and derive Z_i, Z_o, A_V, A_i	[05]	CO1	L4
7 (a)	Describe the h-parameter model for emitter bias circuit and derive Z_i, Z_o, A_V, A_i using approximate hybrid model.	[05]	CO1	L2
(b)	For the network shown below(Fig 6), determine V_{CC} for a voltage gain of $A_V = -180$	[05]	CO1	L3

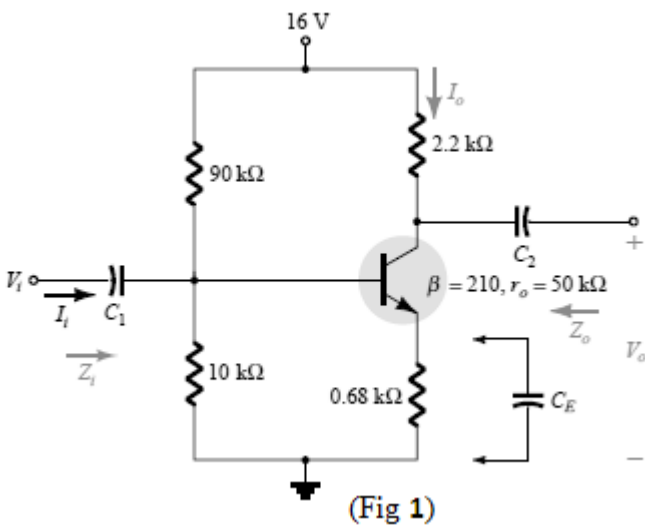


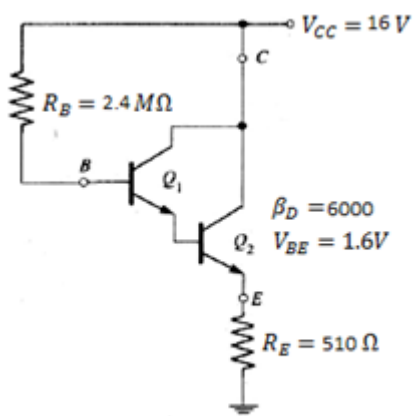


(Fig 3)

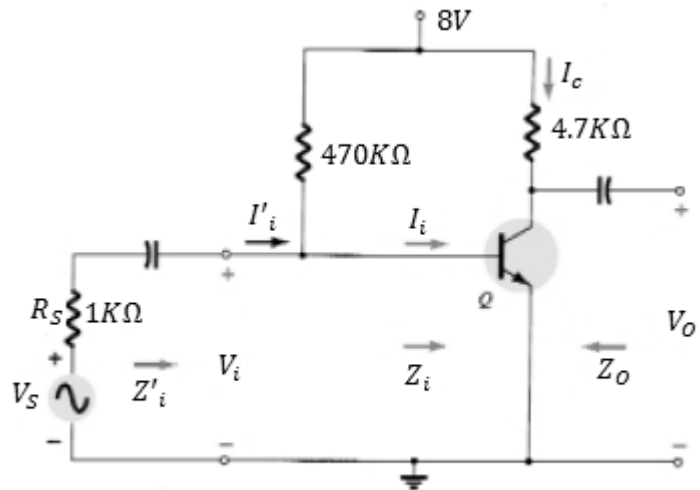

$h_{fe} = 110$ $h_{ie} = 1.6K\Omega$ $h_{re} = 2 \times 10^{-4}$ $h_{oe} = 20 \frac{\mu A}{V}$
(Fig 4)

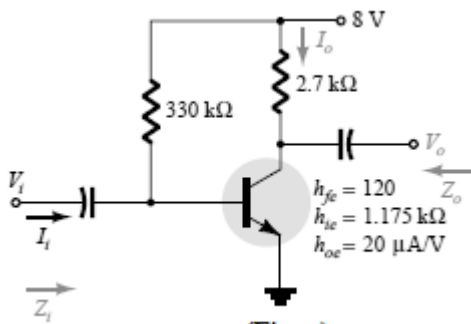

(Fig 5)

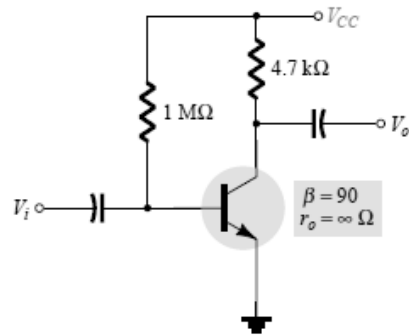


(Fig 6)

SOLUTION AND SCHEME OF EVALUATION

IAT-1: AEC

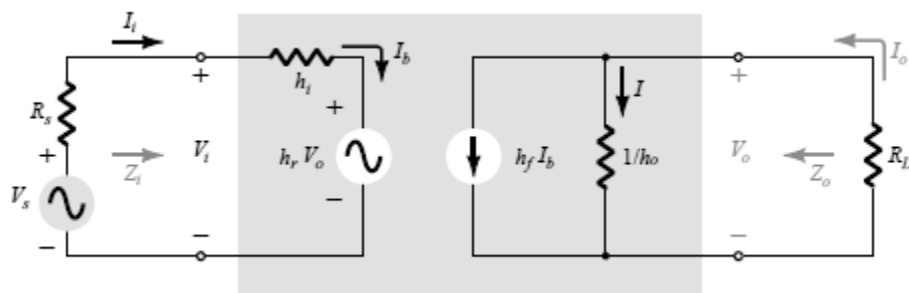1. Derive an expression for input impedance, output impedance, voltage gain and current gain of transistor amplifier using complete hybrid-Model. [10 Marks]

COMPLETE HYBRID EQUIVALENT MODEL: [2 Marks]



Current Gain: [2 Marks]

Applying Kirchoff's current law to the output circuit

$$I_o = h_f I_b + I = h_f I_i + \frac{V_o}{1/h_o} = h_f I_i + h_o V_o \quad \text{as } V_o = -I_o R_L \quad \text{hence } I_o = h_f I_i - h_o I_o R_L$$

$$I_o + h_o I_o R_L = h_f I_i \Rightarrow I_o (1 + h_o R_L) = h_f I_i \Rightarrow A_i = \frac{I_o}{I_i} = \frac{h_f}{1 + h_o R_L}$$

Voltage Gain: [2 Marks]

$$V_i = I_i h_i + V_o h_r \quad \text{as } I_i = \frac{(1 + h_o R_L) I_o}{h_f} \quad \text{and } I_o = \frac{-V_o}{R_L} \Rightarrow V_i = \frac{-(1 + h_o R_L) h_i}{h_f R_L} V_o + V_o h_r$$

$$V_i = \frac{V_o h_r h_f R_L - (1 + h_o R_L) h_i V_o}{h_f R_L} \Rightarrow V_i = \frac{V_o h_r h_f R_L - h_i V_o - h_i V_o h_o R_L}{h_f R_L}$$

$$\Rightarrow V_i = \frac{-V_o [h_i + (h_i h_o - h_r h_f) R_L]}{h_f R_L}$$

$$A_V = \frac{V_o}{V_i} \Rightarrow A_V = \frac{-h_f R_L}{h_i + (h_i h_o - h_r h_f) R_L}$$

Input Impedance: [2 Marks]

$$V_i = I_i h_i + h_r V_o \quad \text{and } V_o = -I_o R_L \quad \text{hence } V_i = I_i h_i - I_o R_L h_r \quad \text{as } I_o = A_i I_i$$

$$V_i = I_i h_i - R_L h_r A_i I_i \quad \text{and } Z_i = \frac{V_i}{I_i} = h_i - R_L h_r A_i \quad \text{as } A_i = \frac{h_f}{1 + h_o R_L} \quad \text{hence } Z_i = h_i - \frac{R_L h_r h_f}{1 + h_o R_L}$$

output Impedance: The output impedance of an amplifier is defined to be the ratio of the output voltage to the output current with the signal V_S set to zero. [2 Marks]


$$V_S - I_i R_S - I_i h_i - h_r V_o = 0 \text{ for calculating } Z_o; V_S \text{ has to be set to zero } \Rightarrow I_i (R_S + h_i) = -h_r V_o$$

$$I_i = \frac{-h_r V_o}{R_S + h_i}$$

$$I_o = h_f I_i + h_o V_o \Rightarrow I_o = \frac{-h_r h_f V_o}{R_S + h_i} + h_o V_o$$

$$Z_o = \frac{V_o}{I_o} = \frac{1}{h_o - \left[\frac{h_r h_f}{(R_S + h_i)} \right]}$$

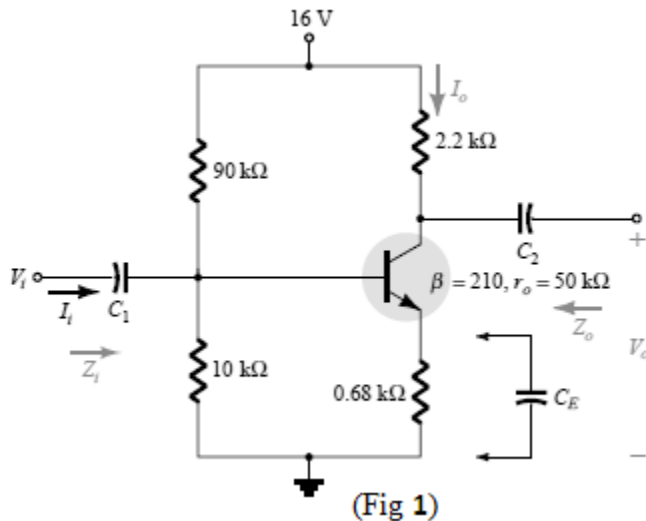
2. Calculate the following for the network shown in (Fig 1) with and without C_E and compare the voltage gain. (a) r_e (b) Z_i (c) Z_o (d) A_V (e) A_i [10 Marks]



ANSWER: (Without C_E)

[5 Marks]
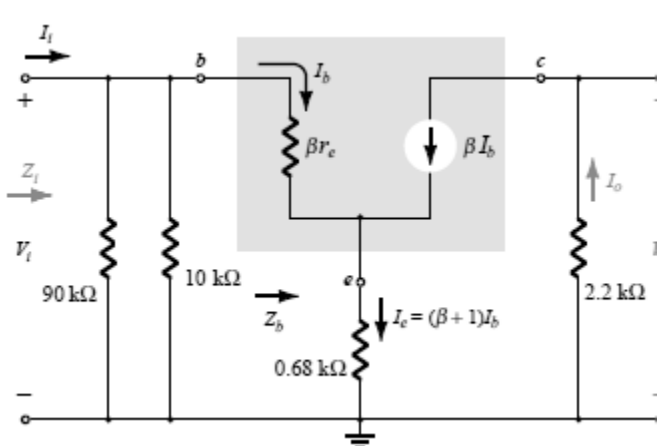
$$\beta R_E \geq 10 R_2 \Rightarrow 210 \times 0.68 \text{K}\Omega \geq 10 \times 10 \text{K}\Omega \Rightarrow 142.8 \text{K}\Omega \geq 100 \text{K}\Omega (\text{Satisfied})$$



$$V_B = \frac{V_{CC} R_2}{R_1 + R_2} = \frac{16 \times 10 \text{K}\Omega}{90 \text{K}\Omega + 10 \text{K}\Omega} = 1.6 \text{V}$$

$$V_E = V_B - V_{BE} = 1.6 - 0.7 = 0.9 \text{V}$$

$$I_E = \frac{V_E}{R_E} = \frac{0.9}{0.68 \text{K}\Omega} = 1.32 \text{mA}$$

$$r_e = \frac{26 \text{mV}}{I_E} = \frac{26 \text{mV}}{1.32 \text{mA}} = 19.69 \Omega$$

$$Z_b = \beta r_e + (\beta + 1)R_E = 210 \times 19.69\Omega + (210 + 1)0.68K\Omega = 147.6K\Omega$$

$$R' = \frac{R_1 R_2}{R_1 + R_2} = \frac{90K\Omega \times 10K\Omega}{90K\Omega + 10K\Omega} = 9K\Omega$$

$$Z_i = R' || Z_b = 9K\Omega || 147.6K\Omega = 8.48K\Omega$$


$$Z_o = R_C = 2.2K\Omega$$

$$A_V = \frac{-R_C}{(R_E + r_e)} = \frac{-2.2K\Omega}{(19.69\Omega + 0.68K\Omega)} = -3.14$$

$$A_i = -A_V \frac{Z_i}{R_C} = 3.14 \times \frac{8.48K\Omega}{2.2K\Omega} = 12.10$$

(With C_E)

[5 Marks]

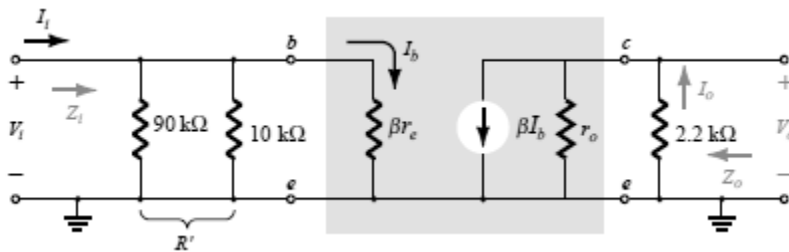

$$R' = \frac{R_1 R_2}{R_1 + R_2} = \frac{90K\Omega \times 10K\Omega}{90K\Omega + 10K\Omega} = 9K\Omega$$

$$A_V = \frac{-R_C}{r_e} = \frac{-2.2K\Omega}{19.69\Omega} = -111.73$$


$$Z_i = R' || \beta r_e = 9K\Omega || 4.135K\Omega = 2.83K\Omega$$

$$A_i = -A_V \frac{Z_i}{R_C} = 111.73 \times \frac{2.83K\Omega}{2.2K\Omega} = 143.72$$

$$Z_o = R_C = 2.2K\Omega$$

3. For the network shown in (Fig 2). Determine r_e, Z_i, Z_o, A_V, A_i

[10 Marks]

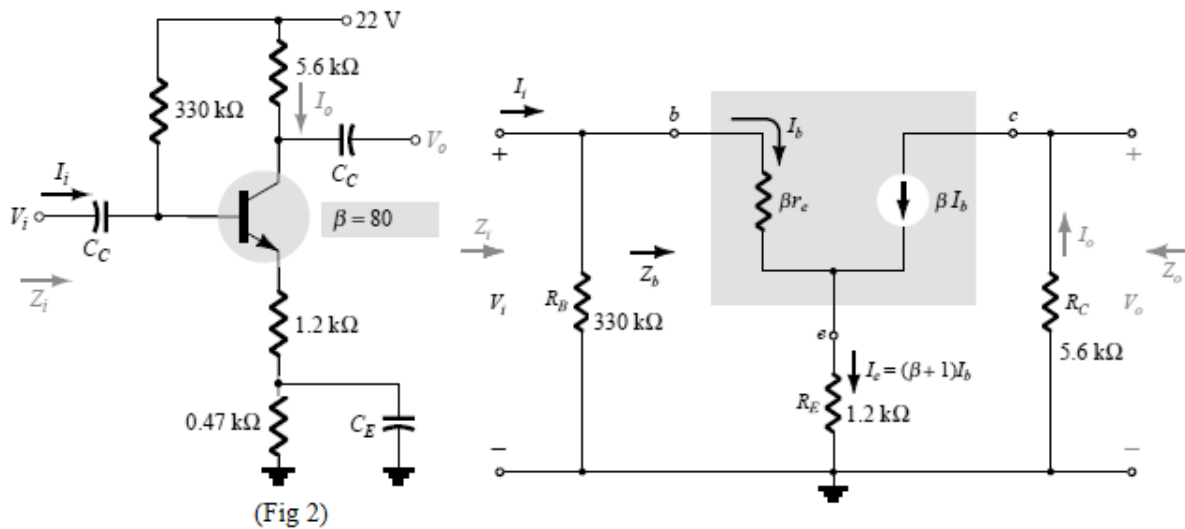

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1)R_E} = \frac{22 - 0.7}{330 \times 10^3 + (80 + 1)(1.2 + 0.47) \times 10^3} = 45.77\mu A$$

$$I_E = (\beta + 1)I_B = (80 + 1)45.77\mu A = 3.708mA$$

$$r_e = \frac{26mV}{I_E} = \frac{26mV}{3.708mA} = 7.01\Omega$$

[2 Marks]

$$Z_b = \beta r_e + (\beta + 1)R_E = (80 \times 7.01\Omega) + (80 + 1)1.2K\Omega = 97.76K\Omega$$

$$Z_i = R_B || Z_b = 330K\Omega || 97.76K\Omega = 75.41K\Omega$$

[2 Marks]

$$Z_o = R_C = 5.6K\Omega$$

[2 Marks]

$$A_V = \frac{-R_C}{(R_E + r_e)} = \frac{-5.6K\Omega}{(1.2K\Omega + 7.01\Omega)} = -4.639$$


[2 Marks]

$$A_i = -A_V \frac{Z_i}{R_C} = 4.639 \times \frac{75.41K\Omega}{5.6K\Omega} = 62.469$$

[2 Marks]

4. (a) Calculate the DC bias voltages and Currents for the given circuit (Fig 3).

[5 Marks]

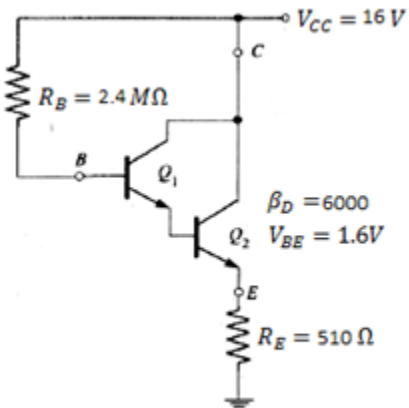

(Fig 3)

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta_D + 1)R_E}$$

[2 Marks]

$$I_B = \frac{16 - 1.6}{2.4 \times 10^6 + (6000 + 1)510} = 2.637\mu A$$

$$I_E = (\beta_D + 1)I_B = (6000 + 1)2.637\mu A = 15.82mA$$


[2 Marks]

$$V_E = I_E R_E = 15.82 \times 10^{-3} \times 510 = 8.0709V$$

[1 Mark]

(b) Draw and explain the hybrid- π model of transistor in CE configuration mentioning significance of each component in Model.

[5 Marks]

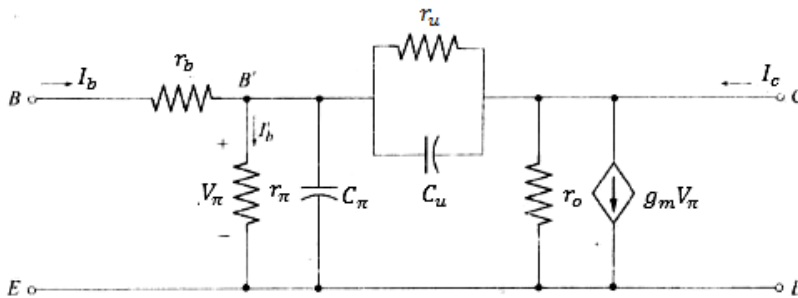

[1 Mark]

HYBRID π MODEL: It is the more accurate model for High frequency effects. For low frequency approximations, the model can be made with the r_e model. [4 Marks]

The capacitors appear in the hybrid π model are stray capacitors. The capacitive effect only come into play at high frequencies. For low and mid frequencies their reactance is very large, and they can be considered open circuit. The capacitance value is in few pico farad(pf) to few tens of pico farad (pf).

r_u, r_π & r_o are the resistance between the indicated terminals of the device, when the device is in the active region.

r_u provides the union, it provides between collector and base terminals.


r_b is usually very small it can be replaced by a short-circuit equivalent.


r_u is usually so large it can be ignored for most applications.

$$r_\pi = \beta r_e \quad g_m = \frac{1}{r_e} \quad r_o = \frac{1}{h_{oe}} \quad h_{re} = \frac{r_\pi}{r_\pi + r_u} = \frac{r_\pi}{r_u}$$


CE amplifier is most widely used because CE transistor have high gain than any other configuration.

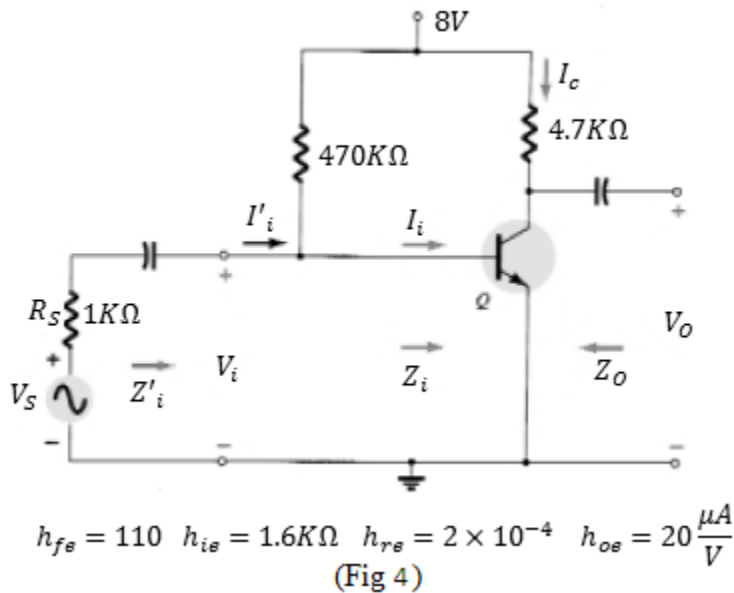5. Calculate the input impedance, output impedance, voltage gain and current gain for the given circuit (Fig 4). [10 Marks]



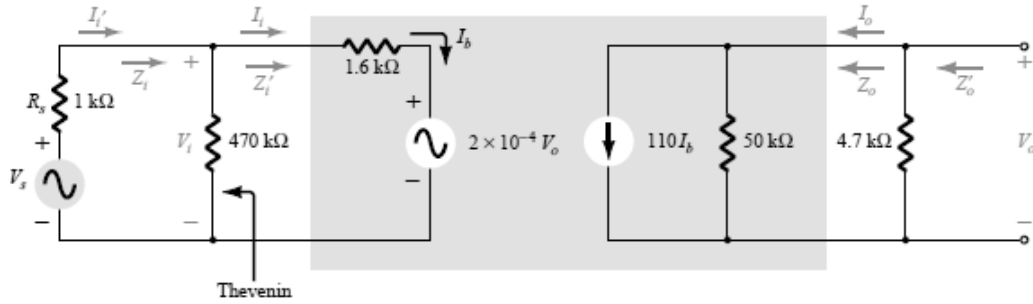

[2 marks]

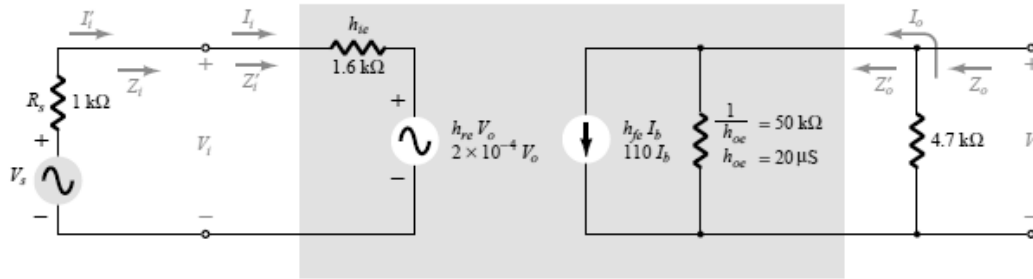

[2 marks]

$$Z'_i = h_{ie} - \frac{R_L h_{re} h_{fe}}{1 + h_{oe} R_L} \Rightarrow Z'_i = 1.6K\Omega - \frac{(4.7K\Omega)(2 \times 10^{-4})110}{1 + (20\mu S \times 4.7K\Omega)} = 1.505K\Omega$$

$$Z_i = 470K\Omega || Z'_i \Rightarrow Z_i = 1.5K\Omega$$

[2 marks]

$$A_V = \frac{-h_{fe} R_L}{h_{ie} + (h_{ie} h_{oe} - h_{re} h_{fe}) R_L} \Rightarrow A_V = \frac{-110(4.7K\Omega)}{1.6K\Omega + (1.6K\Omega \times 20\mu S - (2 \times 10^{-4}) \times 110)(4.7K\Omega)}$$

$$A_V = -313.9$$

[1 mark]

$$A_i = \frac{I_o}{I_i} = \frac{h_{fe}}{1 + h_{oe} R_L} = \frac{110}{1 + (20\mu S \times 4.7K\Omega)} = 100.54$$

[1 mark]


$$Z'_o = \frac{1}{h_{oe} - \left[\frac{h_{re} h_{fe}}{(R_S + h_{ie})} \right]} = \frac{1}{20\mu S - \left[(2 \times 10^{-4}) \times \frac{110}{(1K\Omega + 1.6K\Omega)} \right]} = 86.67K\Omega$$

$$Z_o = R_C || Z'_o \Rightarrow Z_o = 4.7K\Omega || 86.67K\Omega \Rightarrow Z_o = 4.45K\Omega$$

[2 marks]

6. (a) Determine the input impedance, output impedance, voltage gain and current gain for the circuit shown below (Fig 5).

[5 Marks]

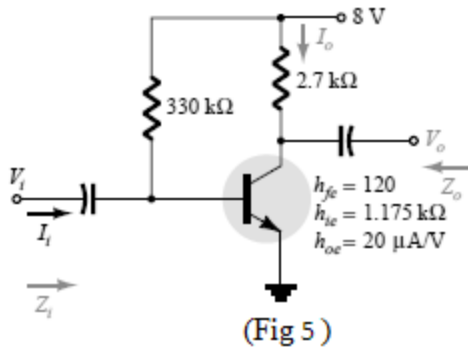

$$(a) \quad Z_i = R_B \parallel h_{ie} = 330 \text{ k}\Omega \parallel 1.175 \text{ k}\Omega \approx h_{ie} = 1.171 \text{ k}\Omega \quad [1 \text{ mark}]$$

$$(b) \quad r_o = \frac{1}{h_{oe}} = \frac{1}{20 \text{ }\mu\text{A/V}} = 50 \text{ k}\Omega$$

$$Z_o = \frac{1}{h_{oe}} \parallel R_C = 50 \text{ k}\Omega \parallel 2.7 \text{ k}\Omega = 2.56 \text{ k}\Omega \approx R_C \quad [1 \text{ mark}]$$

$$(c) \quad A_v = -\frac{h_{fe}(R_C \parallel 1/h_{oe})}{h_{ie}} = -\frac{(120)(2.7 \text{ k}\Omega \parallel 50 \text{ k}\Omega)}{1.171 \text{ k}\Omega} = -262.34 \quad [1 \text{ mark}]$$


$$A_i = -A_v \frac{Z_i}{R_C} = 262.34 \times \frac{1.171 \text{ k}\Omega}{2.7 \text{ k}\Omega} = 113.77$$

[1 Mark]

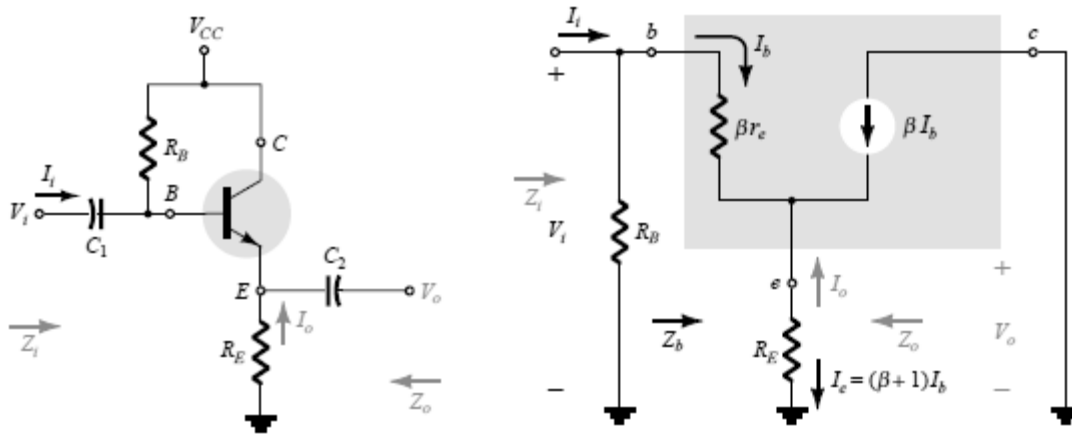(b) Analyze the r_e parameter model for emitter follower circuit and derive Z_i, Z_o, A_v, A_i

[5 Marks]

EMITTER FOLLOWER CIRCUIT/COMMON COLLECTOR CONFIGURATION:



[1 Mark]

For emitter follower circuit the output is taken from the emitter terminal. The output is slightly less than the input signal hence $A_v \approx 1$

$$V_i = I_b \beta r_e + I_e R_E \Rightarrow V_i = I_b \beta r_e + (\beta + 1) I_b R_E$$

$$Z_b = \frac{V_i}{I_b} \Rightarrow Z_b = \beta r_e + (\beta + 1) R_E$$

$$\Rightarrow Z_b \approx \beta (r_e + R_E)$$

$$Z_i = R_B \parallel Z_b$$

[1 Mark]

Output impedance is calculated by setting V_i to zero hence $Z_o = R_E \parallel r_e$

[1 Mark]

$$V_o = \frac{V_i R_E}{R_E + r_e} \Rightarrow A_v = \frac{V_o}{V_i} = \frac{R_E}{R_E + r_e} \quad \text{as } R_E + r_e \approx R_E \Rightarrow A_v \approx 1$$

[1 Mark]

the +ve sign indicates there is no phase shift between V_o & V_i

$$I_b = \frac{I_i R_B}{R_B + Z_b} \Rightarrow I_i = \frac{(R_B + Z_b)I_b}{R_B} \quad \text{and} \quad I_o = -I_e = -(\beta + 1)I_b$$


$$A_i = \frac{I_o}{I_i} = \frac{-(\beta + 1)I_b}{\left[\frac{(R_B + Z_b)I_b}{R_B} \right]} = -(\beta + 1)I_b \times \frac{R_B}{(R_B + Z_b)I_b} = \frac{-(\beta + 1)R_B}{R_B + Z_b} = \frac{-\beta R_B}{R_B + Z_b} \quad \text{as } \beta + 1 \approx \beta$$

The current gain can also be calculated as

$$A_i = -A_V \frac{Z_i}{R_E} \quad [1 \text{ Mark}]$$

7. (a) Describe the h-parameter model for emitter bias circuit and derive Z_i, Z_o, A_V, A_i using approximate hybrid model. [5 Marks]

EMITTER BIAS CONFIGURATION:

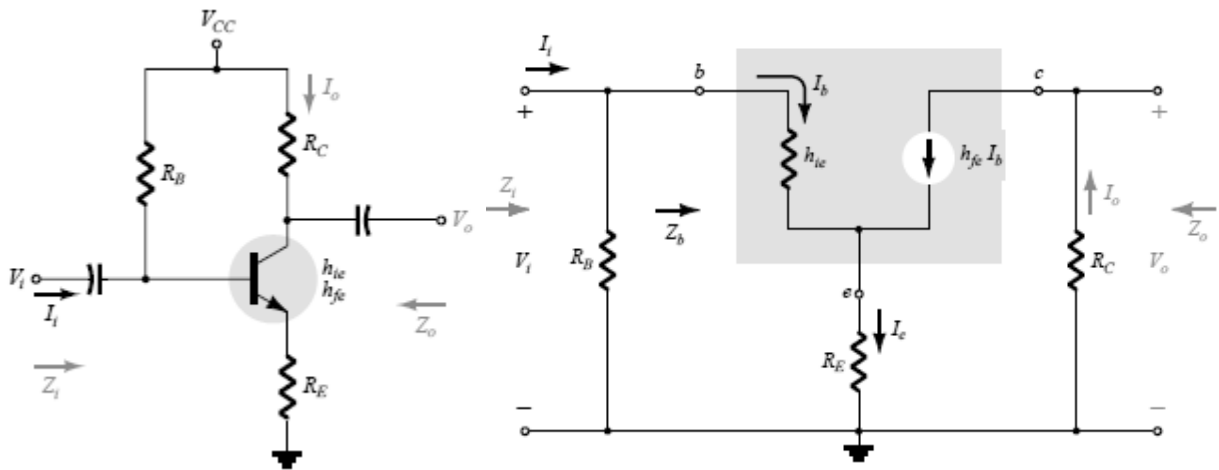

$$Z_b = h_{ie} + (h_{fe} + 1)R_E$$

$$Z_i = R_B || Z_b$$

$$Z_o = R_C$$


$$A_V = \frac{V_o}{V_i} = \frac{-h_{fe}R_C I_b}{Z_b I_b} \Rightarrow A_V = \frac{-h_{fe}R_C}{h_{fe}R_E} \Rightarrow A_V = \frac{-R_C}{R_E}$$

$$I_o = h_{fe}I_b \quad \text{and} \quad I_b = \frac{I_i R_B}{R_B + Z_b} \Rightarrow I_i = \frac{(R_B + Z_b)I_b}{R_B}$$

$$A_i = \frac{I_o}{I_i} = \frac{[h_{fe}I_b]}{\left[\frac{(R_B + Z_b)I_b}{R_B} \right]} = h_{fe}I_b \times \frac{R_B}{(R_B + Z_b)I_b} = \frac{h_{fe}R_B}{Z_b + R_B}$$


The current gain can also be calculated as $A_i = -A_V \frac{Z_i}{R_C}$

(b) For the network shown below (Fig 6), determine V_{CC} for a voltage gain of $A_V = -180$

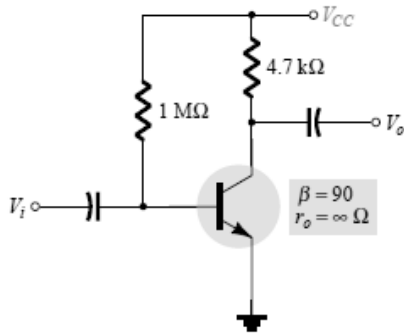

(Fig 6)

[5 Marks]

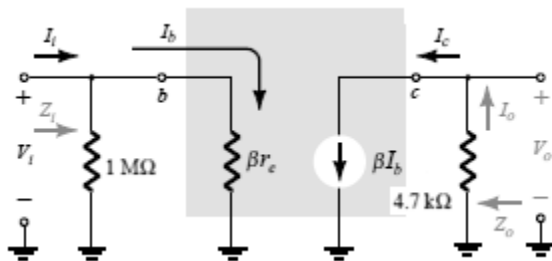

[1 Mark]

As $r_o \geq 10R_C$ (Satisfied)

$$\text{Hence } A_V = \frac{-R_C}{r_e} = -180 \Rightarrow r_e = \frac{R_C}{180} \Rightarrow r_e = 26.11\Omega$$

[1 Mark]

$$r_e = \frac{26mV}{I_E} \Rightarrow I_E = \frac{26mV}{26.11\Omega} = 0.9957mA$$

[1 Mark]

$$I_B = \frac{I_E}{(\beta + 1)} = 10.94\mu A$$

[1 Mark]

$$I_B = \frac{V_{CC} - V_{BE}}{R_B} \Rightarrow V_{CC} = I_B R_B + V_{BE} \Rightarrow V_{CC} = 11.64V$$

[1 Mark]