

Internal Assessment Test 1 – September 2016A&B-Section

Sub: Electric Circuit Analysis

Code: 15EE32


Date: 06/09/2016 Duration: 90 mins Max Marks: 50 Sem: III

Branch: EEE

Note: Answer any five full questions.

10X5=50M

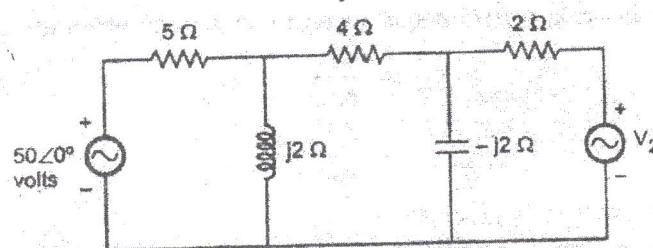
Q 1) In the circuit shown in Fig.1, determine V_2 , which results in zero current through the 4Ω resistor. Use mesh analysis. 10M



$$26.25 \angle 113^\circ \text{ V}$$

Fig. 1

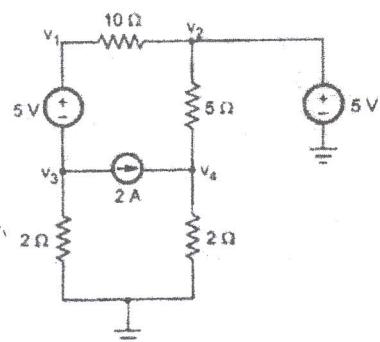
Q2. For the network shown in Fig. 2 determine the node voltages V_1 , V_2 , V_3 and V_4 using nodal analysis. 10M



$$\begin{aligned} V_1 &= 1.67 \text{ V}, \\ V_2 &= 5 \text{ V}, \\ V_3 &= -3.33 \text{ V}, \\ V_4 &= 4.28 \text{ V}. \end{aligned}$$

Fig. 2

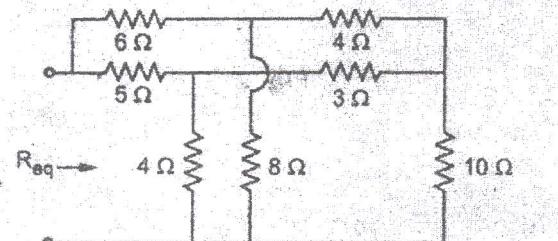
Q3. Referring Fig. 3 determine the equivalent R_{eq} by using star delta transformation. 10M



$$4.935 \Omega$$

Fig. 3

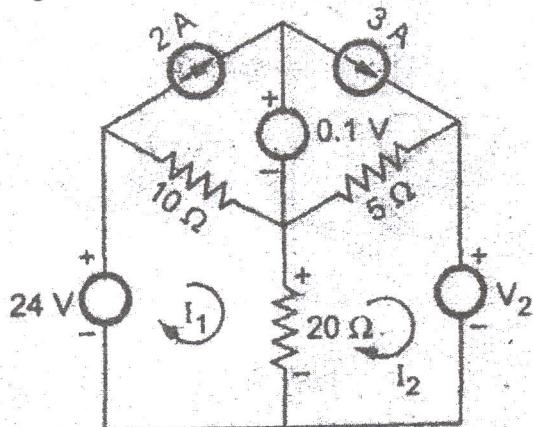
Q4. Use mesh analysis to determine what value of V_2 in the network in Fig. 4 causes $v = 0$ is
the voltage across 20Ω . 10M



$$V_2 = -7V$$

Fig. 4

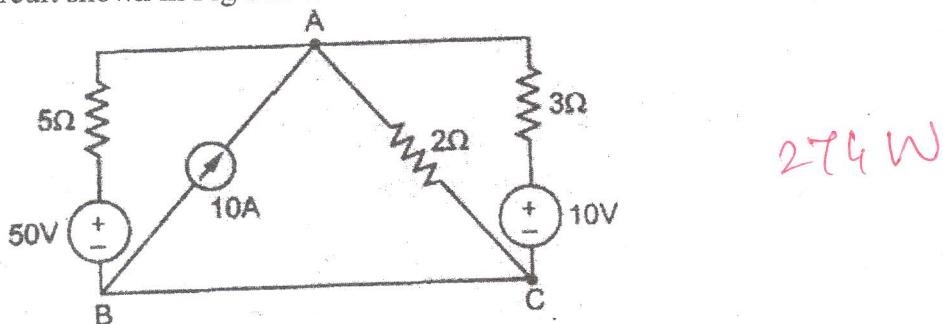Q5. Using source transformation, find the power delivered by the 50 V voltage source
in the circuit shown in Fig below. 10M



Q6) Draw the dual network shown in fig. 6. And write the equilibrium equations. 10M


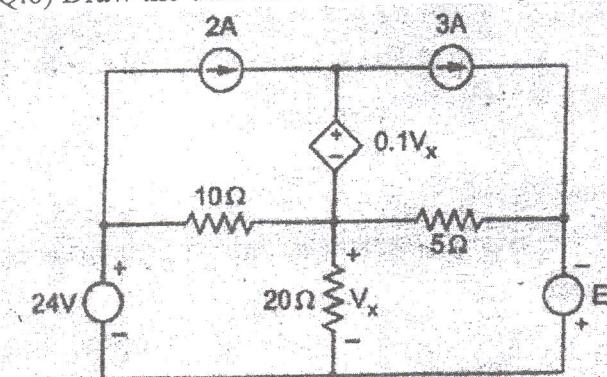


Fig. 6

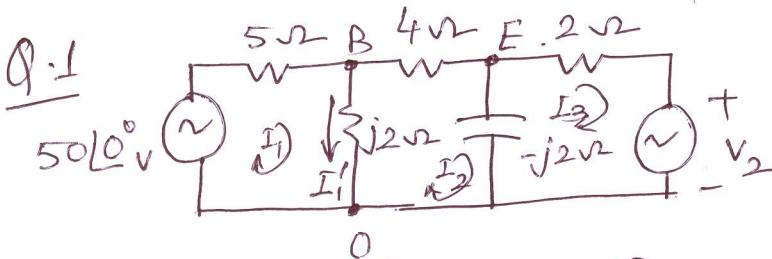

Given I through 4Ω resistor
is $0A$ - that means $I_2 = 0$.
 \therefore potential B = potential E .

Applying KVL in mesh ①,

$$-5I_1 - j2I_1 + 50\angle 0^\circ = 0$$

or, $I_1 = \frac{50\angle 0^\circ}{5+j2} = 9.2847 \angle -21.80^\circ A$.

$I'_1 = I_1$, as $I_2 = 0$.

KVL @ mesh ②:

$$-V_2 - I_3(-j2) - 2I_3 = 0$$


or, $I_3 = \frac{-V_2}{(2-j^2)}$

Potential at B w.r.t 0 is $(9.2847 \angle -21.8^\circ \times j2)$ V.

Potential at E w.r.t 0 is $(-j2) \times (-I_3)$.

$$\therefore 9.2847 \times 2 \angle 90 - 21.8^\circ = j2 \times \frac{(-V_2)}{(2-j^2)}$$
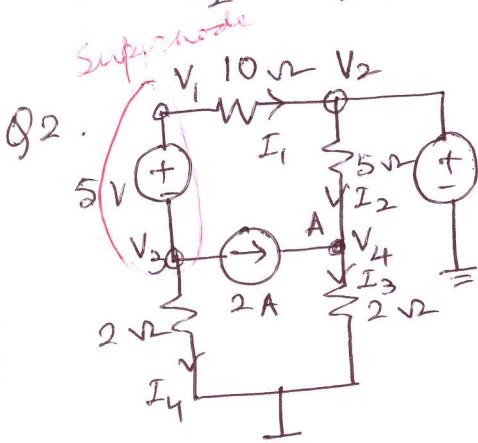
$$\therefore V_2 = 26.26 \angle 113.2^\circ \text{ Volts}$$



$$V_2 = 5 \text{ V}$$

$$V_1 - V_3 = 5 \text{ V} \quad \text{--- (1)}$$

Applying KCL at node A,

$$I_2 - I_3 + 2 = 0$$

or, $\frac{5-V_4}{5} - \frac{V_2-0}{2} + 2 = 0$


or, $V_4 = 4.285 \text{ V}$

KCL at Supernode,

$$I_1 + 2 + I_4 = 0 \quad \text{or, } \frac{V_1-5}{10} + 2 + \frac{V_3-0}{2} = 0$$


or, $\frac{V_1}{10} + \frac{V_3}{2} = -1.5 \rightarrow \text{--- (2)}$ / Solving (1) & (2)

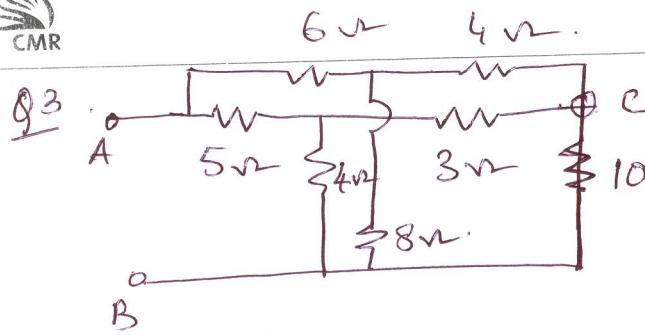$V_1 = 1.666 \text{ V}, V_3 = -3.33 \text{ V}$





Find R_{AB} using
 Δ/Δ or Δ/Δ conversion.

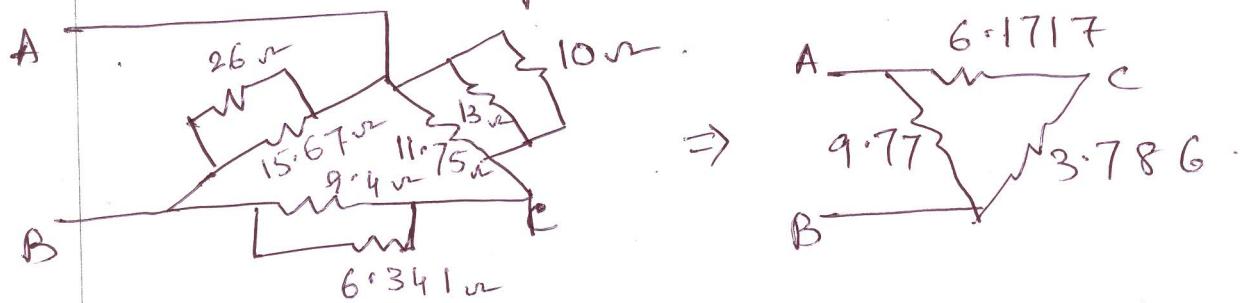Here it is clear that two stars are connected in parallel between the point A, B, & C points. Converting the stars to their equivalent delta we get




$$R_{AB} = (9.77) \parallel (6.1717 + 3.786) \Omega$$

$$= 4.9332 \Omega \text{ Ans}$$

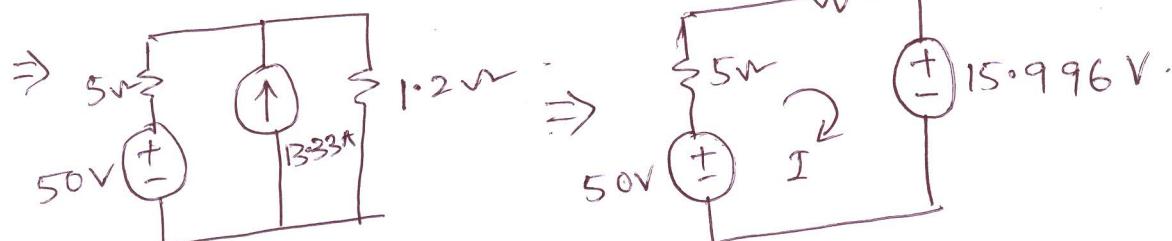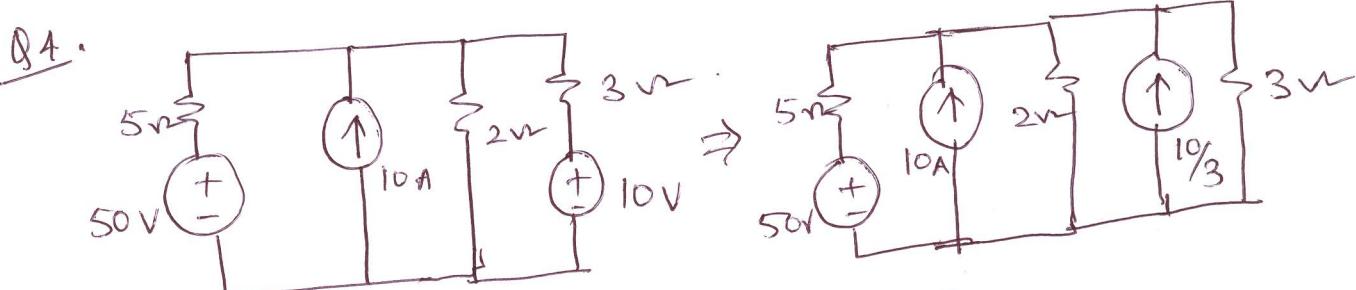

$$I = 5.4845 \text{ A}$$

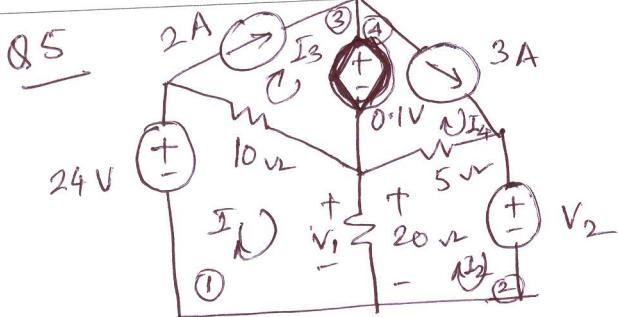\therefore power delivered by 50V source is $VI = 274.225 \text{ W}$.



Given $V_1 = 0$.

Find V_2 .

Applying KVL at mesh 1;

$$+24 - 10(I_1 - I_3) = 0 \quad | \quad \text{Constraint equations:}$$

$$I_3 = 2A, I_4 = 3A$$

KVL @ mesh 2;

$$5(I_2 - I_4) - V_2 = 0.$$


$$V_1 = 0 \therefore I_1 = I_2$$

$$\text{u, } 5I_2 - 5I_4 = V_2 \rightarrow (2)$$

Solving equations, we get $I_1 = 4.4A, I_2 = I_1 = 4.4A$

From eqn. (2)

$$V_2 = -7V.$$

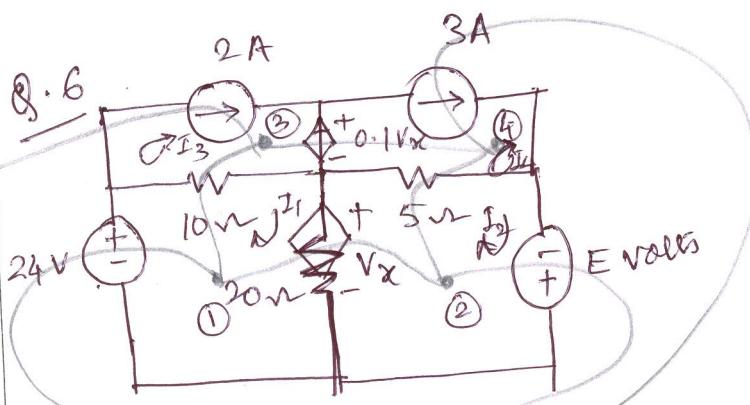


For meshes;

Equilibrium equations:-

$$I_3 = 2A; I_4 = 3A.$$

$$24 - 10(I_1 - I_3) - 20(I_1 - I_2) = 0.$$
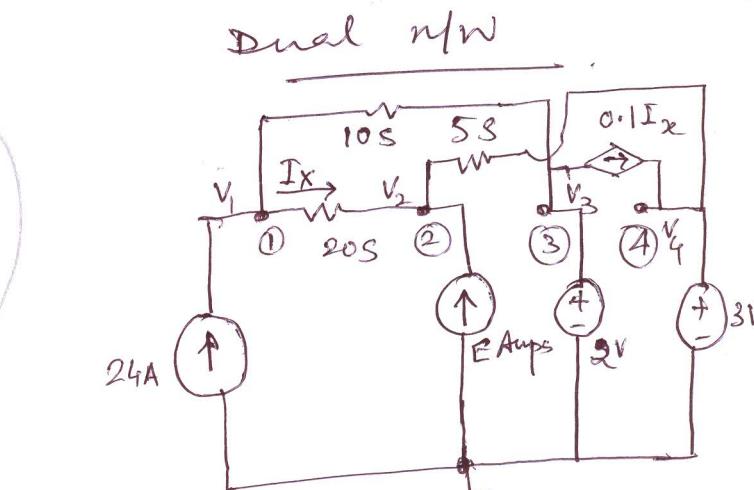
$$- 20(I_2 - I_1) - 5(I_2 - I_4) + E = 0.$$



For dual n/w, $I_x = 20(V_1 - V_2)$
Equilibrium equations

$$V_3 = 2V, V_4 = 3V.$$

$$24 - 10(V_1 - V_3) - 20(V_1 - V_2) = 0.$$

$$- 20(V_2 - V_1) - 5(V_2 - V_4) + E = 0.$$