

15EE71

## Seventh Semester B.E. Degree Examination, Feb./Mar. 2022 **Power System Analysis** – II


Time: 3 hrs.

Max. Marks: 80

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

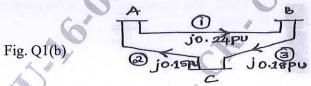- a. Define a Primitive network and hence derive an equation for calculating Y<sub>bus</sub> by Singular Transformation method. (08 Marks)
  - b. For the network shown below in Fig. Q1(b), find Y<sub>bus</sub> by singular Transformation method.
    (08 Marks)



OR

- a. Develop the Gauss Seidel load flow model for a power system with a slack bus and only PQ buses.
   (08 Marks)
  - b. For the network shown in Fig. Q2(b), determine the voltage at bus (2) at the end of 1<sup>st</sup> iteration. Line impedances are shown in P.U. Given

Bus – 1 is Slack bus with  $V_1 = 1 | \underline{0}^{\circ}$  p.u.

Bus - 2 is PQ bus with  $P_2 + j Q_2 = -5.96 + j1.4$ .

Bus 
$$-3 |V_3| = 1.02 \text{ p.u.}$$

(08 Marks)

Fig. Q2(b)

Module-2

a. Explain Newton Raphson method of Load flow analysis with flow chart.

(08 Marks)

b. Deduce the FDLF model stating clearly all assumptions.


(08 Marks)

OR

4 Formulate the Newton - Raphson equation for the system shown in Fig. Q4.

(16 Marks)

Fig. Q4

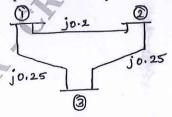

Bus	Voltage	Generation		Load	
		P	Q	P	Q
1	1.2 L0°		-	-	-
2	-	0.7	0.5	0.3	0.2
3		=	<b>3</b>	0.6	0.4

1 of 2

Module-3

- 5 a. Deduce the condition for Optimal load dispatch neglecting transmission losses. (08 Marks)
  - b. The fuel cost of 2 units is given by

 $F_1 = 1.5 + 20 P_{G1} + 0.1 P_{G1}^2 Rs/hr$ 

 $F_2 = 1.9 + 30 P_{G2} + 0.1 P_{G2}^2$ 

Where P<sub>G1</sub> and P<sub>G2</sub> are in MW. Find the optimal load scheduling neglecting loss when demand is 200MW. (08 Marks)

OR

- 6 a. Define Unit Commitment. Explain Dynamic programming method of Unit Commitment solution with flow chart. (08 Marks)
  - b. A Generator is supplying a load and an incremental change in load of 4MW requires a generator to be increased by 6MW. The incremental cost at the plant is 30 Rs/MW. hr, what is the incremental cost at receiving end. (08 Marks)

## Module-4

- 7 a. Write short notes on:
  - i) Power System reliability ii) Power System Security.

(08 Marks)

b. Explain with a flow chart, the optimal load flow solution without inequality constraints.

(08 Marks)

## OR

- 8 a. Discuss the solution procedure of optimal scheduling of Hydro thermal plants. (08 Marks)
  - b. Explain the benefits of maintenance scheduling.

(08 Marks)

Module-5

- 9 a. Derive Z<sub>bus</sub> equation when a branch is added to the partial network. (08 Marks)
  - b. Explain the steps involved in solving Swing equation using Runge Kutta method.

(08 Marks)

OR

10 The series impedances of the line are shown in Fig. Q10. Develop the  $Z_{bus}$  by  $Z_{bus}$  building algorithm, taking the elements in the order of 0 to 1, 0 to 2, 1 to 2. (16 Marks)



